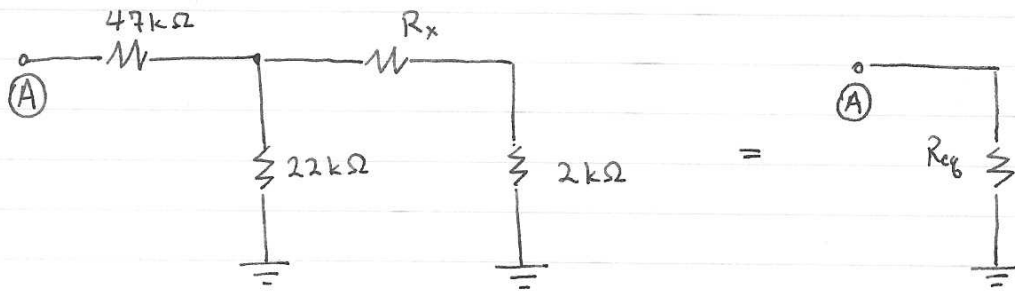


2/36



$$((R_x \oplus 2k\Omega) \parallel 22k\Omega) \oplus 47k\Omega$$

$$R_{eq} = 47 + \frac{22 \cdot (R_x + 2)}{22 + R_x + 2} = 60 \quad k\Omega$$


$$\frac{22(R_x + 2)}{22 + R_x + 2} = 13$$

$$22R_x + 44 = 286 + 13R_x + 26$$


$$9R_x = 268$$

$$R_x \approx 29.8 \quad k\Omega$$

2/40

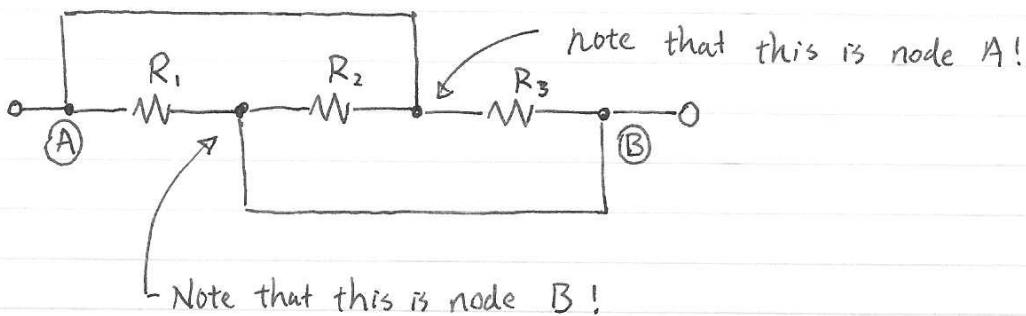


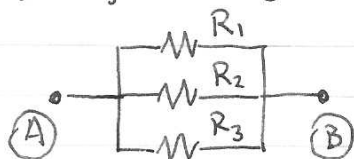R_1 , R_2 , and R_3 are each connected to both nodes A & B



$$R_{eq} = \frac{R}{3} \quad (\text{since } R_1 = R_2 = R_3 = R)$$

2/41

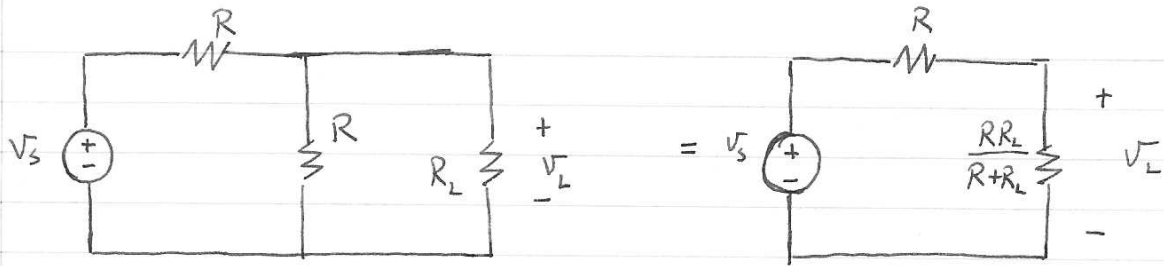


By voltage division: $V_L = V_s \times \frac{\left(\frac{R R_L}{R + R_L} \right)}{R + \frac{R R_L}{R + R_L}}$

$$= \frac{V_s R R_L}{R^2 + 2R R_L}$$

$$V_L = \frac{V_s R_L}{R + 2R_L}$$


2/43

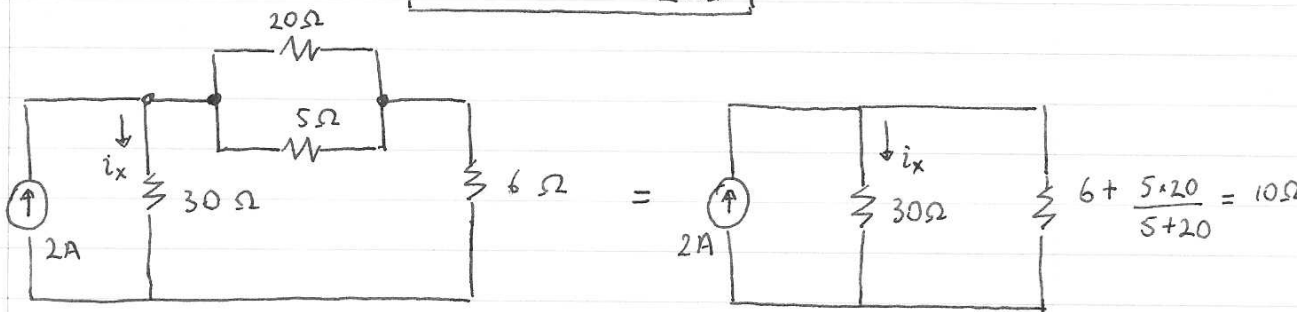

Current division: $i_x = 2A \times \frac{10}{10+30}$

$$i_x = \frac{1}{2} A$$

2/50

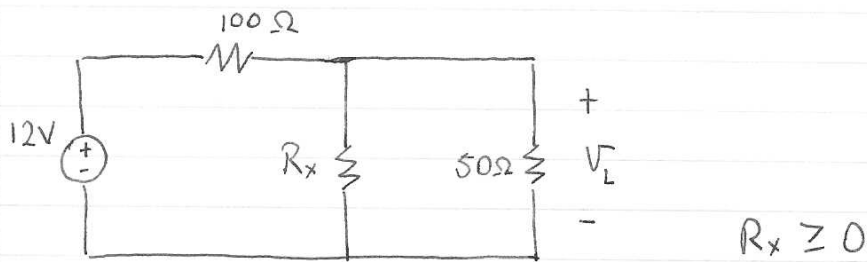

It is impossible to choose R_x s.t. $V_L = 6V$

Proof

V_L is the voltage drop across the equivalent resistance obtained by combining R_x & the 50Ω resistor in parallel,

$$R_{eq} = \frac{50 R_x}{50 + R_x} \quad \text{where } 0 \leq R_x$$

$$R_{eq} < 50 \quad \forall R_x \geq 0$$



Assume $V_L = 6V$

$$\Rightarrow R_{eq} = 100\Omega \quad \text{Contradiction!}$$


\therefore no $R_x \geq 0$ can be chosen s.t. $V_L = 6V$ ■

MAE 140 Fa 07 HW 2

2/53

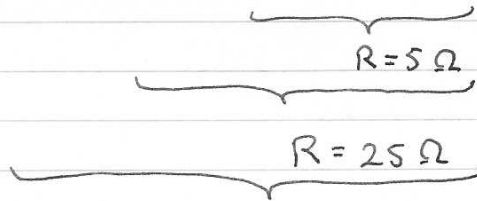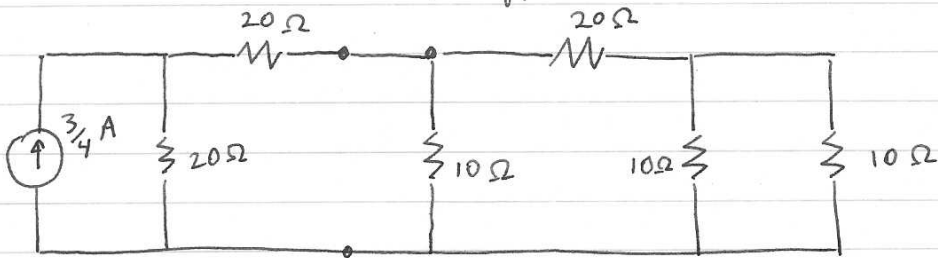

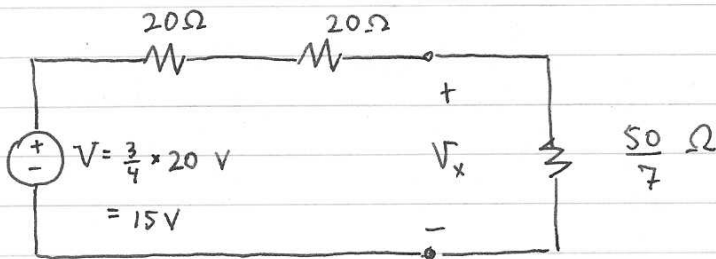
$$R = \frac{10 \times 25}{10 + 25} = \frac{50}{7} \Omega$$




$$V_x = (15V) \times \frac{50/7}{40 + 50/7} = \boxed{2.27 V}$$

MAE 140 Fa 07 HW#2

2/55

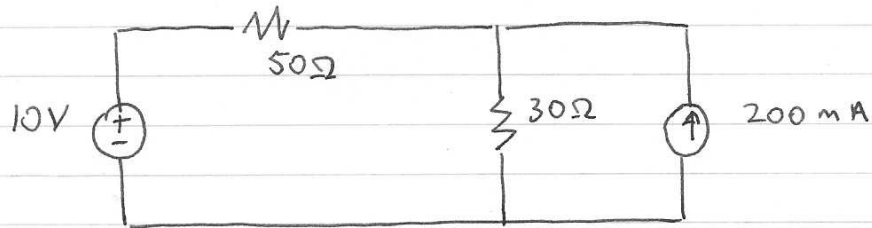

11

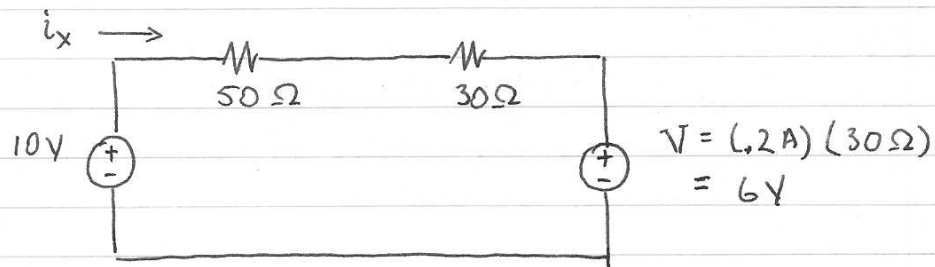



KVL

$$-10 + i_x(80) + 6 = 0$$

$$i_x = 50 \text{ mA}$$

MAE 140 Fa 07 HW # 2

3/36 (a)

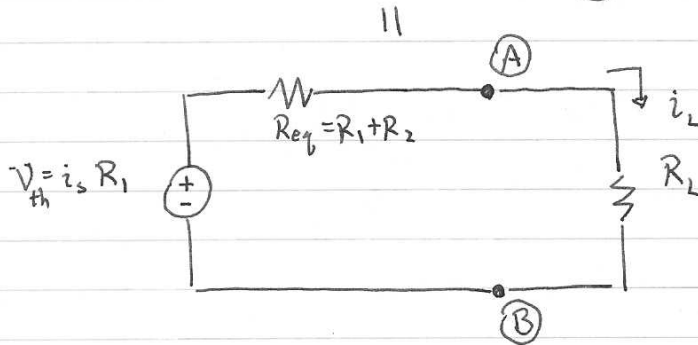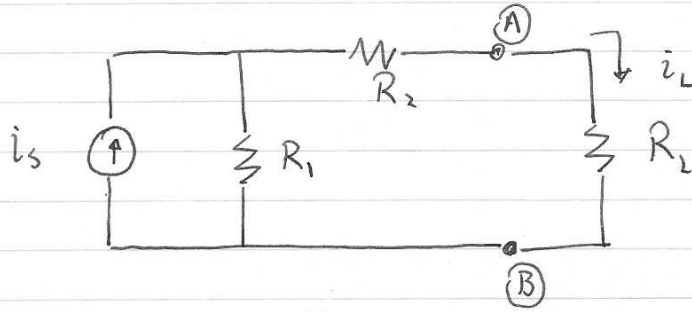

Note that:

$$I_{sc} = \frac{V_{th}}{R_{eq}}$$

$$\begin{aligned} V_{th} &= i_s R_1 \\ R_{eq} &= R_1 + R_2 \\ I_{sc} &= i_s \frac{R_1}{R_1 + R_2} \end{aligned}$$

(b)

$$i_L = \frac{V_{th}}{R_{eq} + R_L}$$


$$i_L = \frac{i_s R_1}{R_1 + R_2 + R_L}$$

(c)

$$i_L = i_s \times \frac{R_1}{R_1 + (R_2 + R_L)} \quad \text{by current division}$$

MAE 140 Fa 07 HW 2

3/39

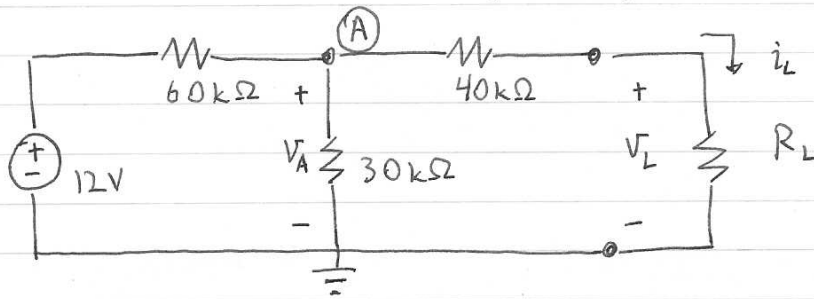

Open Circuit test:

$(R_L \rightarrow \infty)$

$$V_L = V_{oc} = 12 \cdot \frac{30}{30+60} \text{ V}$$

$$\boxed{V_{th} = 4\text{V}}$$

$(V_{oc} = V_{th})$

Short Circuit test:

$(R_L = 0)$

$i_L = i_{sc}$

$$V_A = 12 \cdot \frac{120/7}{60 + 120/7}$$

$$i_{sc} = \frac{V_A}{40}$$

$$\Rightarrow \boxed{I_N = \frac{1}{15} \text{ mA}}$$


$$\boxed{R_{eq} = \frac{V_{th}}{I_N} = 60\text{k}\Omega}$$

$$V_L = V_{th} \times \frac{R_L}{60+R_L} = 4 \times \frac{R_L}{60+R_L}$$

$$P_L = \frac{V_L^2}{R_L} \longrightarrow P_L = \begin{cases} 66.1 \mu\text{W} & \text{when } R_L = 50 \text{ k}\Omega \\ 47.3 \mu\text{W} & \text{when } R_L = 200 \text{ k}\Omega \end{cases}$$

MAE 140 Fa 07 HW 2

2/62

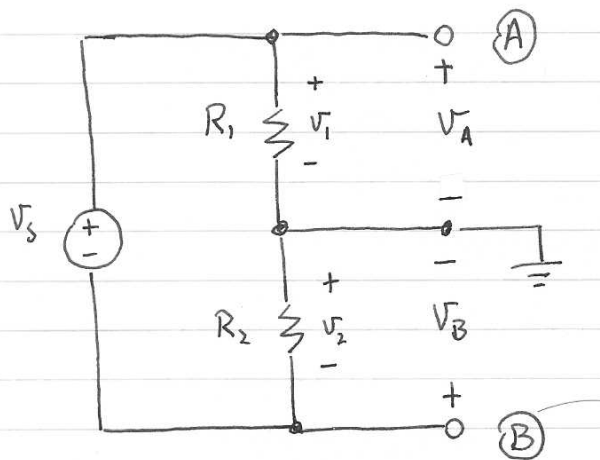

$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$

$$V_A = V_1$$

$$\Rightarrow \boxed{V_A = \frac{V_s R_1}{R_1 + R_2}}$$

$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$

$$V_B = -V_2$$

$$\Rightarrow \boxed{V_B = -\frac{V_s R_2}{R_1 + R_2}}$$