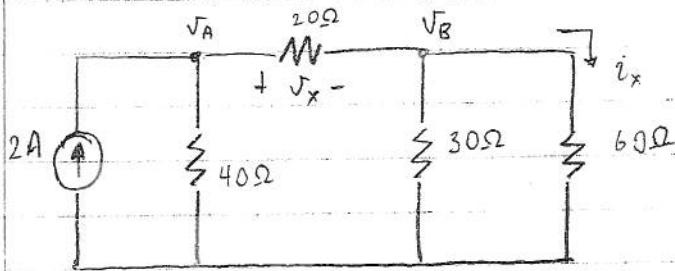


MAE 140 Fa 07 HW#3 3/1, 3, 4, 5, 8, 11, 13, 19, 71, 75

3/1



(a) KCL @ A

$$V_A \left(\frac{1}{40} \right) + (V_A - V_B) \left(\frac{1}{20} \right) = 2$$

$$\Rightarrow V_A \left(\frac{1}{40} + \frac{1}{20} \right) + V_B \left(-\frac{1}{20} \right) = 2 \quad //$$

KCL @ B

$$(V_B - V_A) \left(\frac{1}{20} \right) + V_B \left(\frac{1}{30} \right) + V_B \left(\frac{1}{60} \right) = 0$$

$$V_A \left(-\frac{1}{20} \right) + V_B \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{60} \right) = 0 \quad //$$

$$\boxed{\begin{bmatrix} 3/40 & -1/20 \\ -1/20 & 1/10 \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 2 \\ 0 \end{pmatrix}}$$

(b) From (a) (using a calculator)

$$V_A = 40 \text{ V}$$

$$V_B = 20 \text{ V}$$


$$V_x = V_A - V_B$$

$$\boxed{V_x = 20 \text{ V}}$$

$$i_x = \frac{V_B}{60}$$

$$\boxed{i_x = 1/3 \text{ A}}$$

3/3

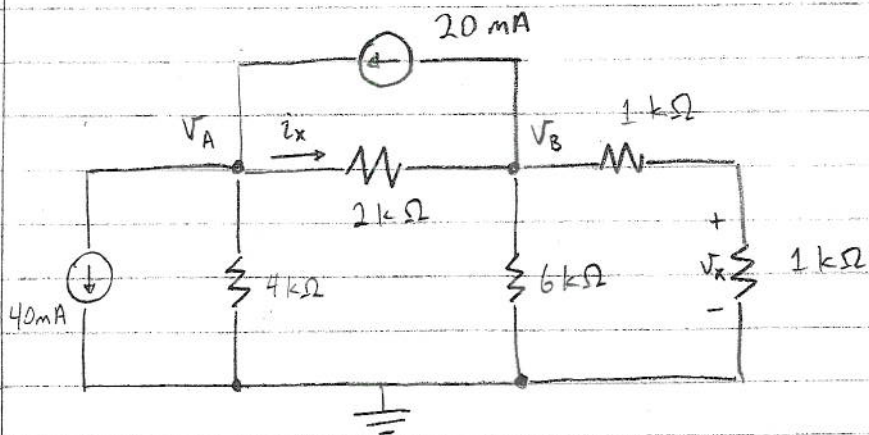

$$(a) \quad \begin{array}{l} \text{KCL @ A:} \\ \text{KCL @ B:} \end{array} \quad \begin{bmatrix} \frac{1}{4} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} + \frac{1}{6} + \frac{1}{1+1} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 20 - 40 \\ -20 \end{pmatrix}$$

$$\begin{bmatrix} \frac{3}{4} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{7}{6} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} -20 \\ -20 \end{pmatrix}$$

$$(b) \quad \begin{array}{l} V_A = -53\frac{1}{3} \text{ V} \\ V_B = -40 \text{ V} \end{array}$$


$$V_x = V_B \frac{1}{1+1} \quad (\text{voltage divider})$$

$$\boxed{V_x = -20 \text{ V}}$$

$$i_x = \frac{V_A - V_B}{2} \text{ mA}$$

$$\boxed{i_x = -6\frac{2}{3} \text{ mA}}$$

3/4

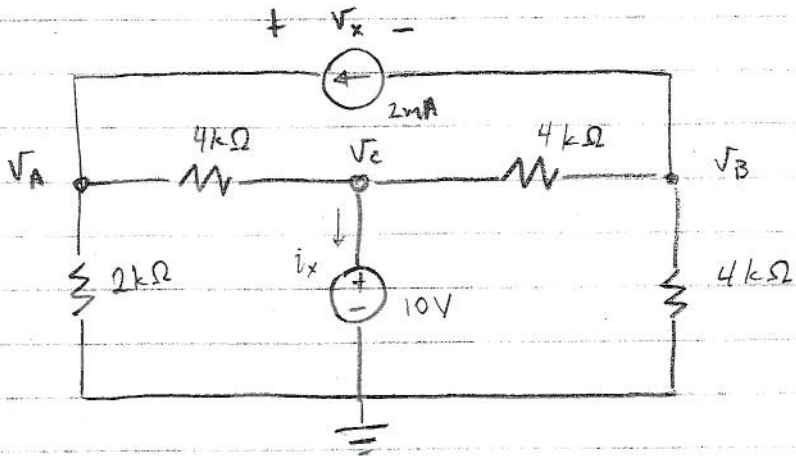

Note $V_c = 10 \text{ V}$

KCL @ A

$$V_A \left(\frac{1}{2} + \frac{1}{4} \right) = 2 + \frac{V_c}{4}$$

$$\frac{3}{4} V_A = \frac{9}{2}$$

$$\therefore V_A = 6 \text{ V}$$

KCL @ B

$$V_B \left(\frac{1}{4} + \frac{1}{4} \right) = -2 + \frac{V_c}{4}$$

$$\frac{V_B}{2} = \frac{1}{2}$$

$$\therefore V_B = 1 \text{ V}$$

$$V_x = V_A - V_B$$


$$V_x = 5 \text{ V}$$

$$i_x = \frac{V_A - V_c}{4} + \frac{V_B - V_c}{4}$$

$$= \frac{1}{4} (6 - 10 + 1 - 10)$$

$$i_x = -\frac{13}{4} \text{ A}$$

3/5

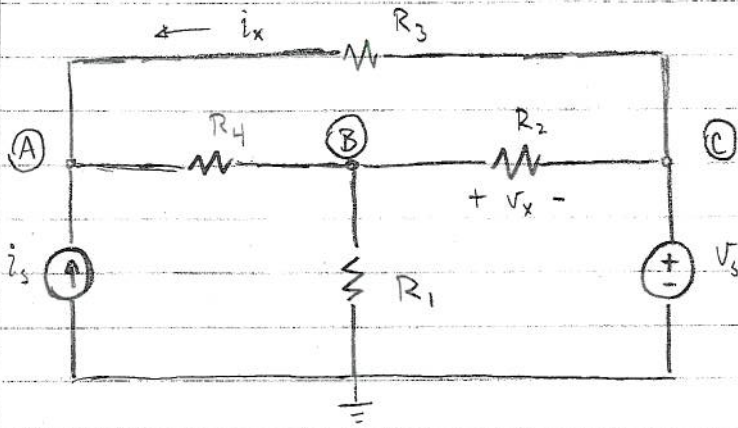

a) Note that $v_c = v_s$

$$\begin{array}{l} \text{KCLA} \\ \text{KCLB} \end{array} \begin{bmatrix} \frac{1}{R_4} + \frac{1}{R_3} & -\frac{1}{R_4} \\ -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \end{bmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} i_s + v_s/R_3 \\ v_s/R_3 \end{pmatrix}$$

b) $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$

$$v_s = 20 \text{ V}, \quad i_s = 2 \text{ mA}$$

$$\Rightarrow v_A = 28 \text{ V}$$

$$v_B = 16 \text{ V}$$


$$i_x = \frac{v_s - v_A}{R_3}$$

$$i_x = -0.8 \text{ mA}$$

$$v_x = v_B - v_s$$

$$v_x = -4 \text{ V}$$

3/8

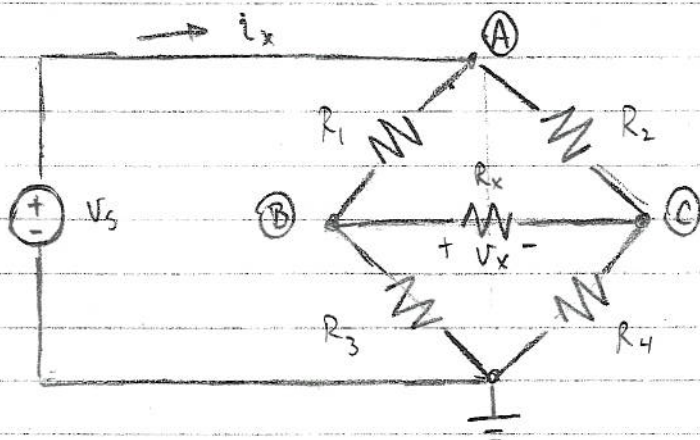(a) Note $V_A = V_s$

KCL @ B

KCL @ C

$$\begin{cases} \frac{1}{R_1} + \frac{1}{R_x} + \frac{1}{R_3} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & \frac{1}{R_2} + \frac{1}{R_x} + \frac{1}{R_4} \end{cases} \begin{pmatrix} V_B \\ V_C \end{pmatrix} = \begin{pmatrix} V_s/R_1 \\ V_s/R_2 \end{pmatrix}$$

(b) $R_1 = R_4 = 10^3 \Omega$

$R_2 = R_3 = 250 \Omega$

$R_x = 500 \Omega$

$V_s = 15 \text{ V}$

$V_B = 5 \text{ V}$

$V_C = 10 \text{ V}$


$$i_x = \frac{V_s - V_B}{R_1} + \frac{V_s - V_C}{R_2}$$

$$i_x = 30 \text{ mA}$$

$$V_x = V_B - V_C$$

$$V_x = -5 \text{ V}$$

3/11

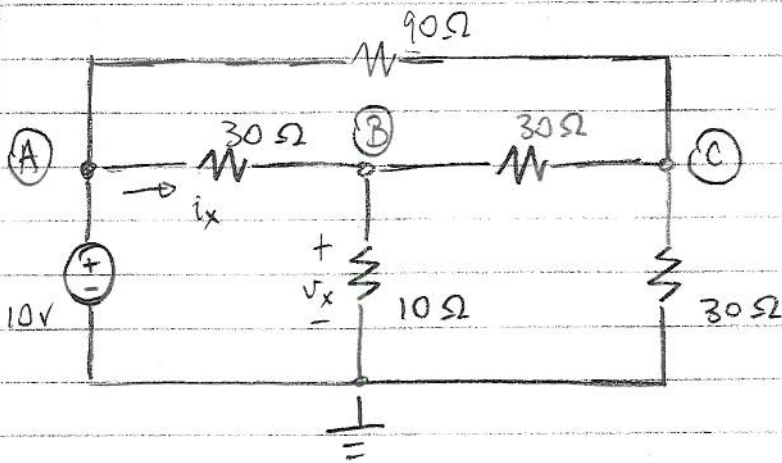

Note $V_A = 10\text{ V}$

$$\begin{array}{l} \text{KCL B} \\ \text{KCL C} \end{array} \left[\begin{array}{cc} \frac{1}{30} + \frac{1}{10} + \frac{1}{30} & -\frac{1}{30} \\ -\frac{1}{30} & \frac{1}{30} + \frac{1}{30} + \frac{1}{90} \end{array} \right] \begin{array}{l} \left(\begin{array}{c} V_B \\ V_C \end{array} \right) = \left(\begin{array}{c} 10/30 \\ 10/90 \end{array} \right) \end{array}$$

$$V_B = 2.5\text{ V}$$

$$V_C = 2.5\text{ V}$$


$$V_x = V_B$$

$$\boxed{V_x = 2.5\text{ V}}$$

$$i_x = \frac{10 - V_B}{30}$$

$$\boxed{i_x = 250\text{ mA}}$$

3/13

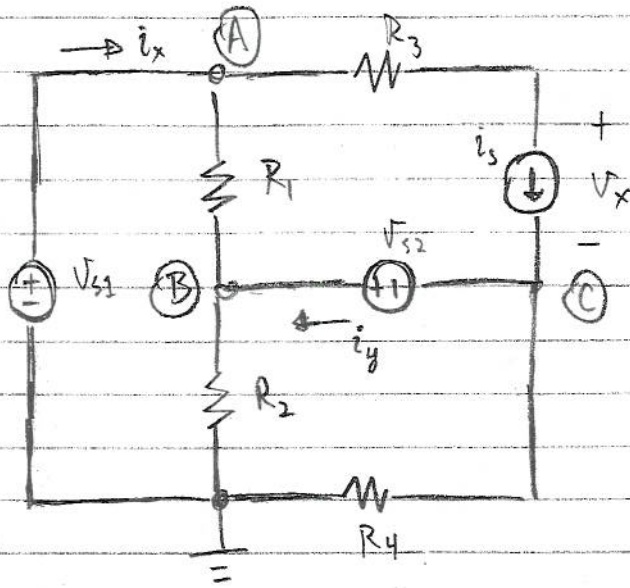

(a) note that $\begin{cases} V_C + V_{s2} = V_B \Leftrightarrow V_C = V_B - V_{s2} \\ V_A = V_B \end{cases} //$

$$\text{KCL B: } V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = i_y + \frac{V_{s1}}{R_1} \quad (1)$$

$$\text{KCL C: } \frac{V_B - V_{s2}}{R_4} = -i_y + i_s \quad (2)$$

Combine (1) and (2)

$$V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{V_B}{R_4} - \frac{V_{s2}}{R_4} = \frac{V_{s1}}{R_1} + i_s$$

$$V_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) = \frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_4} + i_s //$$

(b) $R_1 = R_2 = 10 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, $R_4 = 1 \text{ k}\Omega$, $i_s = 2.5 \text{ mA}$, $V_{s1} = 12 \text{ V}$, $V_{s2} = 0.5 \text{ V}$

$$\Rightarrow V_B = 3.5 \text{ V}$$

$$V_C = 3 \text{ V}$$

$$V_x = V_A - i_s R_3 - V_C$$


$$\boxed{V_x = 4 \text{ V}}$$

$$i_x = \frac{V_{s1} - V_B}{R_1} + i_s$$

$$\boxed{i_x = 3.35 \text{ mA}}$$

$$\boxed{P = V_{s1} i_x = 40.2 \text{ W generated}}$$

3/19

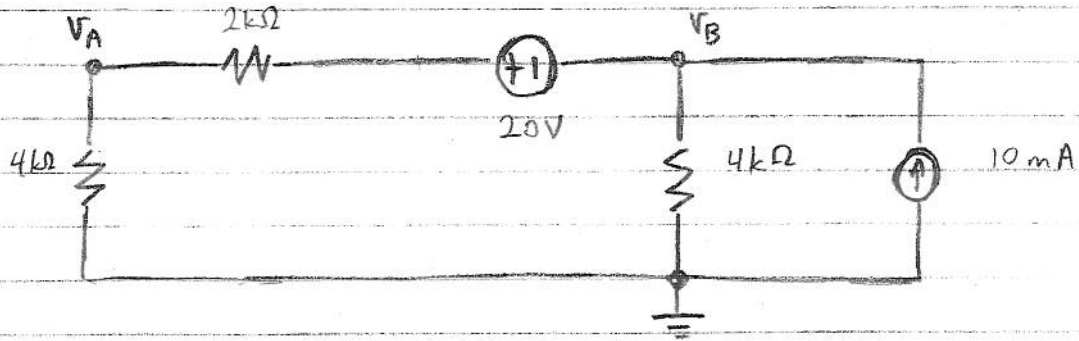

$$\text{KCL @ A: } V_A \left(\frac{1}{4} \right) + (V_A - 20 - V_B) \left(\frac{1}{2} \right) = 0$$

$$\Rightarrow V_A \left(\frac{3}{4} \right) + V_B \left(-\frac{1}{2} \right) = 10$$


$$\text{KCL @ B: } V_B \left(\frac{1}{4} \right) + (V_B + 20 - V_A) \left(\frac{1}{2} \right) = 10$$

$$\Rightarrow V_A \left(-\frac{1}{2} \right) + V_B \left(\frac{3}{4} \right) = -10 + 10$$

$$\begin{bmatrix} 3/4 & -1/2 \\ -1/2 & 3/4 \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \end{pmatrix}$$

$V_A = 24 \text{ V}$
$V_B = 16 \text{ V}$

3/71

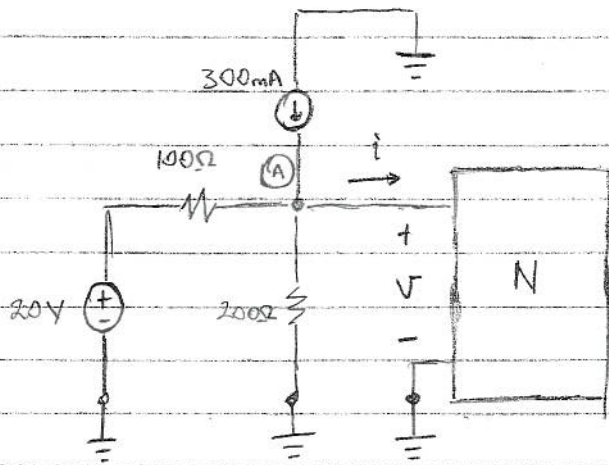

$$i = (5 \times 10^{-3} v - 0.5) \text{ A} \quad * \text{note that } v_A = v$$

KCL @ A:

$$\frac{1}{100}(v_A - 20) + \frac{v_A}{200} + 5 \times 10^{-3} v_A = 0.3 + 0.5$$


$$\frac{v_A}{50} = 1$$

$$\Rightarrow \boxed{v_A = 50 \text{ V}}$$


3.75

Re-draw circuits:

$$0 \leq R_v \leq 100$$

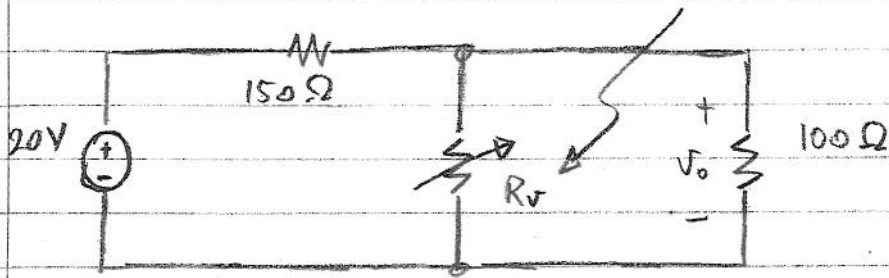

Circuit 1

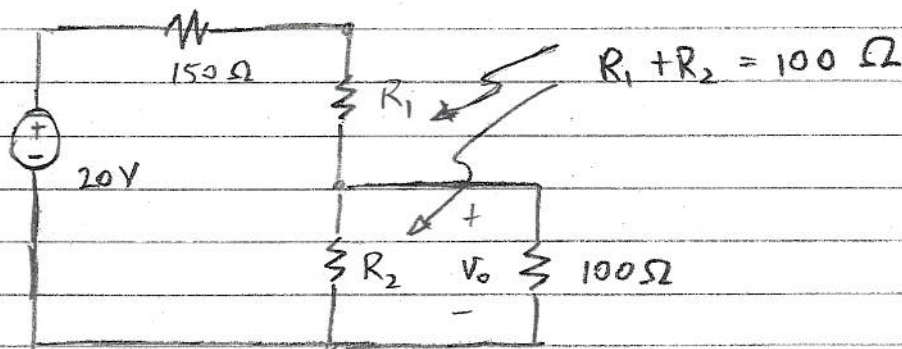

Circuit 2

For circuit 1

$$v_o = 20 \cdot \left(\frac{100 R_v}{100 + R_v} \right) \frac{150 + 100 R_v}{100 + R_v}$$

$$v_o = 20 \cdot \frac{100 R_v}{15,000 + 250 R_v}$$

For circuit 2

$$v_o = 20 \cdot \frac{100 R_2}{(150 + R_1)(100 + R_2) + 100 R_2}$$

$$\text{where } R_1 + R_2 = 100$$

$$v_o = 20 \cdot \frac{100 R_2}{25,000 + 250 R_2 - R_2^2}$$

From the voltage division formulae for each circuit, one can see that for a desired v_o close to zero, v_o is more sensitive to changes in R_v than R_2 , i.e. controlling the first circuit is more difficult when the desired output is close to zero. Physically, this is similar to turning a volume knob very little and suddenly having your eardrums blasted out. One can also argue that cct 2 drains less power.