

MAE 140 HW #4

3.10, 3.11, 3.13, <sup>3.20</sup> 3.26, 3.28, 3.31, 4.1, 4.7, 4.13

$$3.10) a) \begin{bmatrix} 2+2+4 \text{ k}\Omega & -4 \text{ k}\Omega \\ -4 \text{ k}\Omega & 4+2+4 \text{ k}\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 5-15 \text{ V} \\ 15 \text{ V} \end{bmatrix}$$

$$\rightarrow \begin{bmatrix} 8 & -4 \\ -4 & 10 \end{bmatrix} \text{ k}\Omega \begin{bmatrix} i_A \\ i_B \end{bmatrix} \text{ mA} = \begin{bmatrix} -10 \\ 15 \end{bmatrix} \text{ V}$$

$$b) i_A = -0.625 \text{ mA}, i_B = 1.25 \text{ mA}$$

$$i_x = -i_A + i_B = \boxed{1.875 \text{ mA}}$$

$$V_x = i_B \cdot (4 \text{ k}\Omega) = (1.25)(4) \text{ V} = \boxed{5 \text{ V}}$$

$$3.11) a) \begin{bmatrix} 30+10 & -10 & -30 \\ -10 & 10+30+30 & -30 \\ -30 & -30 & 30+90+30 \end{bmatrix} \Omega \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} A = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} V$$


$$\rightarrow \begin{bmatrix} 40 & -10 & -30 \\ -10 & 70 & -30 \\ -30 & -30 & 150 \end{bmatrix} \Omega \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} A = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} V$$

$$b) i_A = 0.333, i_B = 0.0833, i_C = 0.0833$$

$$V_x = (i_A - i_B)(10 \Omega) = \boxed{2.5 V}$$

$$i_x = i_A - i_C = \boxed{0.25 A}$$

3.13) a)

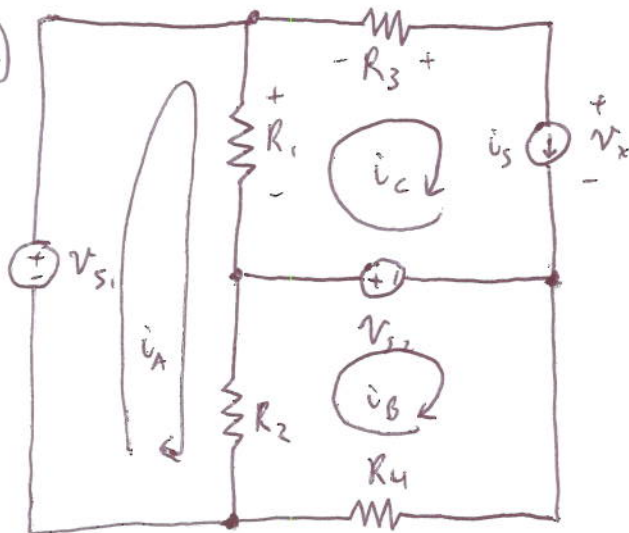

$$\begin{bmatrix} R_1+R_2 & -R_2 & -R_1 \\ -R_2 & R_2+R_4 & 0 \\ -R_1 & 0 & R_1+R_3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} v_{s1} \\ -v_{s2} \\ v_{s2} - v_x \end{bmatrix} \begin{matrix} +R_1 i_s \\ +0 \cdot i_s \\ \end{matrix}$$

$\hookrightarrow i_C = i_s$

$$\rightarrow \begin{bmatrix} R_1+R_2 & -R_2 \\ -R_2 & R_2+R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} v_{s1} + R_1 i_s \\ -v_{s2} \end{bmatrix}, \quad i_C = i_s$$

$$b) \begin{bmatrix} 20 & -10 \\ -10 & 11 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 12 + 10(2.5) \\ -0.5 \end{bmatrix} \rightarrow \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 3.35 \\ 3.00 \end{bmatrix} \text{ mA}$$

$$v_x = v_{s2} - v_{R1} - v_{R3} = 0.5 \text{ V} - (i_C - i_A)R_1 - (i_s)R_3$$

$$= 0.5 - (2.5 - 3.35)10 - (2.5)2$$

$$\rightarrow v_x = 4 \text{ V}$$

$$i_x = i_A \rightarrow i_x = 3.35 \text{ mA}$$


$$c) (\text{power supplied by } v_{s1}) = v_{s1} \cdot i_A = (12 \text{ V})(3.35 \text{ mA})$$

$$= 40.2 \text{ mW}, \text{ or according to book's convention, } -40.2 \text{ mW}$$


$$3.20) \begin{bmatrix} 6 & -6 & 0 \\ -6 & 6+2+8 & -2 \\ 0 & -2 & 4+2 \end{bmatrix} \text{ k}\Omega \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} \text{ mA} = \begin{bmatrix} 5+10 \\ 0 \\ -10 \end{bmatrix} \text{ V}$$

$$\rightarrow \begin{cases} i_A = 3.75 \text{ mA} \\ i_B = 1.25 \text{ mA} \\ i_C = -1.25 \text{ mA} \end{cases}$$


3.26) Find  $v_o$  by superposition:

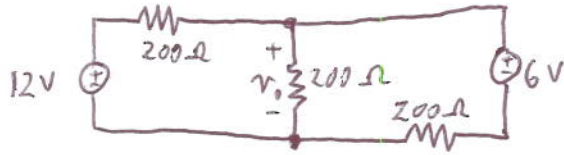

set 12V to zero ...

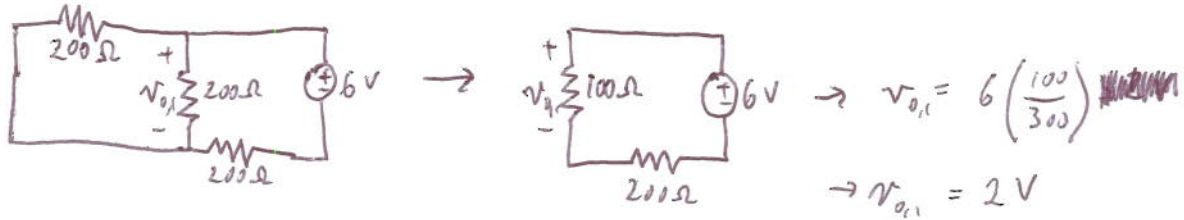


now set 6V to zero ...


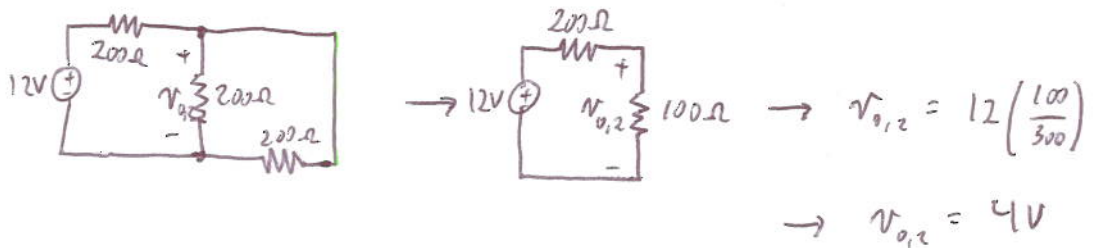


$$v_o = v_{o,1} + v_{o,2} = \boxed{6V}$$

3.28) use superposition to find  $v_o$

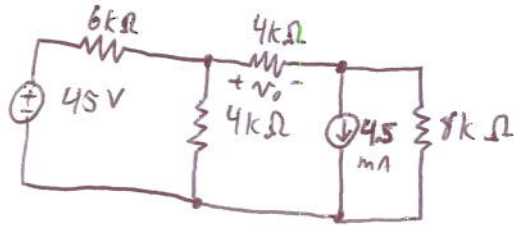


set 45V to zero...

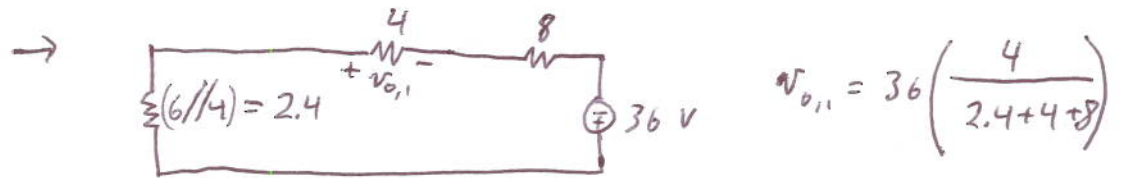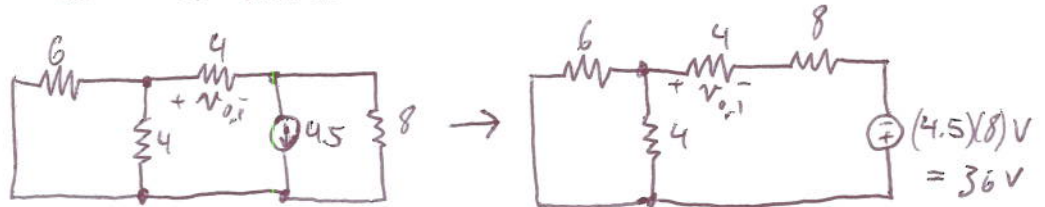

$$\rightarrow v_{o,1} = 10V$$

now set 4.5mA to zero...

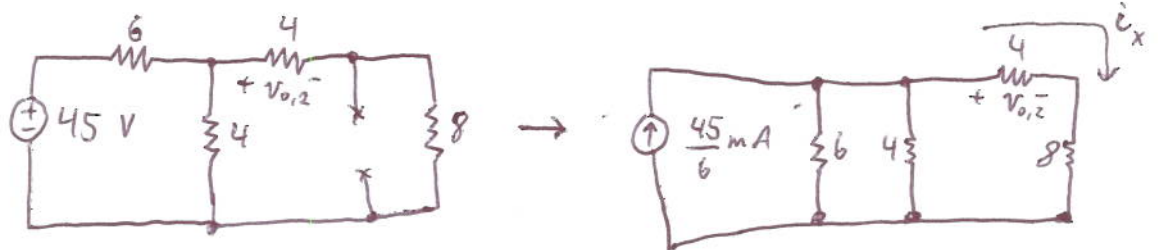


$$i_x = \frac{45}{6} \text{ mA} \left( \frac{\left(\frac{1}{4+8}\right)}{\frac{1}{6} + \frac{1}{4} + \frac{1}{4+8}} \right) = 1.25 \text{ mA}$$


$$v_{o,2} = (i_x)(4k\Omega) = 5V$$

$$v_o = v_{o,1} + v_{o,2} = \boxed{15V}$$


3.31) use superposition to find  $v_o$

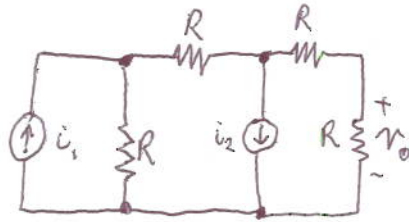

set  $i_1 = 0 \dots$

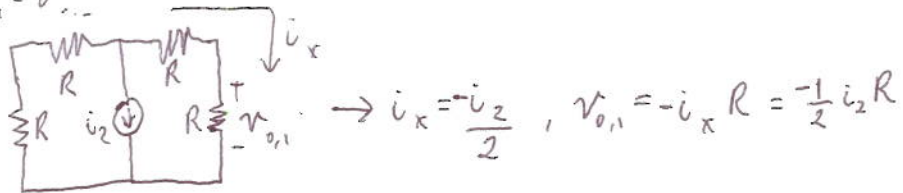

now set  $i_2 = 0 \dots$

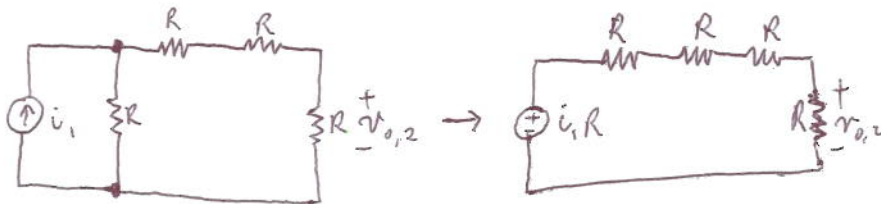


$$v_{o,2} = i_1 R \left( \frac{R}{4R} \right) = \frac{1}{4} i_1 R$$

$$v_o = v_{o,1} + v_{o,2} = -\frac{1}{2} i_2 R + \frac{1}{4} i_1 R = \boxed{\frac{R(i_1 - 2i_2)}{4}}$$



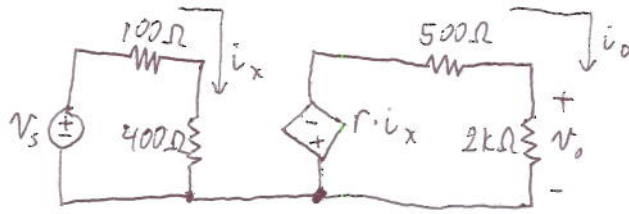4.1) Find  $\frac{V_o}{V_s}$  and  $\frac{i_o}{i_x}$  For  $r = 4\text{ k}\Omega$



$$i_o = \frac{-r i_x}{2.5\text{ k}\Omega} \rightarrow \frac{i_o}{i_x} = \frac{-r}{2.5\text{ k}\Omega} = \frac{-4}{2.5} = -1.6$$

$$\boxed{\frac{i_o}{i_x} \triangleq k_I = -1.6}$$



$$\left. \begin{aligned} i_x &= \frac{V_s}{(100 + 400)\Omega} \rightarrow r_s = 500\Omega (i_x) \\ V_o &= i_o (2\text{ k}\Omega) \end{aligned} \right\} \frac{V_o}{V_s} = \frac{i_o (2\text{ k}\Omega)}{i_x (500\Omega)}$$

$$\frac{V_o}{V_s} = 4 \frac{i_o}{i_x} = -6.4$$

$$\boxed{\frac{V_o}{V_s} \triangleq k_V = -6.4}$$



4.7) Find  $v_o$ :

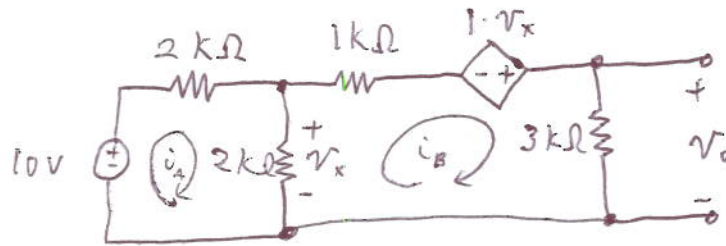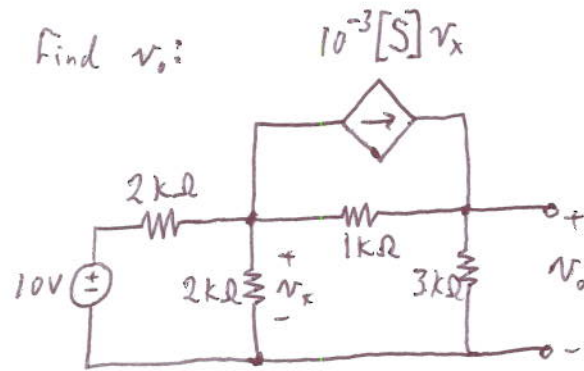

$$\begin{bmatrix} 2+2 & -2 \\ -2 & 2+1+3 \end{bmatrix} \text{k}\Omega \begin{bmatrix} i_A \\ i_B \end{bmatrix} \text{mA} = \begin{bmatrix} 10 \\ v_x \end{bmatrix} \text{V}$$


$v_x = (i_A)(2\text{k}\Omega)$

$$\begin{bmatrix} 4 & -2 \\ -2-2 & 6 \end{bmatrix} \text{k}\Omega \begin{bmatrix} i_A \\ i_B \end{bmatrix} \text{mA} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \text{V}$$

$$\rightarrow i_A = 3.333 \text{ mA}, \quad i_B = 1.667 \text{ mA}$$

$$v_o = (i_B)(3\text{k}\Omega) = \boxed{5\text{V}}$$

4.13) Find  $R_{IN}$

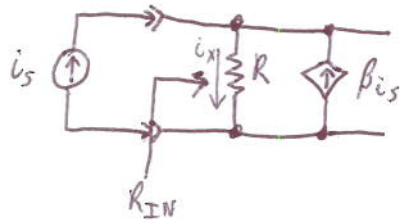

$$R_{IN} = \frac{V_{IN}}{i_{IN}} = \frac{(i_x)R}{i_s}, \quad i_x = i_s + \beta i_s = i_s(1+\beta)$$

$$R_{IN} = \frac{i_s(1+\beta)R}{i_s} = (1+\beta)R$$

$$R_{IN} = R(\beta+1)$$