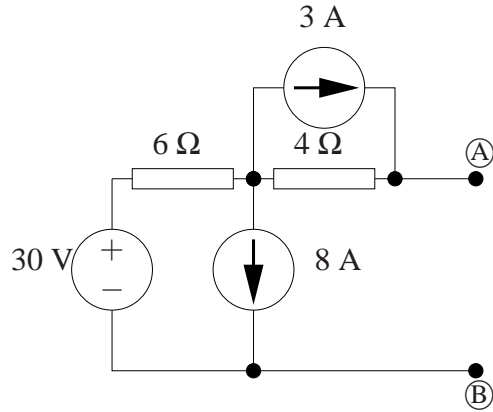


MAE 140 – Linear Circuits – Fall 2007
Midterm – Solution


Question 1 [Thevenin equivalent]

Regarding the following circuit:




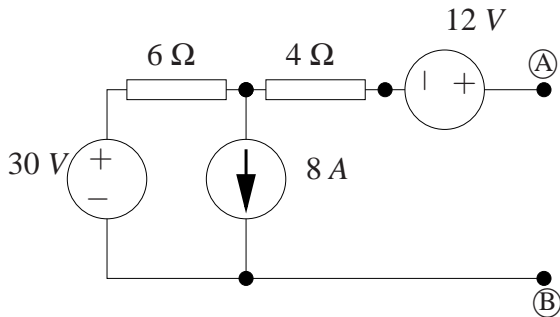- a) [4 marks] Determine the Thevenin equivalent as seen from terminals Ⓐ and Ⓑ using source transformations only.


Transform the 3 A current source in parallel with the 4 Ω resistor.



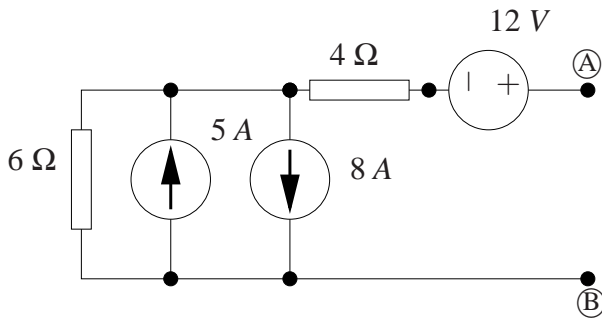
Transform the 30 V voltage source in series with the 6 Ω resistor.



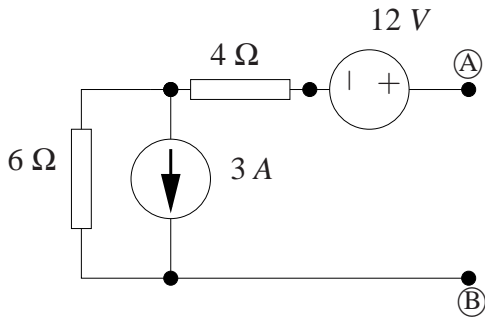
Combine the 5 A and the 8 A sources of current into a single 3 A source of current.



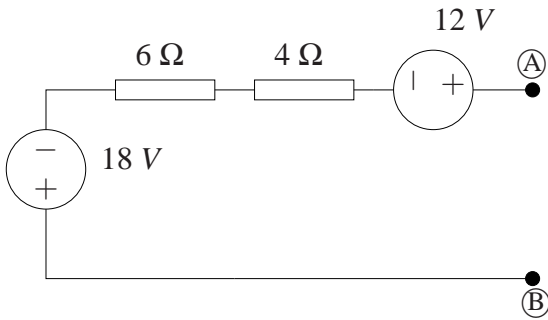Transform the 3 A current source in parallel with the 6 Ω resistor.



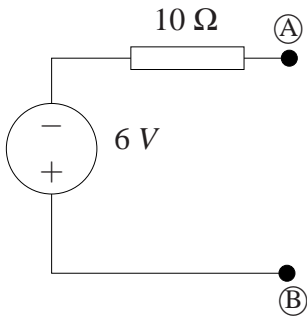
Combine the 12 V and the 18 V sources of voltage into a single 6 V source of voltage and associate the resistor to obtain the Thevenin equivalent circuit.



REMARK: You get 1 mark per correct transformation up to a max of 4 marks.

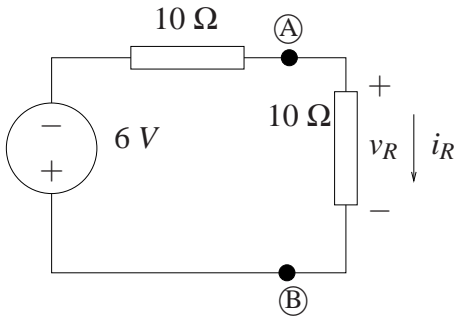- b) [2 marks] How much power would be absorbed by a $10\ \Omega$ resistor connected between terminals $\textcircled{\text{A}}$ and $\textcircled{\text{B}}$?

Plug the resistor in the Thevenin equivalent.




Use the voltage divider formula to conclude that

$$v_R = \frac{10}{10 + 10}(-6) = -3\ \text{V}, \quad i_R = \frac{v_R}{10} = -\frac{3}{10}\ \text{A}$$

so that the power absorbed by the resistor is $p_R = v_R i_R = 9/10\ \text{W}$.

Question 2 [Superposition / Mesh analysis]

Regarding the following circuit:

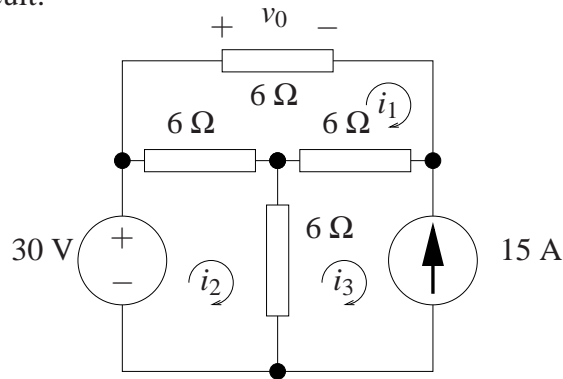


a) [4 marks] Find v_0 using superposition.

We will use superposition to compute

$$v_0 = v_1 + v_2$$

where v_1 is the solution when the current source is zero and v_2 is the solution when the voltage source is zero.

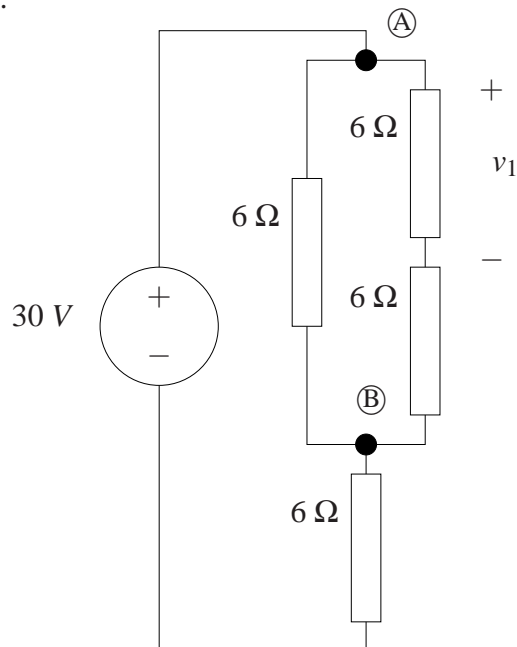First case: Zero the current source, that is, replace the current source by an open circuit, and redraw the circuit as follows.



Voltage v_1 can now be found using the voltage divider formula

$$v_1 = \frac{6}{6+6}(v_A - v_B) = \frac{1}{2}(v_A - v_B)$$


and

$$v_A - v_B = \frac{6 // (6 + 6)}{6 + [6 // (6 + 6)]} 30 = \frac{4}{6 + 4} 30 = 12 \text{ V}$$

where we used the fact that $6 // (6 + 6) = 6 \times 12 / (6 + 12) = 4$. That is

$$v_1 = \frac{1}{2}(v_A - v_B) = 6 \text{ V.}$$

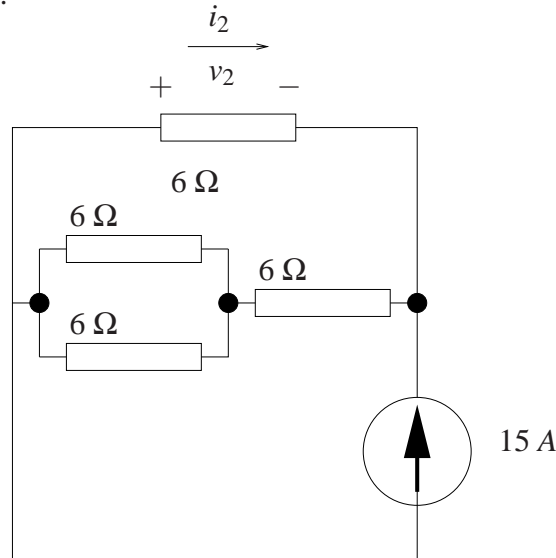Second case: Zero the voltage source, that is, replace the voltage source by a short circuit, and redraw the circuit as follows.



Voltage v_2 is

$$v_2 = 6 i_2$$

where can now be found using the current divider formula. Indeed

$$i_2 = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{6 + (6 // 6)}} (-15) \text{ A} = -\frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{9}} 15 \text{ A} = -\frac{3}{5} 15 \text{ A} = -9 \text{ A}$$

where we used the fact that $6 + (6 // 6) = 6 + 3 = 9$. That is

$$v_2 = 6 i_2 = -54 \text{ V.}$$

The final result is then

$$v_0 = v_1 + v_2 = 6 - 54 = -48 \text{ V.}$$

REMARK: Two marks per case: one for correct setup, another for correct answer.

- b) [4 marks] Formulate mesh-current equations for the circuit. Clearly indicate the equations to be solved and the unknowns. Use the mesh currents indicated in the drawing.

Because the 15 A source of current is on a single mesh we have

$$i_3 = -15 \text{ A.} \quad (1)$$

Writing the mesh-current equations by inspection for meshes 1 and 2 we have

$$\begin{bmatrix} 6+6+6 & -6 & -6 \\ -6 & 6+6 & -6 \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 30 \end{pmatrix}$$

Using (1) we obtain the final form of the mesh-current equations

$$\begin{bmatrix} 18 & -6 \\ -6 & 12 \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} -90 \\ -60 \end{pmatrix}, \quad i_3 = -15 \text{ A.}$$

REMARK: You get 1 mark if you stated eq. (1) correctly. 1 mark if you stated mesh-current equation for mesh 1 correctly. One more if mesh 2 is correct. One more mark if indicated the final equations to be solved, either by substituting i_3 or clearly indicating that meshes 1 and 2 must be solved in the presence of this constraint.

- c) [2 marks] Use the mesh-current equations to find v_0 .

First note that

$$v_0 = 6i_1. \quad (2)$$

Then determine i_1 by solving

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \frac{1}{6} \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}^{-1} \begin{pmatrix} -90 \\ -60 \end{pmatrix} = \frac{1}{30} \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix} \begin{pmatrix} -90 \\ -60 \end{pmatrix} = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix} \begin{pmatrix} -3 \\ -2 \end{pmatrix} = \begin{pmatrix} -8 \\ -9 \end{pmatrix}.$$


Hence

$$v_0 = 6i_1 = -48 \text{ V.}$$

REMARK: You get 1 mark if you stated eq. (2) correctly. 1 more mark if you solved for i_1 correctly.

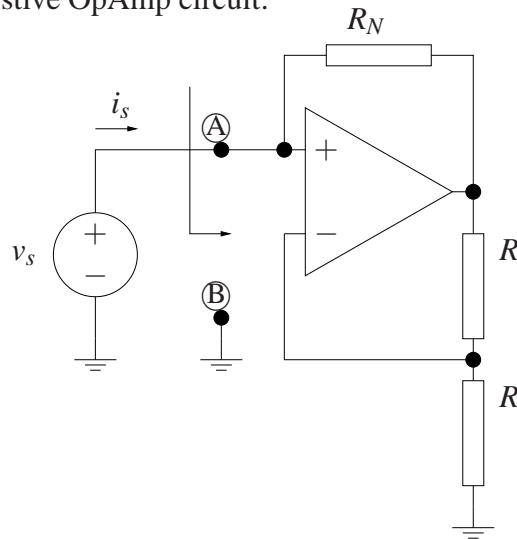
Question 3 [OpAmp Circuit Analysis]

Regarding the following resistive OpAmp circuit:



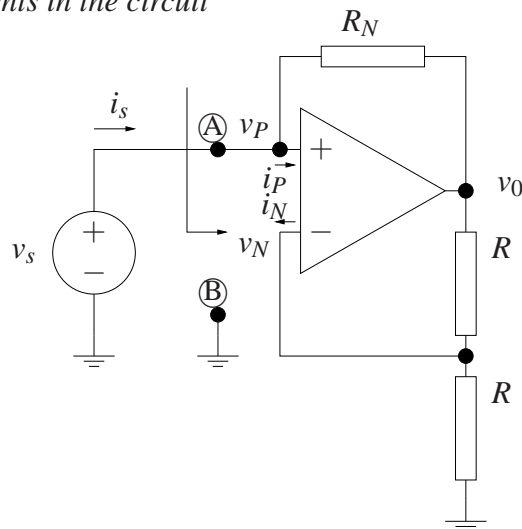a) [4 marks] Show that the current $i_s = -v_s/R_N$.

Label voltages and currents in the circuit



Because $i_N = 0$, the resistors R form a voltage divider

$$v_N = \frac{R}{R+R}v_0 = \frac{1}{2}v_0.$$

KCL at node (A) implies

$$i_s = i_P + \frac{(v_P - v_0)}{R_N}$$

These two equations combined with $v_P = v_N = v_s$ and $i_P = 0$, yield

$$i_s = \frac{(v_P - v_0)}{R_N} = \frac{(v_s - 2v_s)}{R_N} = -\frac{v_s}{R_N}$$

as desired.

REMARK: You get one mark for stating v_N correctly. One more for stating KCL @ node (A). One for using $v_P = v_N = v_S$, $i_P = i_n = 0$. One for getting the right answer.

- b) [2 marks] Draw the equivalent circuit as seen from terminals (A) and (B) in the direction indicated by the arrow. Explain why this circuit is called a “negative resistance”?


Hint: Recall that an equivalent circuit is one which has the same v - i characteristic.

From part a)

$$v_S = R_S i_S,$$

$$R_S = -R_N.$$

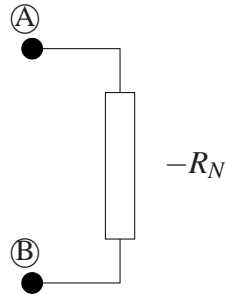
The above is Ohm's Law for a “negative resistance” R_N . Hence the name of the circuit. The equivalent is simply




Question 4 [OpAmp Circuit Analysis (bonus)]

[2 marks] Consider the connection of the “negative resistance” circuit of Question 3 in parallel with a load R_L as seen in the next circuit. What is the equivalent circuit as seen from terminals ③ and ④? Draw the circuit. What happens when $R_L = R_N$?

Hint: Make use of Question 3.

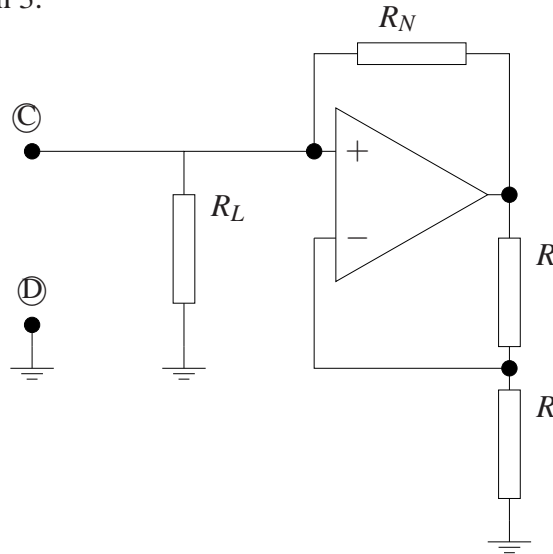

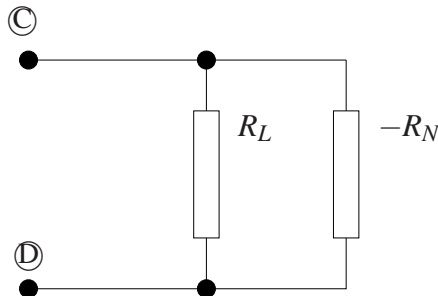Use the equivalent obtained in Question 3



from where an equivalent can be obtained after associating R_L and $-R_N$ in parallel

$$R_{EQ} = R_L // -R_N = \frac{1}{\frac{1}{R_L} - \frac{1}{R_N}} = \frac{R_L R_N}{R_N - R_L}$$

When $R_N \rightarrow R_L$ then $R_{EQ} \rightarrow \infty$, that is, the equivalent becomes an open circuit.

REMARK: One mark for R_{EQ} and one for the limit case.