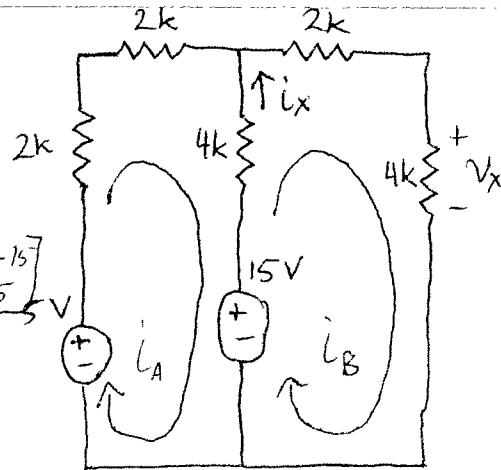


3.10

a) form mesh eqns

$$\begin{bmatrix} 2000 + 2000 + 4000 & -4000 \\ -4000 & 4000 + 2000 + 4000 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 5 - 15 \\ 15 \end{bmatrix}$$



b) find i_x & v_x

$$i_A = -0.625 \text{ mA}$$

$$i_B = 1.25 \text{ mA}$$


$$i_x = i_B - i_A = 1.875 \text{ mA}$$

$$v_x = i_B \cdot 4k\Omega = 5 \text{ V}$$

3.13

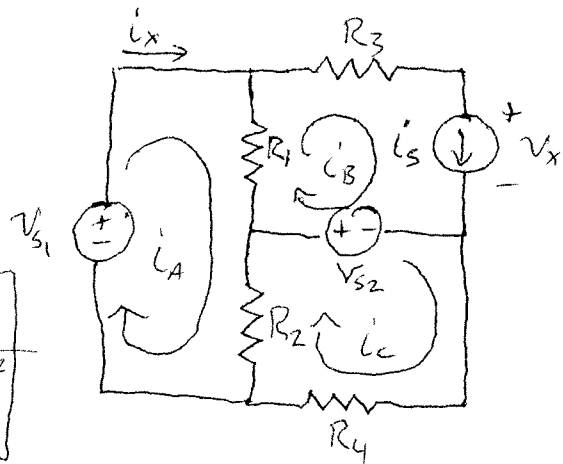a) form mesh eqns

$$\begin{bmatrix} R_1 + R_2 & -R_1 & -R_2 \\ -R_1 & R_1 + R_3 & 0 \\ -R_2 & 0 & R_2 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} v_{s1} \\ -v_x + v_{s2} \\ -v_{s2} \end{bmatrix}$$



$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_C \end{bmatrix} = \begin{bmatrix} v_{s1} + i_s R_1 \\ -v_{s2} \end{bmatrix}$$

b) solve for i_x & v_x when $R_1 = 10k\Omega$, $R_2 = 10k\Omega$, $R_3 = 2k\Omega$, $R_4 = 1k\Omega$, $v_{s1} = 12 \text{ V}$, $v_{s2} = 0.5 \text{ V}$, $i_s = 2.5 \text{ mA}$

$$i_A = 3.35 \text{ mA}$$

$$i_x = i_A = 3.35 \text{ mA}$$

$$i_B = 2.5 \text{ mA}$$

KVL for loop B

$$i_C = 3 \text{ mA}$$

$$-v_{s2} + v_{R1} + v_{R3} + v_x = 0$$

$$v_x = v_{s2} - (10k\Omega)(i_B - i_A) - (2k\Omega)i_B$$

$$v_x = 4 \text{ V}$$


c) find power supplied by v_{s1}

$$P = i_A \cdot (-v_{s1}) = -40.2 \text{ mW}$$

3.15

a) form mesh eqns.

$$i_A = 5 \text{ mA}$$

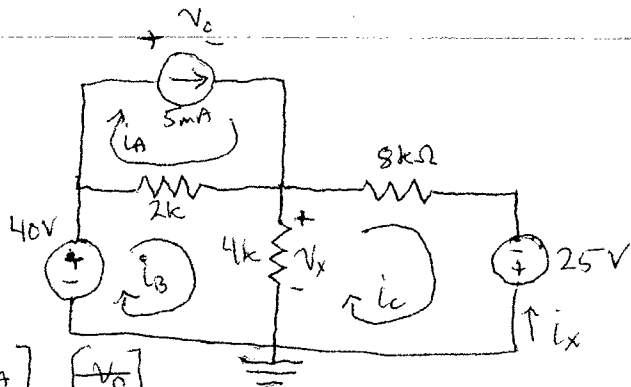

$$\begin{bmatrix} 2000 & -2000 & 0 \\ -2000 & 2000 + 4000 & -4000 \\ 0 & -4000 & 4000 + 2000 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 0 \\ 40 \\ 25 \end{bmatrix}$$

$$\begin{bmatrix} 6000 & -4000 \\ -4000 & 12000 \end{bmatrix} \begin{bmatrix} i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 40 + 2000 i_A \\ 25 \end{bmatrix}$$

b) solve for i_x & v_x

$$i_B = 12.5 \text{ mA}$$

$$i_C = 6.25 \text{ mA}$$

$$i_x = -i_C = \boxed{-6.25 \text{ mA}}$$

$$v_x = 4 \text{ k}\Omega (i_B - i_C) = \boxed{25 \text{ V}}$$

c) find the total power delivered to the resistors


$$P_R = (2 \text{ k}\Omega)(i_A - i_B)^2 + (4 \text{ k}\Omega)(i_B - i_C)^2 + (8 \text{ k}\Omega)(i_C)^2 = \boxed{581 \text{ mW}}$$

3.17 Find node voltages v_A & v_D , & mesh currents i_A & i_B

$$v_C = -2 \text{ V}$$

$$v_B = 0 \text{ V}$$
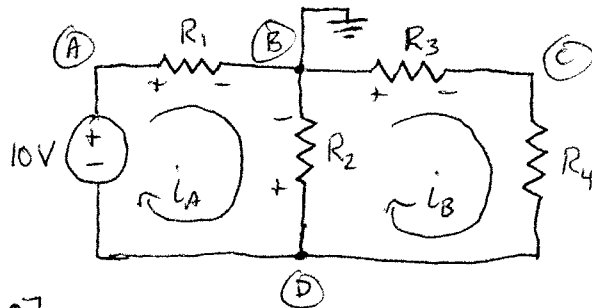
$$R_1 = R_2 = R_3 = R_4 = 1 \text{ k}\Omega$$



mesh eqns

$$\begin{bmatrix} 2000 & -1000 \\ -1000 & 3000 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$i_A = 6 \text{ mA}$$


$$i_B = 2 \text{ mA}$$

$$v_A = R_1 i_A = \boxed{6 \text{ V}}$$


$$v_D = R_2 (i_B - i_A) = \boxed{-4 \text{ V}}$$

$$\text{confirm } v_A - v_D = 10 \text{ V}$$

3.26 use superposition to find v_o

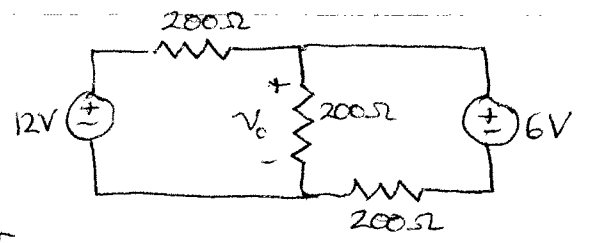


step 1

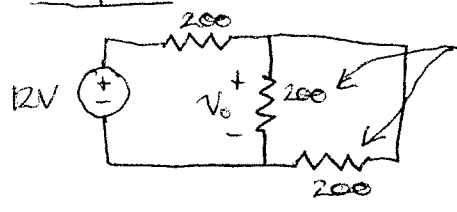

add in parallel voltage divider
 $v_o = \frac{100}{300} \cdot 12V = 4V$


step 2

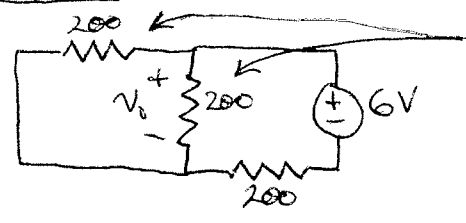


add in parallel voltage divider
 $v_o = \frac{100}{300} \cdot 6V = 2V$

total
 $v_o = 4V + 2V = \boxed{6V}$

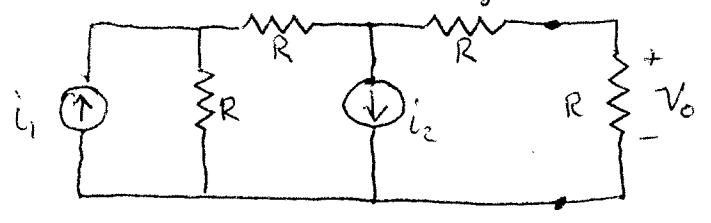3.31 use superposition to find v_o in terms of i_1, i_2 & R




step 1

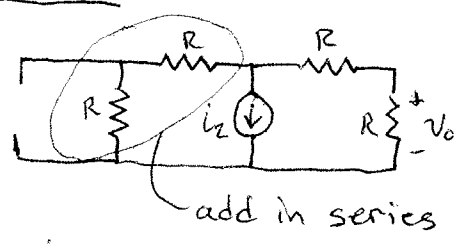


add in series

redraw

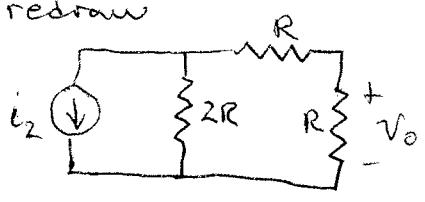

source transformation

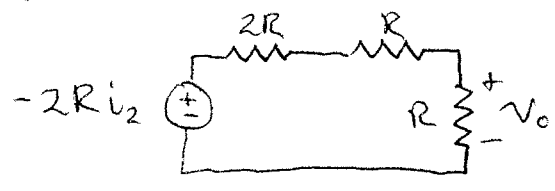


voltage divider


$$v_o = -\frac{R}{4R} \cdot (2Ri_2) = -\frac{Ri_2}{2}$$

3.31 continued

step 2

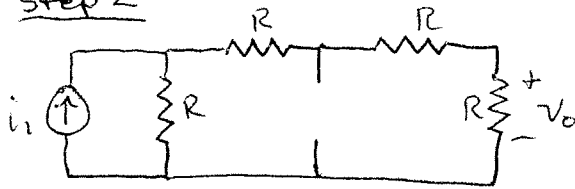

source transformation

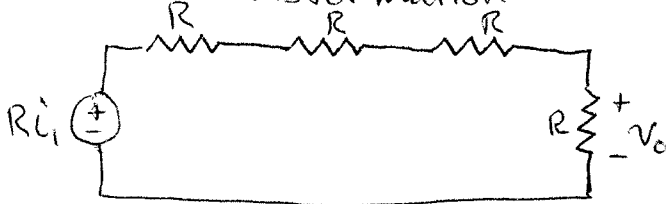

voltage divider

$$V_0 = \frac{R}{4R} \cdot i_1 R = \frac{i_1 R}{4}$$

total

$$V_0 = \frac{i_1 R}{4} - \frac{i_2 R}{2}$$

$$V_0 = \frac{R}{4} (i_1 - 2i_2)$$

3.32

Can't be sure without looking at the circuit as a whole.

The answer is not 4.25 W because the power is a product of linear terms, making it non-linear. Therefore superposition does not hold for power.

$$i_1 = \sqrt{(250 \text{ mW}) / (100 \Omega)} = 0.05 \text{ A}$$

$$i_2 = \sqrt{(4 \text{ W}) / (100 \Omega)} = 0.2 \text{ A}$$

If the currents flow in the same direction through the wire

$$P = (0.2 \text{ A} + 0.05 \text{ A})^2 (100 \Omega) = 6.25 \text{ W}$$


if they oppose one another

$$P = (0.2 \text{ A} - 0.05 \text{ A})^2 (100 \Omega) = 2.25 \text{ W}$$

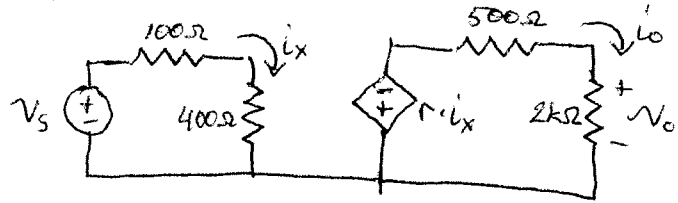4.1 find v_o/v_s & i_o/i_x for $r = 4k\Omega$

KVL

$$i_x = \frac{v_s}{100\Omega + 400\Omega}$$



$$i_o = - \frac{r \cdot i_x}{500\Omega + 2k\Omega} = - \frac{40}{25} i_x = - \frac{8}{5} i_x$$

voltage divider

$$v_o = - \frac{2000\Omega}{500\Omega + 2k\Omega} \cdot r i_x = - \frac{2000}{2500} \cdot \frac{4000}{500} v_s = - \frac{32}{5} v_s$$

$$\frac{v_o}{v_s} = - \frac{32}{5} = -6.4$$


$$\frac{i_o}{i_x} = - \frac{8}{5} = -1.6$$

4.5 find i_o/i_s

$$i_o = - \frac{50 v_x}{1000}$$

$$v_x = v_s - (-50 v_x)$$

$$v_x = - \frac{v_s}{49}$$

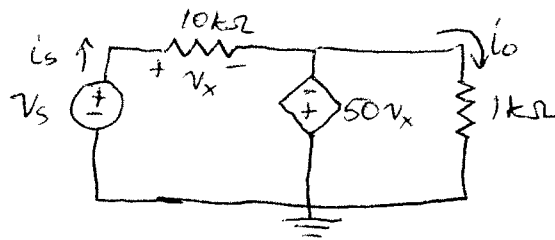

$$i_s = \frac{v_x}{10k\Omega} = - \frac{1}{49} \frac{v_s}{10k\Omega}$$

$$i_o = \frac{50}{1000} \frac{v_s}{49}$$

$$\frac{i_o}{i_s} = -500$$

4.6 find i_o/i_s

KCL


$$i_o = -\beta i_E$$

@A

$$i_E = \beta i_E + i_s$$

$$i_E = \frac{i_s}{(1-\beta)}$$

$$i_o = - \frac{\beta i_s}{(1-\beta)}$$

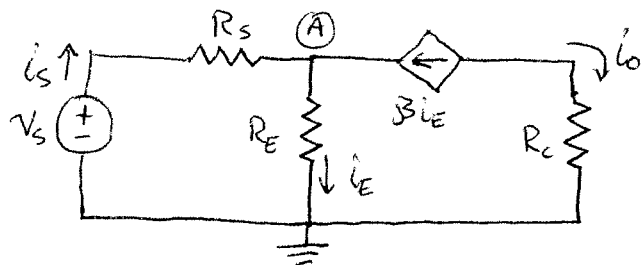

$$\frac{i_o}{i_s} = - \frac{\beta}{(1-\beta)}$$