
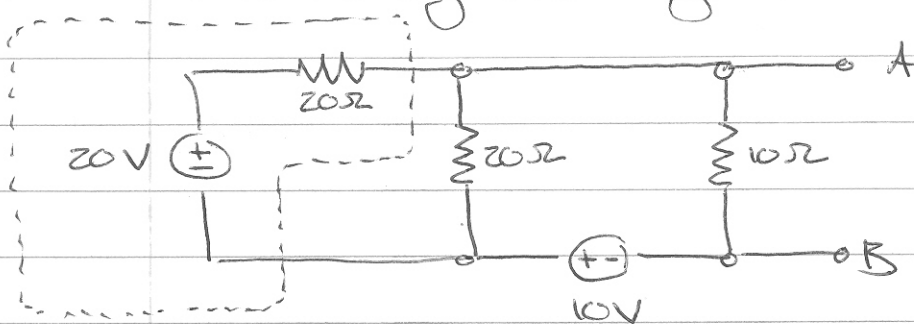


+1 point per step, no need to explicitly show each w/ proper results!

ii) Redrawing the original circuit:

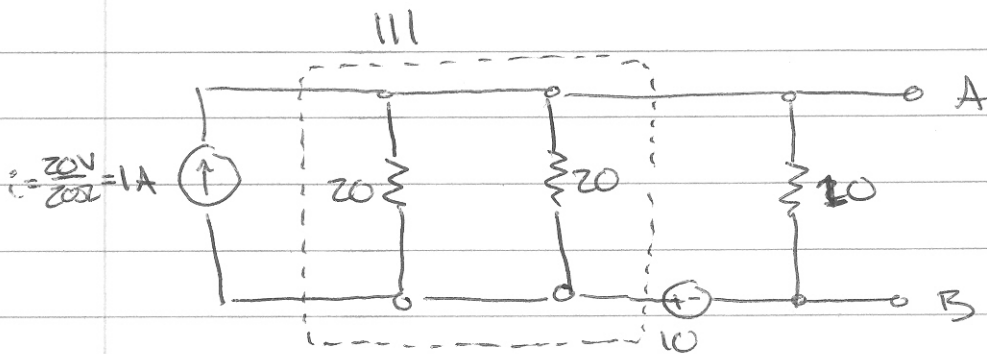


$V = 20V$





+1 (source transform)
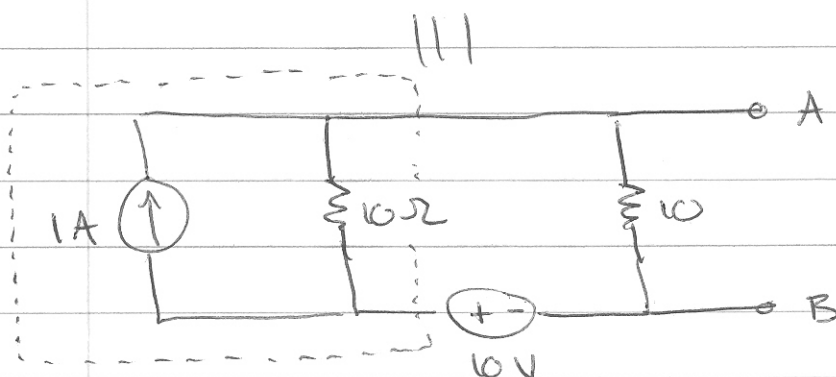
$$20\Omega \parallel 20\Omega = \frac{(20)(20)}{20+20} = \frac{400}{40} = 10\Omega$$





+1 (combining R's)

1 cont.)

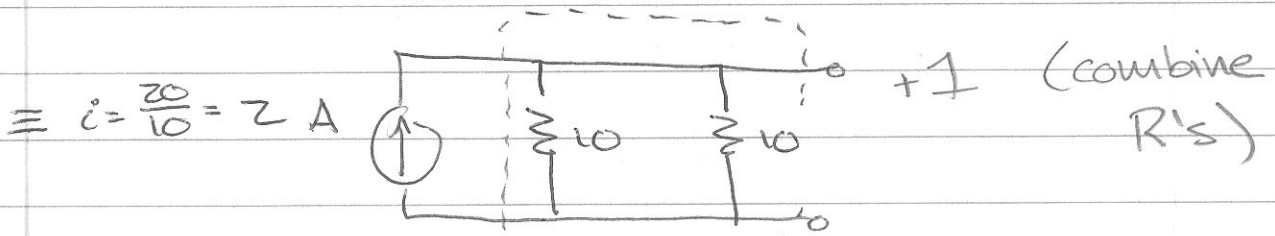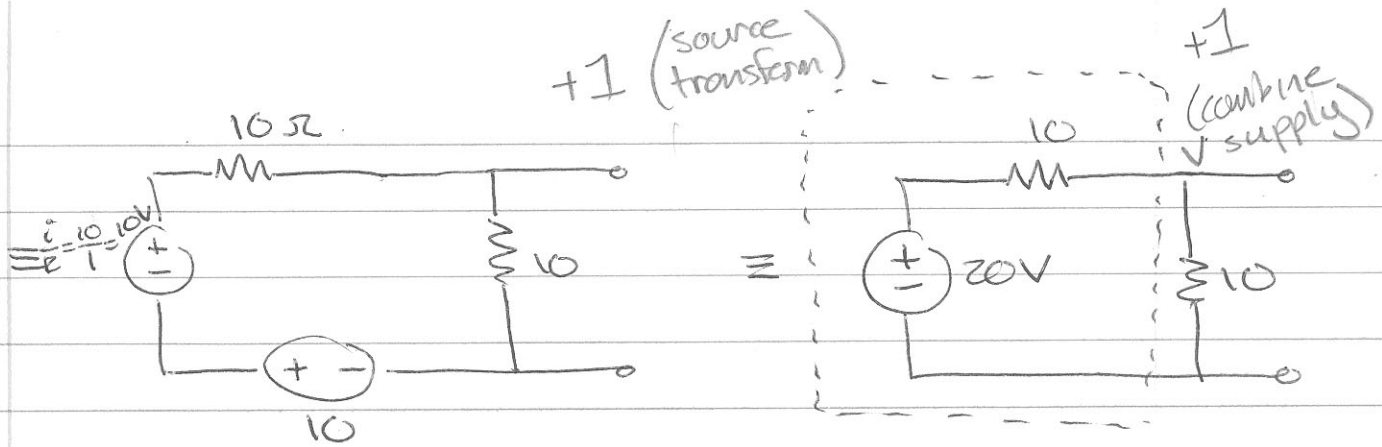

$$i = \frac{20}{10} = 2 \text{ A}$$
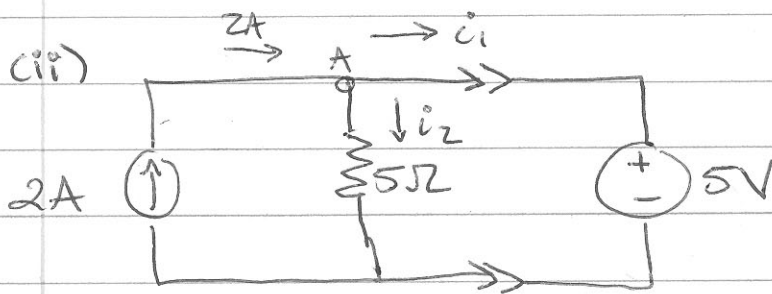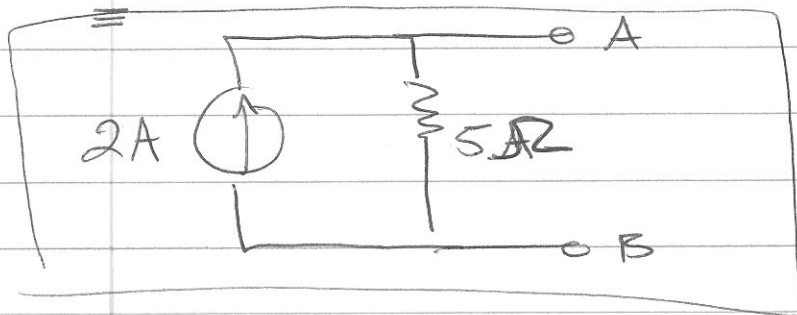
$$10 \parallel 10 = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = 5$$




KCL @ A:  $2\text{A} = i_1 + i_2$

$$i_2 = \frac{5}{5} = 1\text{A} \Rightarrow 2\text{A} = 1\text{A} + i_2 \Rightarrow i_2 = 1\text{A}$$

$$P = iV \Rightarrow P = (1\text{A})(5\text{V}) = \boxed{5\text{W}} +1$$

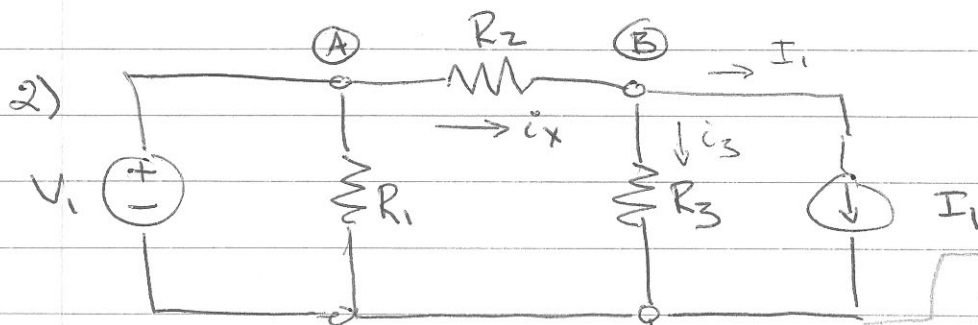P is (+)  $\Rightarrow$  the voltage supply absorbs power +1



Need to give each equation for the nodes (A)

then supply an explanation (+2)

(not necessarily an eq.) to get  $V_B$ .

(i)

$$V_A - 0 = V_1 \Rightarrow V_A = V_1 \quad +1$$

$$i_x - i_z - I_1 = 0, \quad i_x = \frac{V_A - V_B}{R_2}, \quad i_z = \frac{0 - V_B}{R_3}$$

$$\Rightarrow \frac{V_A - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \quad +1$$

(subbing in  $V_A = V_1$ )


$$\Rightarrow \left[ \frac{V_1 - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \right] \text{ and we solve this for } V_B \quad +2$$

(ii) as noted  $i_x = \frac{V_A - V_B}{R_2} \Rightarrow i_x = \frac{V_1 - V_B}{R_2}$

$$\therefore \frac{V_1 - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \Rightarrow i_x - \frac{V_B}{R_3} - I_1 = 0$$

$$\Rightarrow \left[ i_x = I_1 + \frac{V_B}{R_3} \right] \quad \& V_B \text{ found above!}$$

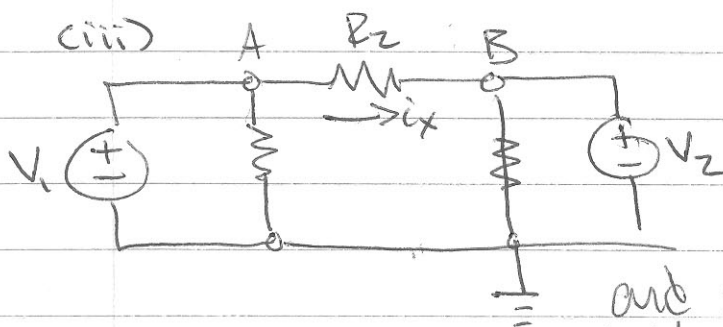Any approp. eq. for  $i_x$  w/ respect to work in (i)   
 +2




$$V_B = V_2 \quad +1$$

$\Rightarrow$  we no longer need (i)

and simply solve Ohm's law
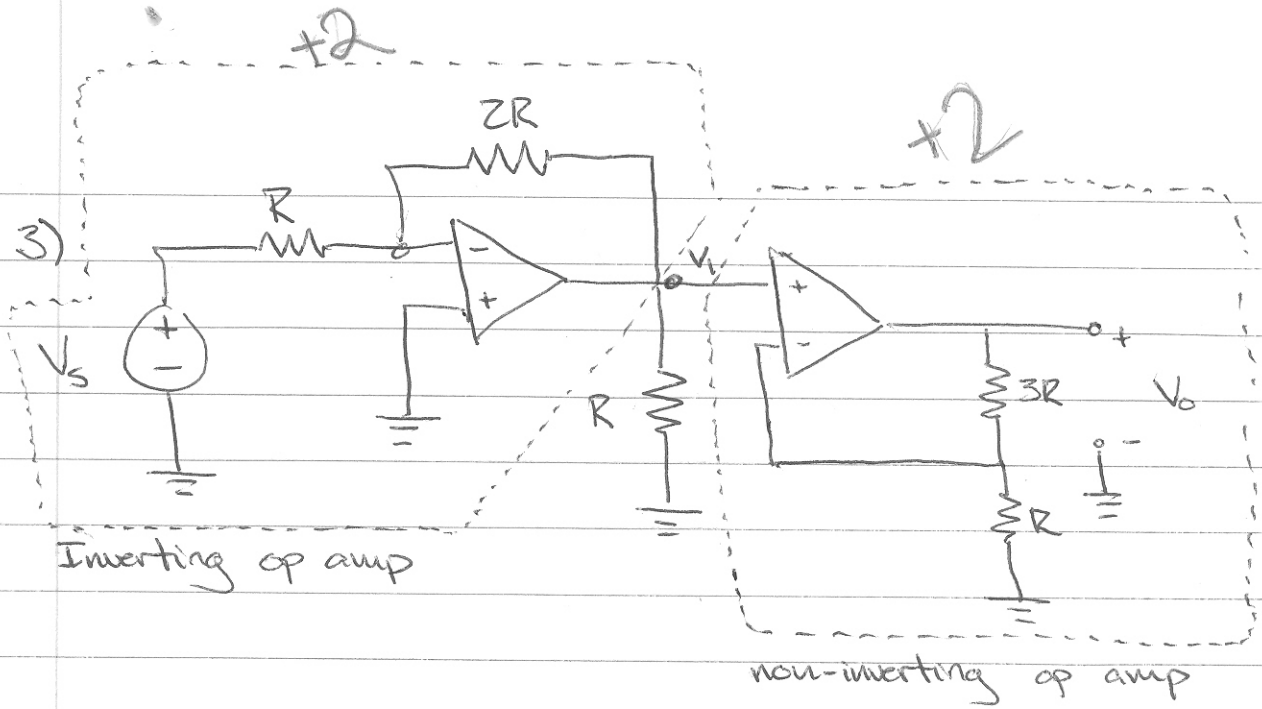
$$\frac{V_A - V_B}{R_2} = i_x = \frac{V_1 - V_2}{R_2} \quad +1$$



cii) inverting op amp:  $+2$


$$\frac{V_1}{V_s} = -\left(\frac{2R}{R}\right) \Rightarrow \cancel{V_1} = \cancel{-R} V_s \quad (\text{this is the input voltage to the next block!})$$

$$V_1 = -2V_s$$

non-inverting op amp:  $+2$

$$\frac{V_0}{V_1} = \frac{(3R+R)}{R} \Rightarrow V_0 = 4V_1$$
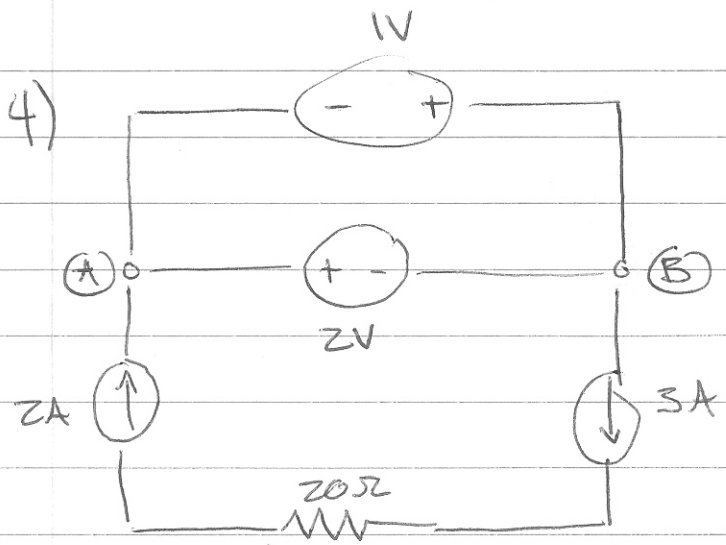
$$\therefore V_0 = 4(-2)V_s = \boxed{-8V_s = V_0}$$



if note this only +1

(Nodes A & B are both at 2V and 1V simultaneously!) +7

∴ KVL is violated! +1/+2 (if note this only +2)

(The resistor loop connecting A & B is at 3A and 2A at the same time.) +1

∴ KCL is violated! +1/+2

(if this only) +2

if this only +7