



**MAE 140 – Linear Circuits – Summer 2007**  
**Final**

**Instructions**

- 1) This exam is open book. You may use whatever written materials you choose, including your class notes and textbook. You may use a hand calculator with no communication capabilities.
- 2) You have 170 minutes.
- 3) On the questions for which I have given the answers, please provide detailed derivations.

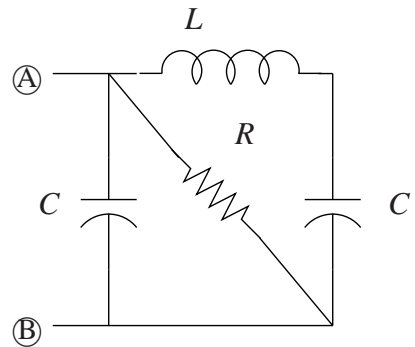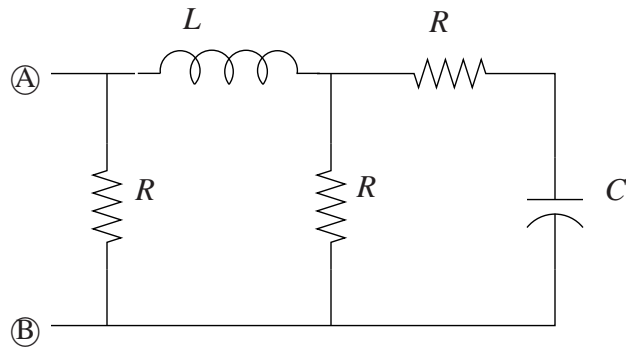
**Question 1 [Equivalent Circuits]**

[4 marks] Find the equivalent impedance between terminals **(A)** and **(B)** in the following circuits.



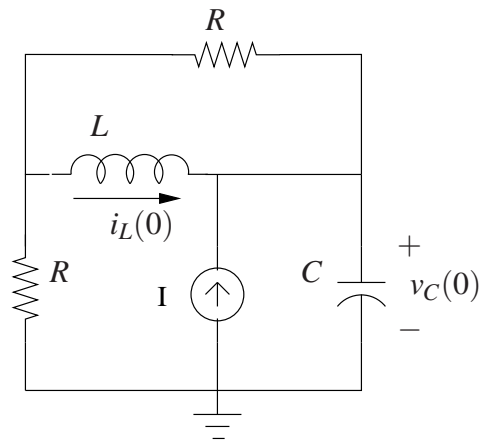
**Question 2 [Nodal Analysis in the s-Domain]**

[6 marks] Transform the following circuit to the s-domain and formulate node-voltage equations. Assume initial conditions and reference ground as indicated in the figure. The current source is constant.



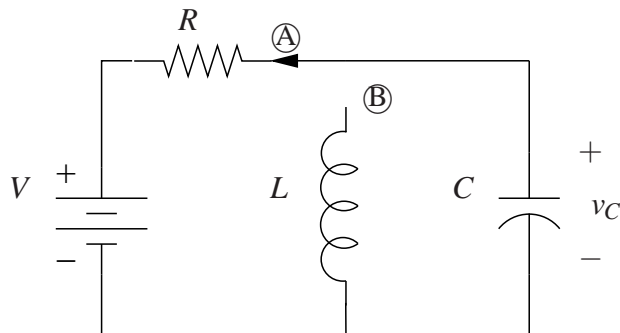
**Question 3 [Transient Analysis in the s-Domain]**

[6 marks] The switch in the next circuit has been left in position **(A)** for a long time and is moved to position **(B)** at  $t = 0$ . Find  $v_c(t)$  for  $t \geq 0$ . The voltage source is constant.




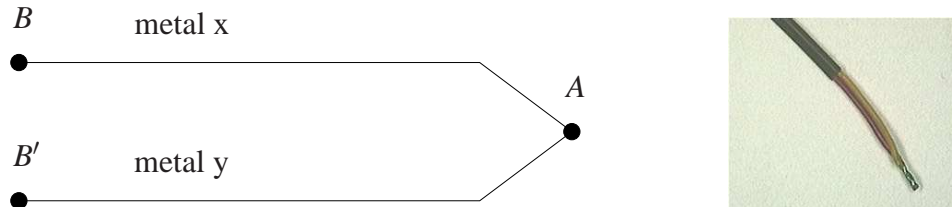**Question 4 [Circuit Variables and OpAmp Circuit Design]**

When two *different* metal wires are placed in contact (creating a junction) a voltage appears that is proportional to the junction temperature and the material properties. A pair of wires made with different materials connected at one end as in the next figure is known as a *thermocouple*, and is a very popular temperature sensor. No voltage appears on junctions made of same materials because of temperature. The points  $B$  and  $B'$  are at the same temperature  $T_B$ .




A good model for the thermocouple junction is as a voltage source with voltage  $v = \bar{K} + KT$ , where  $\bar{K}$  and  $K$  are constants that depend only on the material used in the junction and  $T$  is the junction temperature. A simple circuit model for the above thermocouple is given in the next diagram, where  $R_x$  and  $R_y$  represent the resistance of the wires, which are essentially functions of the cross section area and length of the thermocouple. It is fair to assume that  $R_x \approx R_y$ .

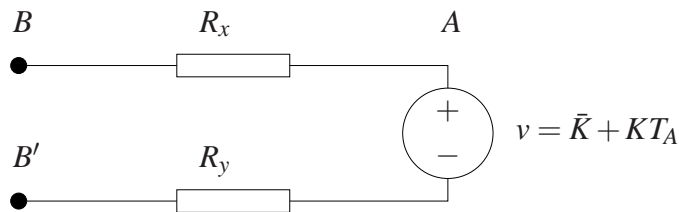

A thermocouple made with 'metal x' being copper and 'metal y' being constantan can measure temperatures in the range  $-200\text{ }^\circ\text{C}$  to  $350\text{ }^\circ\text{C}$  with  $K = 43\mu\text{ V}/^\circ\text{C}$ . The voltage  $v$  is measured from the copper terminal (+) to the constantan terminal (-). As you will see soon, the value of  $\bar{K}$  is not important.

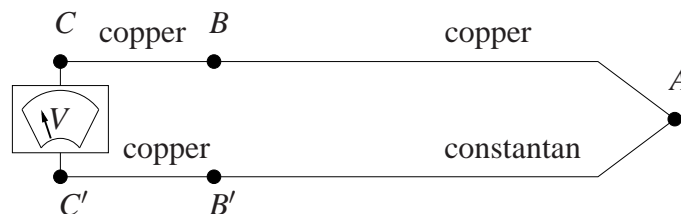- a) [3 marks] A friend of yours suggested that you can measure the temperature of point  $A$  ( $T_A$ ) by simply connecting a voltmeter with copper leads to the points  $B$  and  $B'$  and measure the resulting voltage in  $C$  and  $C'$  (internal to the voltmeter), as in the next figure. The points  $B$  and  $B'$  are at the same temperature  $T_B$ . The points  $C$  and  $C'$  are at the same temperature  $T_C$ . Draw the circuit diagram corresponding to this setup and show that he/she is not correct: this setup can only measure  $V_C - V_{C'} = K(T_A - T_B)$ .

(Hint: remember that a voltage appear on all junctions made with different materials!)



One way of overcoming the above problem is to let the temperature  $T_B$  be known. A popular approach is to have the junction  $B'$  be immersed in a bath of water and ice, in which the temperature

is exactly  $0.01\text{ }^{\circ}\text{C}$  (known as the triple point of water) so that  $T_A = T_B + (V_C - V_{C'})/K \approx (V_C - V_{C'})/K$ .

- b) [4 marks] Assume that  $T_B$  is in a cold bath at the triple point of water (assume  $T_B \approx 0$ ) and design an OpAmp circuit to be connected at  $C-C'$  that outputs a voltage  $v_0 = \alpha T_A$ , where  $\alpha = 10\text{ mV}/^{\circ}\text{C}$ . Note that this circuit should make the measurement independent of the wire resistance. If the OpAmp is powered with  $+10\text{V}$  and  $-10\text{V}$  what is the temperature range that you can measure accurately with your circuit?


Another way of overcoming the temperature reference problem is to directly measure the temperature  $T_B$ . The justification for this is that  $T_B$  is the temperature of a controlled environment, say your workbench, while  $T_A$  may be an extreme temperature you're trying to measure. Therefore, you could use a temperature sensor to measure  $T_B$  that is less expensive or perhaps accurate only on ambient temperature. One such device is called a *termistor*, which is a resistor whose resistance varies with the temperature. Termistors are typically accurate and approximately linear from  $0\text{ }^{\circ}\text{C}$  to a dozen degrees above ambient temperature.

- c) [2 marks] You have a linear termistor with a resistance of  $30\text{K}\Omega$  at  $0\text{ }^{\circ}\text{C}$  and a resistance of  $10\text{K}\Omega$  at  $20\text{ }^{\circ}\text{C}$ . Show that the relationship between the termistor resistance ( $R_T$ ) and the termistor temperature ( $T_B$ ) is

$$R_T = (30 - T_B) \times 10^3 \Omega.$$

Up to what temperature do you think this termistor is accurate (or at least linear)? Why?

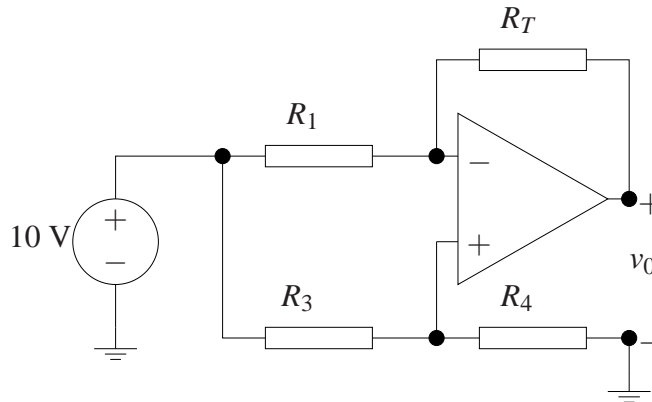- d) [Bonus: 4 marks] Using the above relationship between the termistor resistance and temperature find values for the components  $R_1$ ,  $R_3$  and  $R_4$  so that the following circuit produces  $v_0 = \alpha T_B$ , where  $\alpha = 10\text{ mV}/^{\circ}\text{C}$  and  $T_B$  is the temperature of the termistor and the junction  $B'$ .



- e) [Bonus: 4 marks] Design an OpAmp circuit that has as output voltage  $v_0 = \alpha(T_A - T_B)$ , where  $\alpha = 10\text{ mV}/^{\circ}\text{C}$  and  $T_B$  is measured using the termistor as in item d). (Hint: use the circuit you designed in item d)!