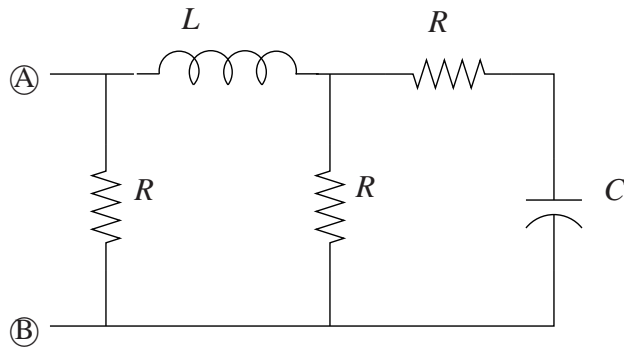


**MAE 140 – Linear Circuits – Summer 2007**  
**Final Solution**

**NOTE: The items d) and e) of Question 4 gave you bonus marks.**

**Question 1 [Equivalent Circuits]**

[4 marks] Find the equivalent impedance between terminals **(A)** and **(B)** in the following circuits.



$$Z(s) = R // [sL + R // (R + 1/sC)]$$

*Let's compute one term at a time. First*


$$R // (R + 1/sC) = \frac{R(R + 1/sC)}{R + (R + 1/sC)} = \frac{R(sRC + 1)}{sRC + (sRC + 1)},$$

*followed by*

$$sL + R // (R + 1/sC) = sL + \frac{R(sRC + 1)}{sRC + (sRC + 1)} = \frac{s^2RLC + (sL + R)(sRC + 1)}{sRC + (sRC + 1)}.$$

*Finally*
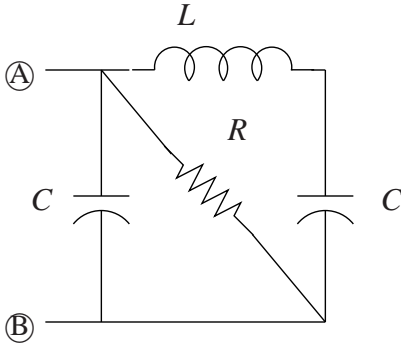
$$\begin{aligned} Z(s) &= R // [sL + R // (R + 1/sC)] \\ &= \frac{\frac{s^2R^2LC + R(sL + R)(sRC + 1)}{sRC + (sRC + 1)}}{R + \frac{s^2RLC + (sL + R)(sRC + 1)}{sRC + (sRC + 1)}} = \frac{s^2R^2LC + R(sL + R)(sRC + 1)}{sRC(sL + R) + (sL + 2R)(sRC + 1)}. \end{aligned}$$



$$Z(s) = 1/sC // R // (sL + 1/sC)$$


*so all there is to do is to compute the parallel association*

$$Z(s) = \frac{1}{sC + \frac{1}{R} + \frac{sC}{s^2LC + 1}} = \frac{R(s^2LC + 1)}{sCR + (sCR + 1)(s^2LC + 1)}$$



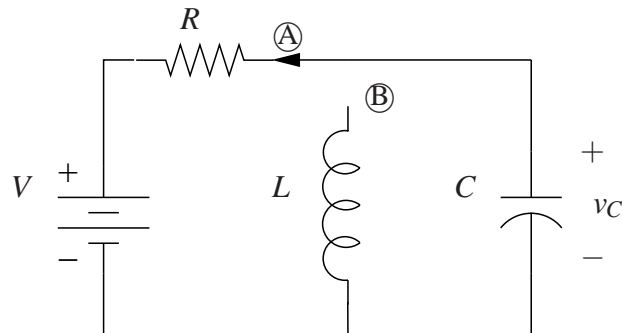
**Question 3 [Transient Analysis in the s-Domain]**

[6 marks] The switch in the next circuit has been left in position **(A)** for a long time and is moved to position **(B)** at  $t = 0$ . Find  $v_c(t)$  for  $t \geq 0$ . The voltage source is constant.



The first step is to determine  $v_c(0)$ . This is obtained by noticing that if the switch is on **(A)** for a long time then the current in  $C$ , and consequently in  $R$ , should be zero, therefore,  $v_c(0) = V$ .

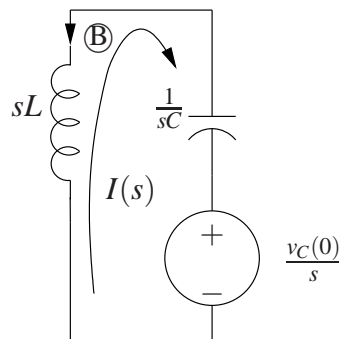Now transform the circuit after the switch is moved to **(B)** to the  $s$ -domain as in the following diagram.



Mesh analysis applied to the diagram provides

$$(sL + 1/sC)I(s) = -\frac{v_c(0)}{s} \quad \Rightarrow \quad I(s) = -\frac{v_c(0)}{s(sL + 1/sC)} = -\frac{CV}{s^2LC + 1}$$

Noticing that


$$v_c(s) = \frac{v_c(0)}{s} + \frac{1}{sC}I(s) = \left(1 - \frac{1}{s^2LC + 1}\right) \frac{V}{s} = \frac{sLC}{s^2LC + 1} V = \frac{s}{s^2 + 1/LC} V$$

Therefore, applying the Laplace inverse we have


$$v_c(t) = V \mathcal{L}^{-1} \left\{ \frac{s}{s^2 + 1/LC} \right\} = V \cos(\omega t) u(t), \quad \omega := \sqrt{\frac{1}{LC}}.$$

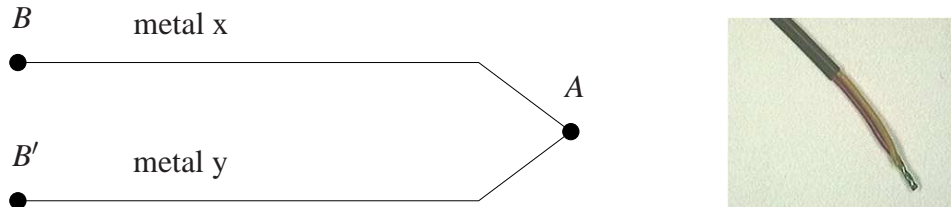**Question 4 [Circuit Variables and OpAmp Circuit Design]**

When two *different* metal wires are placed in contact (creating a junction) a voltage appears that is proportional to the junction temperature and the material properties. A pair of wires made with different materials connected at one end as in the next figure is known as a *thermocouple*, and is a very popular temperature sensor. No voltage appears on junctions made of same materials because of temperature. The points  $B$  and  $B'$  are at the same temperature  $T_B$ .




A good model for the thermocouple junction is as a voltage source with voltage  $v = \bar{K} + KT$ , where  $\bar{K}$  and  $K$  are constants that depend only on the material used in the junction and  $T$  is the junction temperature. A simple circuit model for the above thermocouple is given in the next diagram, where  $R_x$  and  $R_y$  represent the resistance of the wires, which are essentially functions of the cross section area and length of the thermocouple. It is fair to assume that  $R_x \approx R_y$ .

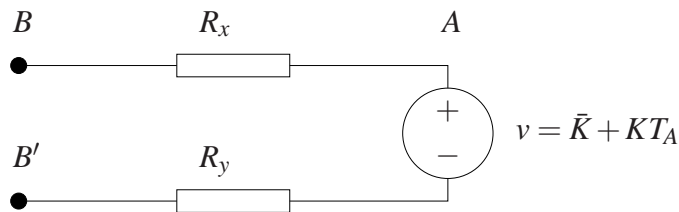


A thermocouple made with 'metal x' being copper and 'metal y' being constantan can measure temperatures in the range  $-200\text{ }^\circ\text{C}$  to  $350\text{ }^\circ\text{C}$  with  $K = 43\mu\text{ V}/^\circ\text{C}$ . The voltage  $v$  is measured from the copper terminal (+) to the constantan terminal (-). As you will see soon, the value of  $\bar{K}$  is not important.

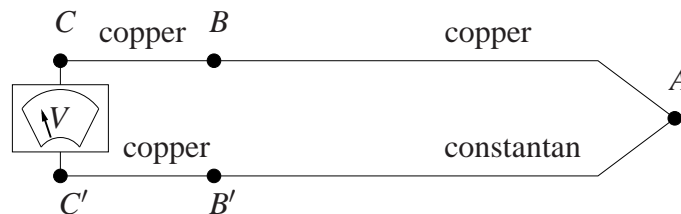- a) [3 marks] A friend of yours suggested that you can measure the temperature of point  $A$  ( $T_A$ ) by simply connecting a voltmeter with copper leads to the points  $B$  and  $B'$  and measure the resulting voltage in  $C$  and  $C'$  (internal to the voltmeter), as in the next figure. The points  $B$  and  $B'$  are at the same temperature  $T_B$ . The points  $C$  and  $C'$  are at the same temperature  $T_C$ . Draw the circuit diagram corresponding to this setup and show that he/she is not correct: this setup can only measure  $V_C - V_{C'} = K(T_A - T_B)$ .

(Hint: remember that a voltage appear on all junctions made with different materials!)



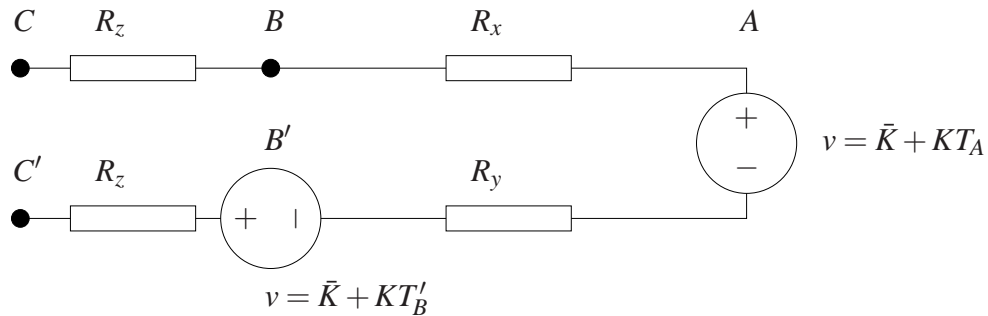Because the junction  $B'$  has two different metals the circuit diagram of the above setup is as follows:



Because no current flows into the voltmeter, then

$$V_C - V'_C = (\bar{K} + KT_A) - (\bar{K} + KT'_B) = K(T_A - T'_B) = K(T_A - T_B)$$

as stated.

One way of overcoming the above problem is to let the temperature  $T_B$  be known. A popular approach is to have the junction  $B'$  be immersed in a bath of water and ice, in which the temperature is exactly  $0.01^\circ\text{C}$  (known as the triple point of water) so that  $T_A = T_B + (V_C - V'_C)/K \approx (V_C - V'_C)/K$ .

- b) [4 marks] Assume that  $T_B$  is in a cold bath at the triple point of water (assume  $T_B \approx 0$ ) and design an OpAmp circuit to be connected at  $C$ - $C'$  that outputs a voltage  $v_0 = \alpha T_A$ , where  $\alpha = 10 \text{ m V}/^\circ\text{C}$ . Note that this circuit should make the measurement independent of the wire resistance. If the OpAmp is powered with  $+10\text{V}$  and  $-10\text{V}$  what is the temperature range that you can measure accurately with your circuit?


Because  $T_A \approx (V_C - V'_C)/K$  our circuit have to implement the function

$$\begin{aligned} v_0 &= \alpha T_A \\ &\approx (\alpha/K)(V_C - V'_C) \end{aligned}$$

with gain

$$\frac{\alpha}{K} = \frac{10 \times 10^{-3} \text{ V}/^\circ\text{C}}{43 \times 10^{-6} \text{ V}/^\circ\text{C}} = \frac{10}{43} \times 10^3 \approx 232.$$

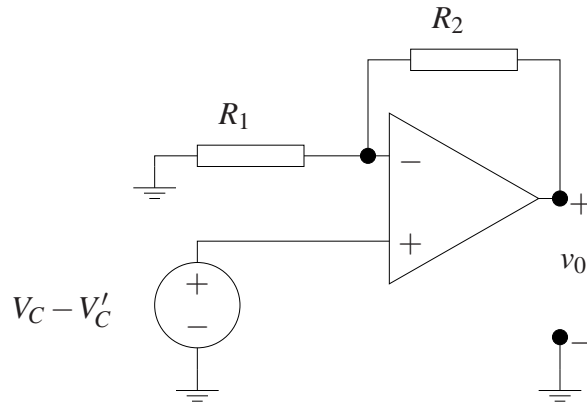One possible answer is to use a non-inverting amplifier setup



with gain

$$\frac{R_2 + R_1}{R_1} = 1 + \frac{R_2}{R_1} = 232.$$

This configuration has a high input impedance so the effect of the ohmic wire resistances is minimized. Possible (unrealistic) choices for  $R_1$  and  $R_2$  that could be used are

$$R_1 = 1K\Omega,$$

$$R_2 = 231K\Omega.$$

We should be able to read temperatures while the OpAmp stays in the linear range. So we look for the saturation points:

$$10 \times 10^{-3} T_{\text{low}} = -10 \quad \Rightarrow \quad T_{\text{low}} = -1000^\circ\text{C},$$

$$10 \times 10^{-3} T_{\text{high}} = 10 \quad \Rightarrow \quad T_{\text{high}} = +1000^\circ\text{C}.$$

As the thermocouple is accurate in the range  $[-200, 350]^\circ\text{C}$  we should be able to read accurately the entire scale of the thermocouple. Indeed, we could have used a higher gain to enhance the circuit resolution, perhaps using two stages of amplification.

Another way of overcoming the temperature reference problem is to directly measure the temperature  $T_B$ . The justification for this is that  $T_B$  is the temperature of a controlled environment, say your workbench, while  $T_A$  may be an extreme temperature you're trying to measure. Therefore, you could use a temperature sensor to measure  $T_B$  that is less expensive or perhaps accurate only on ambient temperature. One such device is called a *termistor*, which is a resistor whose resistance varies with the temperature. Termistors are typically accurate and approximately linear from  $0^\circ\text{C}$  to a dozen degrees above ambient temperature.

- c) [2 marks] You have a linear termistor with a resistance of  $30K\Omega$  at  $0^\circ\text{C}$  and a resistance of  $10K\Omega$  at  $20^\circ\text{C}$ . Show that the relationship between the termistor resistance ( $R_T$ ) and the termistor temperature ( $T_B$ ) is

$$R_T = (30 - T_B) \times 10^3 \Omega.$$

Up to what temperature do you think this termistor is accurate (or at least linear)? Why?

Because the termistor is linear it should satisfy

$$R_T = aT_B + b$$

for some  $a$  and  $b$ . Evaluating  $R_T$  at  $T_B = 0^\circ\text{C}$  and  $T_B = 20^\circ\text{C}$  yields

$$a \times 0 + b = b = 30 \times 10^3 \Omega, \quad a \times 20 + b = 10 \times 10^3 \Omega$$

from where

$$b = 30 \times 10^3$$

$$a = (10 \times 10^3 - b)/20 = (10 \times 10^3 - 30 \times 10^3)/20 = -1 \times 10^3 \Omega/^\circ\text{C}.$$

Hence


$$R_T = (30 - T_B) \times 10^3 \Omega.$$

You should start being suspicious about this termistor model when it reaches temperatures for which  $R_T$  becomes near zero, that is, near

$$(30 - T_B) \times 10^3 = 0 \quad \Rightarrow \quad T_B = 30^\circ\text{C}.$$

You should then worry about using it in a hot day or improve your linear assumption :).

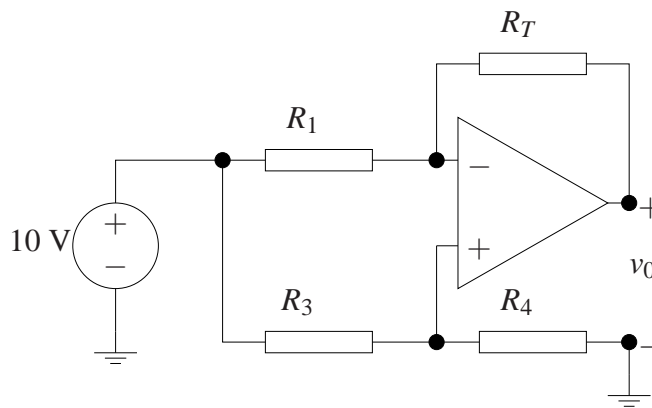- d) [Bonus: 4 marks] Using the above relationship between the termistor resistance and temperature find values for the components  $R_1$ ,  $R_3$  and  $R_4$  so that the following circuit produces  $v_0 = \alpha T_B$ , where  $\alpha = 10 \text{ mV}/^\circ\text{C}$  and  $T_B$  is the temperature of the termistor and the junction  $B'$ .



First recognize that the above circuit is a differential amplifier where

$$v_0 = K_1 v_1 + K_2 v_2, \quad K_1 = -\frac{R_T}{R_1}, \quad K_2 = \frac{R_T + R_1}{R_1} \frac{R_4}{R_3 + R_4} = \left(1 + \frac{R_T}{R_1}\right) \frac{R_4}{R_3 + R_4}$$



and  $v_1 = v_2 = 10V$ . Using this fact

$$\begin{aligned} v_0 &= 10(K_1 + K_2) \\ &= 10 \left( \frac{R_1 + R_T}{R_1} \frac{R_4}{R_3 + R_4} - \frac{R_T}{R_1} \right) \\ &= \frac{10}{R_1} \left( \frac{R_4(R_1 + R_T)}{R_3 + R_4} - R_T \right) \\ &= \frac{10}{R_1(R_3 + R_4)} (R_1R_4 - R_3R_T) \end{aligned}$$

Now substitute for  $R_T = R_0 - \beta T_B$ , where  $R_0 = 30 \times 10^3 \Omega$  and  $\beta = 10^3$

$$\begin{aligned} v_0 &= \frac{10}{R_1(R_3 + R_4)} (R_1R_4 - R_3R_0 + \beta R_3T_B) \\ &= \frac{10}{R_1(R_3 + R_4)} (R_1R_4 - R_3R_0) + \frac{10\beta R_3}{R_1(R_3 + R_4)} T_B. \end{aligned}$$

For  $v_0 = \alpha T_B$  we need to chose

$$\frac{R_3}{R_4} = \frac{R_1}{R_0}, \quad \frac{10\beta R_3}{R_1(R_3 + R_4)} = \frac{10\beta}{R_1 \left(1 + \frac{R_4}{R_3}\right)} = \alpha$$

This fixes the choice of  $R_1$  since

$$R_1 = 10\beta\alpha^{-1} - R_0 = 10 \times 10^3 \times 10^2 - 30 \times 10^3 = (1000 - 30)K\Omega = 970K\Omega$$

Possible choices of  $R_3$  and  $R_4$  are

$$R_3 = R_1 = 970K\Omega, \quad R_4 = R_0 = 30K\Omega, \quad \frac{R_3}{R_4} = \frac{R_1}{R_0} = \frac{970 \times 10^3}{30 \times 10^3} \approx 32$$

- e) [Bonus: 4 marks] Design an OpAmp circuit that has as output voltage  $v_0 = \alpha(T_A - T_B)$ , where  $\alpha = 10 \text{ mV}/^\circ\text{C}$  and  $T_B$  is measured using the termistor as in item d). (Hint: use the circuit you designed in item d)!

The simplest solution is to reuse the circuits developed in items b) and d) through a differential amplifier configuration with

$$v_0 = K_1v_1 + K_2v_2, \quad K_1 = -\frac{R_2}{R_1}, \quad K_2 = \frac{R_2 + R_1}{R_1} \frac{R_4}{R_3 + R_4}$$

with  $v_1 = \alpha T_B$  as in item d) and  $v_2 = \alpha T_A$  as in item b). This requires

$$K_1 = -\frac{R_2}{R_1} = -1, \quad K_2 = 2\frac{R_4}{R_3 + R_4} = 1$$

Possible choices of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are

$$R_1 = R_2 = R_3 = R_4 = 100\text{K}\Omega.$$

The final circuit diagram is as follows.

