

1-13 The 12-V automobile battery in Figure P1-13 has an output capacity of 100 ampere-hours (Ah) when connected to a head lamp that absorbs 200 watts of power. Assume the battery voltage is constant.

- (a) Find the current supplied by the battery.
- (b) How long can the battery power the headlight?

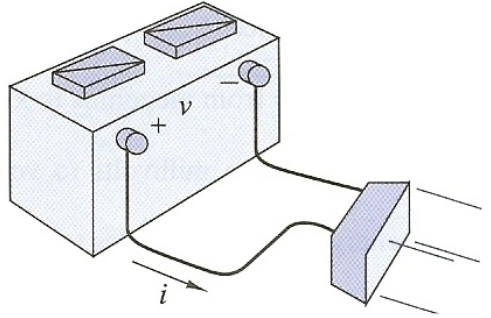


FIGURE P 1 - 13

1-21 Two electrical devices are connected as shown in Figure P1-21. Using the reference marks shown in the figure, find the power transferred and state whether the power is transferred from A to B or B to A when

- (a) $v = +33 \text{ V}$ and $i = -2.2 \text{ A}$
- (b) $v = -12 \text{ V}$ and $i = -1.2 \text{ mA}$
- (c) $v = +37.5 \text{ V}$ and $i = +40 \text{ mA}$
- (d) $v = -15 \text{ V}$ and $i = -43 \text{ mA}$

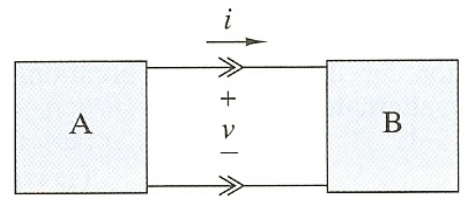


FIGURE P 1 - 21

2-5 In Figure P2-5 find R_x and the power delivered to the resistor.

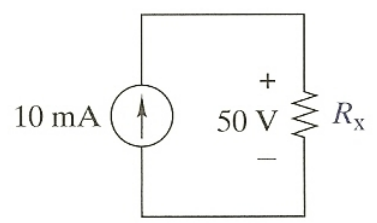


FIGURE P 2 - 5

2-10 In Figure P2-10 $i_2 = 2 \text{ A}$ and $i_3 = -5 \text{ A}$. Find i_1 and i_4 .

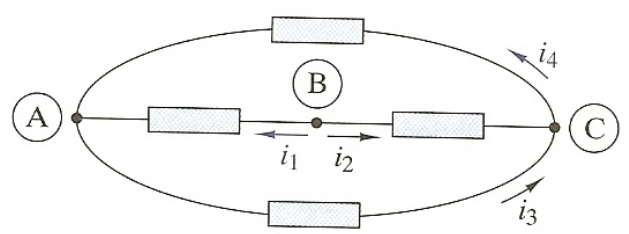


FIGURE P 2 - 10

2-28 Find the equivalent resistance R_{EQ} in Figure P2-28.

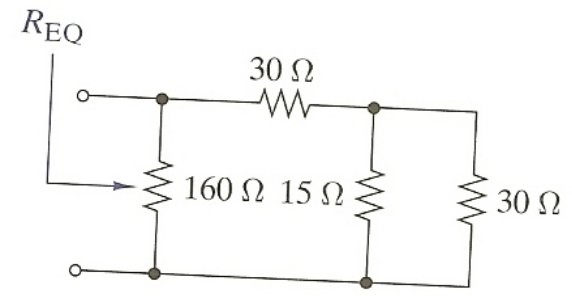


FIGURE P 2 - 28

2-40 Find the equivalent resistance between terminals A and B in Figure P2-40.

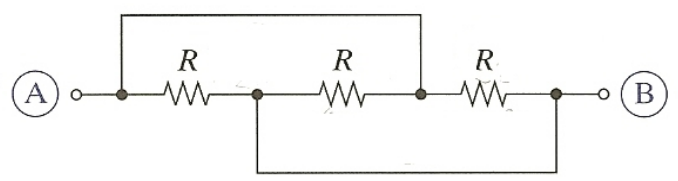


FIGURE P 2 - 40