

2-53 Use circuit reduction to find  $v_x$  in Figure P2-53.

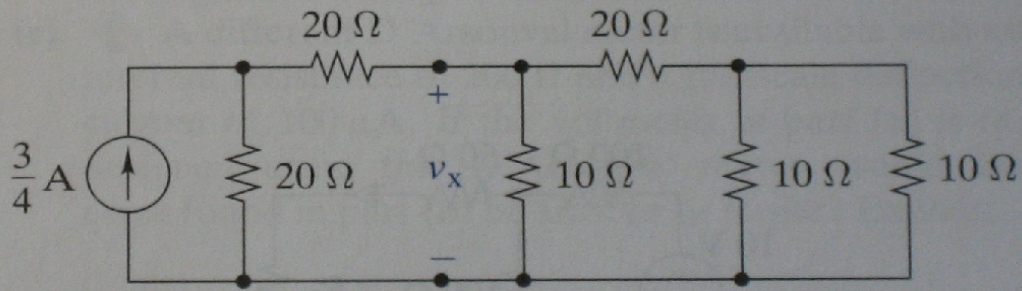


FIGURE P2-53

2-58 The current through  $R_L$  in Figure P2-58 is 40 mA. Use source transformations to find  $R_L$ .

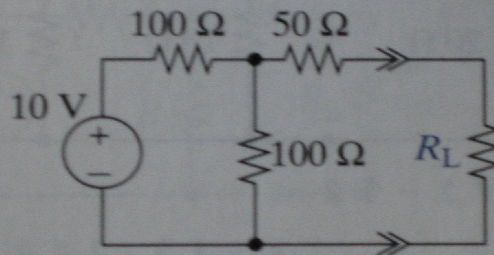


FIGURE P2-58

2-62 Center Tapped Voltage Divider **A**

Figure P2-62 shows a voltage divider with the center tap connected to ground. Derive equations relating  $v_A$  and  $v_B$  to  $v_S$ ,  $R_1$ , and  $R_2$ .

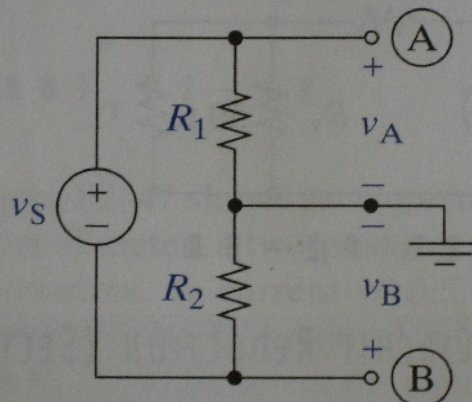


FIGURE P2-62

3-2 (a) Formulate node-voltage equations for the circuit in Figure P3-2.

(b) Use these equations to find  $v_x$  and  $i_x$ .

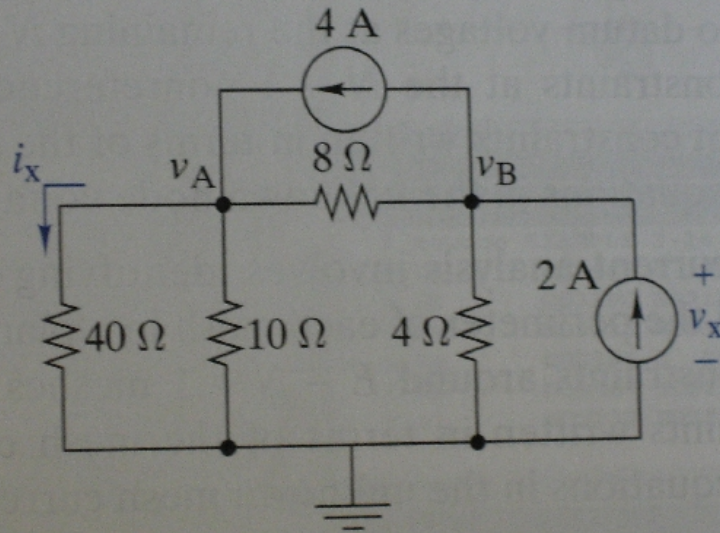


FIGURE P3-2

3-5 (a) Formulate node-voltage equations for the circuit in Figure P3-5.

(b) Solve for  $v_x$  and  $i_x$  when  $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$ ,  $v_s = 20 \text{ V}$ , and  $i_s = 2 \text{ mA}$ .

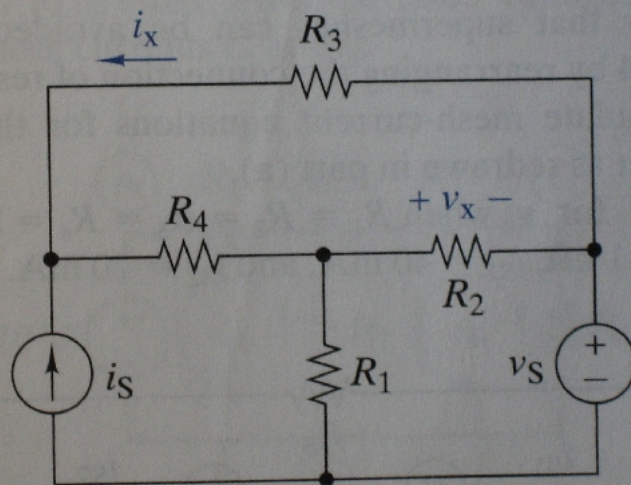


FIGURE P3-5

3-37 Find the Thévenin equivalent circuit seen by  $R_L$  in Figure P3-37. Find the voltage across the load when  $R_L = 5 \Omega$ ,  $10 \Omega$ , and  $50 \Omega$ .

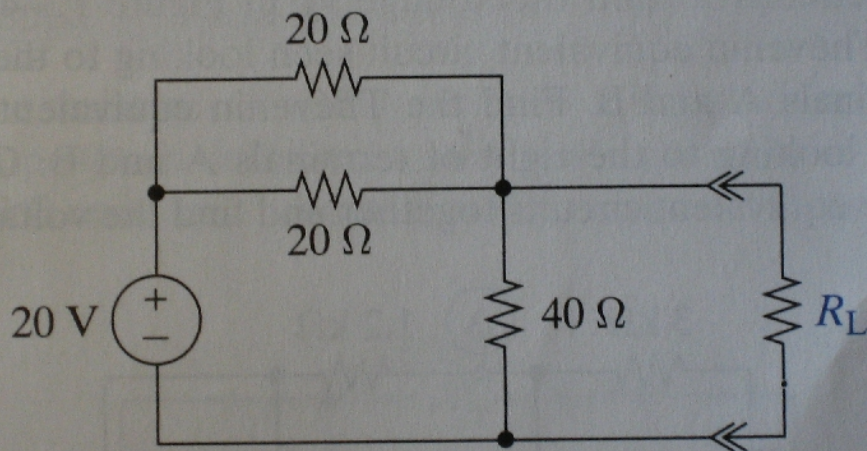


FIGURE P3-37

3-41 The purpose of this problem is to use Thévenin equivalent circuits to find the voltage  $v_X$  in Figure P3-41. Find the Thévenin equivalent circuit seen looking to the left of terminals A and B. Find the Thévenin equivalent circuit seen looking to the right of terminals A and B. Connect these equivalent circuits together and find the voltage  $v_X$ .

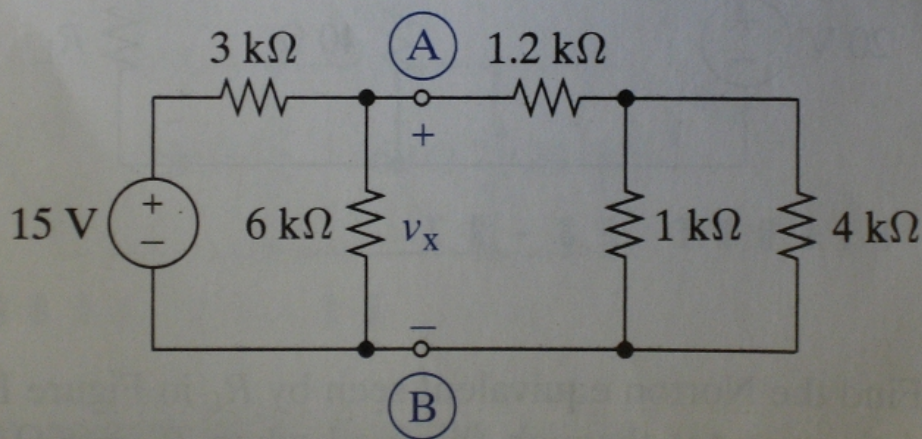


FIGURE P3-41