
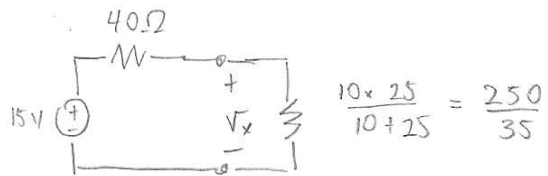
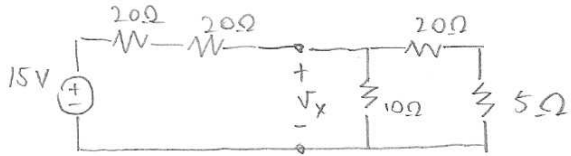






2-531

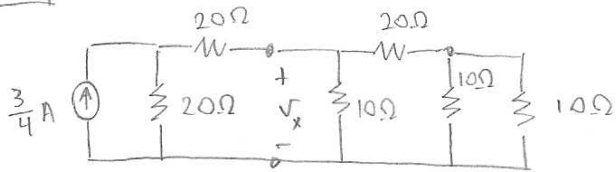

$$V_x = 15 \times \frac{250/35}{40 + 250/35}$$

$$V_x \approx 2.273$$

2/58

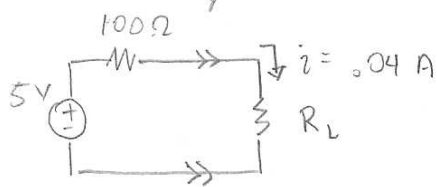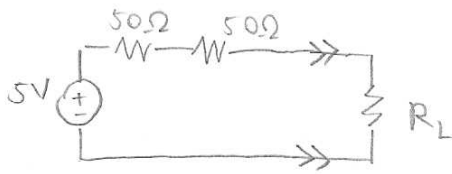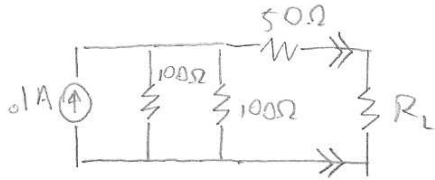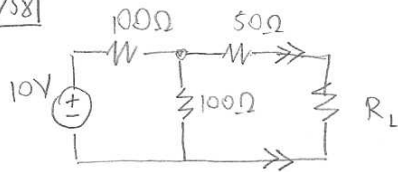


$$\text{KVL: } -5 + 0.04 \times 100 + 0.04 \times R_L = 0$$

$$R_L = 125 - 100 \Omega$$

$$\boxed{R_L = 25 \Omega}$$

2/62

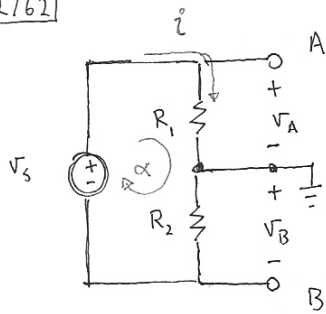

$$V_A = i R_1$$

$$V_B = -i R_2$$

KVL @ α

$$V_s - V_A + V_B = 0$$


$$V_s - i R_1 - i R_2 = 0$$

$$i = \frac{V_s}{R_1 + R_2}$$

$$\therefore V_A = V_s \frac{R_1}{R_1 + R_2}$$

$$V_B = -V_s \frac{R_2}{R_1 + R_2}$$

3/2

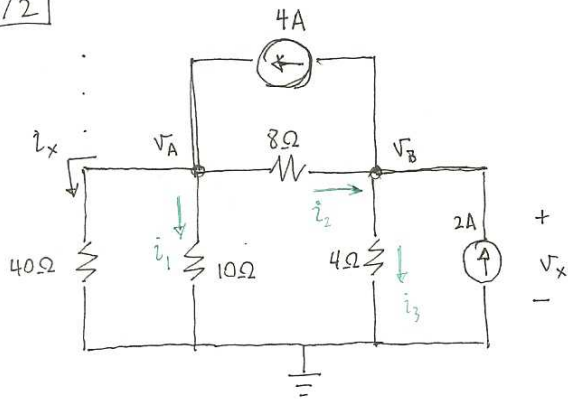

$$\text{KCL@A: } 4 - i_x - i_1 - i_2 = 0$$

$$\text{KCL@B: } i_2 - i_3 + 2 - 4 = 0$$

$$i_x = \frac{V_A}{40}$$

$$i_1 = \frac{V_A}{10}$$

$$i_2 = \frac{V_A - V_B}{8}$$

$$i_3 = \frac{V_B}{4}$$

$$\text{KCL@A: } \frac{V_A}{40} + \frac{V_A}{10} + \frac{V_A}{8} - \frac{V_B}{8} = 4$$

$$\text{KCL@B: } \frac{V_A}{8} - \frac{V_B}{8} - \frac{V_B}{4} = 2$$


$$\begin{bmatrix} \frac{1}{40} + \frac{1}{10} + \frac{1}{8} & -\frac{1}{8} \\ \frac{1}{8} & \frac{1}{8} - \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4 \\ 2 \end{bmatrix}$$

$$V_A = 16 \text{ V}$$

$$V_B = 0 \text{ V}$$

$$\therefore i_x = 0.4 \text{ A}$$
$$V_x = 0 \text{ V}$$

3/5 |

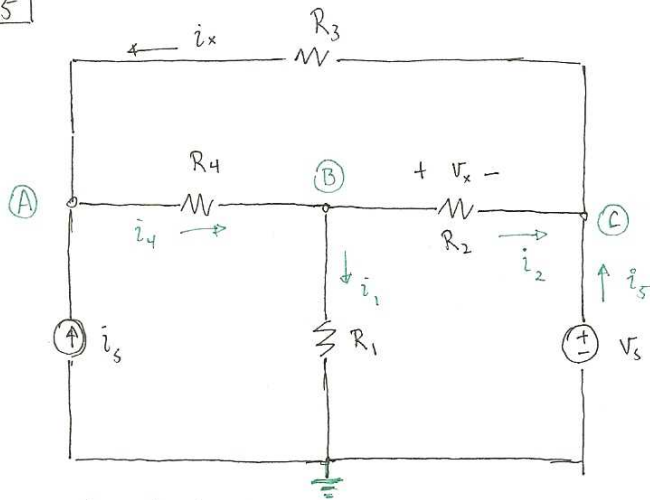

Step 1: Label!

Step 2: Set-up nodal equations

KCL @ A

$$i_s + i_x - i_4 = 0 \quad (1)$$

KCL @ B

$$i_4 - i_1 - i_2 = 0 \quad (2)$$

* KCL @ C is only necessary if you want to solve for i_s

$$i_1 = \frac{\varphi_B}{R_1} \quad i_2 = \frac{\varphi_B - \varphi_C}{R_2} \quad i_4 = \frac{\varphi_A - \varphi_B}{R_4} \quad i_x = \frac{\varphi_C - \varphi_A}{R_3}$$

$$\varphi_C = V_s$$

$$(1) \Rightarrow \frac{V_s}{R_3} - \frac{\varphi_A}{R_3} - \frac{\varphi_A - \varphi_B}{R_4} = -i_s$$

$$(2) \Rightarrow \frac{\varphi_A}{R_4} - \frac{\varphi_B}{R_4} - \frac{\varphi_B}{R_1} - \frac{\varphi_B - V_s}{R_2} = 0$$


Step 3: Arrange terms into a matrix equation

$$\begin{bmatrix} -\frac{1}{R_3} - \frac{1}{R_4} & \frac{1}{R_4} \\ \frac{1}{R_4} & -\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_4} \end{bmatrix} \begin{pmatrix} \varphi_A \\ \varphi_B \end{pmatrix} = \begin{pmatrix} -i_s - \frac{V_s}{R_3} \\ -\frac{V_s}{R_2} \end{pmatrix}$$


$$\left. \begin{array}{l} \varphi_A = 28 \text{ V} \\ \varphi_B = 16 \text{ V} \end{array} \right\} \begin{array}{l} i_x = \frac{V_s - \varphi_A}{R_3} = -0.8 \text{ mA} \\ v_x = \varphi_B - V_s = -4 \text{ V} \end{array}$$

$$\boxed{\begin{array}{l} i_x = -0.8 \text{ mA} \\ v_x = -4 \text{ V} \end{array}}$$

3/37

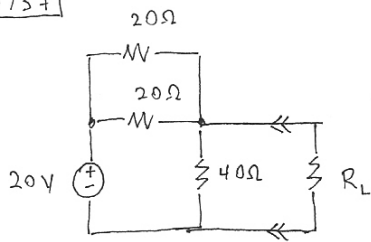

* easier to do by source transformations

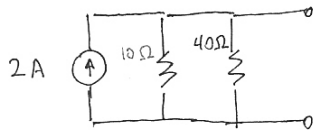


$$I_N = 2A$$

$$R_{eq} = \frac{10 \times 40}{10 + 40} \Omega$$

$$R_{eq} = 8 \Omega$$

$$V_{th} = I_N \times R_{eq} = 2 \times 8$$


$$V_{th} = 16 V$$

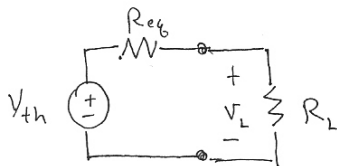

$$V_L = V_{th} \times \frac{R_L}{R_{eq} + R_L}$$


R_L	V_L
5Ω	6.15 V
10Ω	8.89 V
50Ω	13.8 V

3/41

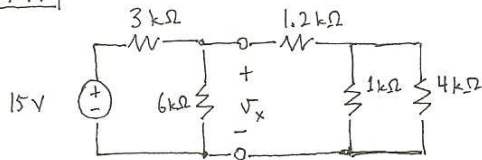

Thévenin eq. LHS

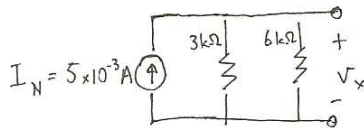* easier to do by source transformations (rather than by using SC/OC tests)





$$R_{eq} = \frac{3 \times 6}{3 + 6} \text{ k}\Omega = \boxed{2 \text{ k}\Omega = R_{eq(LHS)}}$$


$$V_{th} = I_N \times R_{eq} = 5 \times 10^{-3} \times 2 \times 10^3 = \boxed{10 \text{ V} = V_{th}}$$

Thévenin eq. RHS

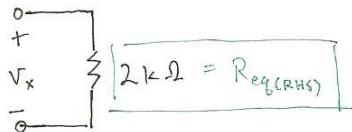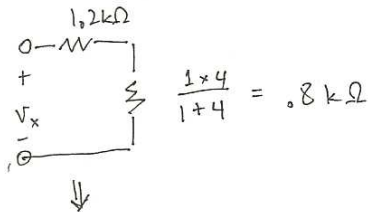* When there is not an independent source, the OC & SC tests will fail. Treat this as an equivalent resistance problem.



Combined:

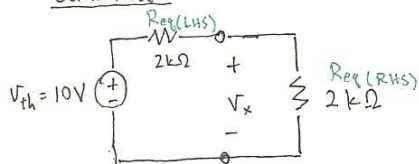

$$V_x = V_{th} \times \frac{R_{eq(RHS)}}{R_{eq(LHS)} + R_{eq(RHS)}} = 10 \times \frac{2}{4} \Rightarrow \boxed{V_x = 5 \text{ V}}$$