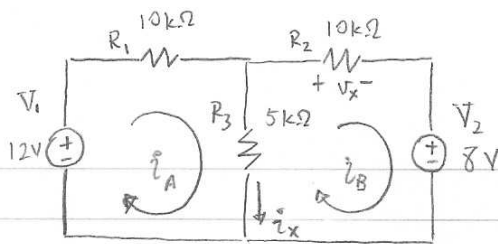


- 3/9 (a) Formulate mesh equations
 (b) Use mesh eqns to find v_x , i_x



(a) KVL A: $R_1(i_A) + R_3(i_A - i_B) = V_1$

$$\Rightarrow i_A(R_1 + R_3) + i_B(-R_3) = V_1$$

KVL B: $R_2(i_B) + R_3(i_B - i_A) = -V_2$

$$\Rightarrow i_A(-R_3) + i_B(R_2 + R_3) = -V_2$$

$$\therefore \begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} V_1 \\ -V_2 \end{pmatrix}$$

$$\Rightarrow \begin{bmatrix} 15\text{k}\Omega & -5\text{k}\Omega \\ -5\text{k}\Omega & 15\text{k}\Omega \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 12\text{V} \\ -8\text{V} \end{pmatrix}$$

$$i_A = 0.7\text{ mA}$$

$$i_B = -0.3\text{ mA}$$


(b) $v_x = i_B \times R_2$

$$v_x = -3\text{ V}$$

$$i_x = i_A - i_B$$

$$i_x = 1\text{ mA}$$

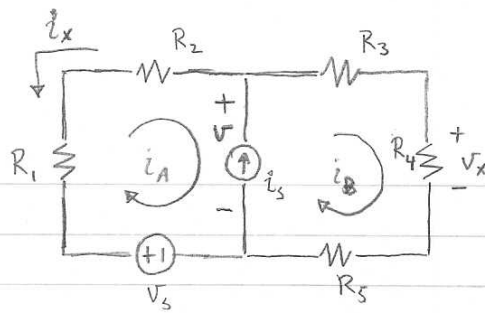- 3/12 (a) Formulate mesh eqns.
 (b) Find v_x , i_x when
 $R_1 = 200\Omega$, $R_2 = 300\Omega$,
 $R_3 = 50\Omega$, $R_4 = 250\Omega$,
 $R_5 = 200\Omega$, $i_s = 50\text{mA}$,
 $V_s = 15\text{V}$



- (c) Find total power dissipated by circuit.

- (a) Note: Super nodes & super meshes are useful tricks to greatly expedite the solutions of circuit problems, and they have insightful conceptual foundations; however, always remember that they, like establishing equations by inspection, are short-cuts. You can always fall back on just KCL, KVL, and Ohm's Law and a little math to solve any linear circuit problem, so don't spend time remembering how to apply the tricks. Instead, use your time to understand why the tricks work.

$$\text{KVL @ A: } R_1 i_A + R_2 i_A = V_s - V; \quad V \triangleq \text{voltage gain across } i_s$$

$$\text{KVL @ B: } R_3 i_B + R_4 i_B + R_5 i_B = V$$

$$\text{combining: } (R_1 + R_2) i_A + (R_3 + R_4 + R_5) i_B = V_s$$

$$\text{also note that } i_B = i_s + i_A$$

$$\therefore (R_1 + R_2 + R_3 + R_4 + R_5) i_A = V_s - (R_3 + R_4 + R_5) i_s$$

- (b) subst. appropriate values $\Rightarrow i_A = \frac{V_s - (R_3 + R_4 + R_5) i_s}{R_1 + R_2 + R_3 + R_4 + R_5}$

$$P = 2V \quad i = \frac{1}{2} \quad \dots$$

$$i_A = -10\text{mA}$$

$$i_B = i_s - i_A = 40\text{mA}$$

$$i_x = -i_A$$

$$v_x = R_4 i_B$$

$$i_x = 10\text{mA}$$


$$v_x = 10\text{V}$$

- (c) Current is forced through V_s
 $\Rightarrow V_s$ dissipates power

$$P = i_A^2 (R_1 + R_2) + i_B^2 (R_3 + R_4 + R_5) - V_s i_A$$

$$P = 1\text{W}$$

3/28

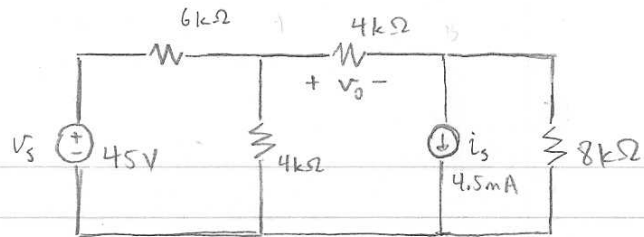Use super position
Find V_o 

Turn off the voltage source.
 $\Rightarrow V_s = 0 \Rightarrow$ short circuit

KCL @ A

$$V_A \left(\frac{1}{2.4+4} + \frac{1}{8} \right) \times 10^{-3} = -4.5 \times 10^{-3}$$

$$V_A = -16 \text{ V}$$

$$-V_{o1} = V_A - \underbrace{V_A \times \frac{2.4}{4+2.4}}$$

↑ note the minus sign!
 voltage divider

$$V_{o1} = +10 \text{ V}$$

Turn off current source
 $\Rightarrow i_s = 0 \Rightarrow$ open circuit

$$\text{KVL A: } 6\text{k}\Omega \times i_A + 4\text{k}\Omega \times (i_A - i_B) = 45\text{V}$$

$$\text{KVL B: } 4\text{k}\Omega (i_B - i_A) + 4\text{k}\Omega \times i_B + 8\text{k}\Omega \times i_B = 0$$

$$10^3 \times \begin{bmatrix} 6+4 & -4 \\ -4 & 4+4+8 \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 45 \\ 0 \end{pmatrix}$$


$$i_B = 1.25 \text{ mA}$$

$$V_{o2} = 4\text{k}\Omega \times 1.25 \text{ mA}$$

$$V_{o2} = 5 \text{ V}$$

$$\therefore V_o = V_{o1} + V_{o2}$$

$$V_o = 15 \text{ V}$$

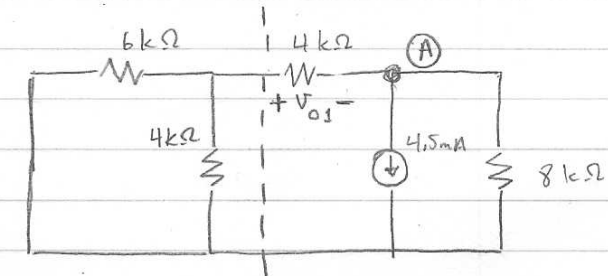

$$R_{eq} = \frac{4 \times 6}{4+6} = 2.4\text{k}\Omega$$

