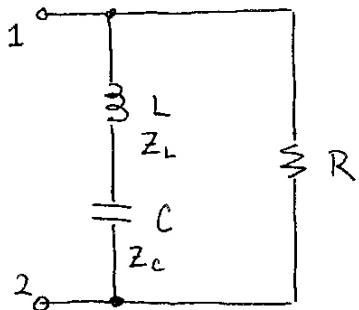


10/3

1st Transform circuit to s-domain

$$Z_L = sL$$

$$Z_c = \frac{1}{sC}$$

(No IC for an equivalent impedance problem)

2nd Apply methods for resistive networks

$$\begin{aligned} Z_{eq} &= \left(\frac{1}{Z_L + Z_c} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{1}{sL + \frac{1}{sC}} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{sC}{s^2LC + 1} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{sRC + s^2LC + 1}{s^2RLC + R} \right)^{-1} \\ &= R \times \frac{s^2 + 1/(LC)}{s^2 + s(R/L) + (LC)^{-1}} \end{aligned}$$

where $\left\{ \begin{array}{l} R = 4 \times 10^3 \Omega \\ L = 0.4 \text{ H} \\ C = 10^{-7} \text{ F} \end{array} \right.$

Use the following MatLab command:

```


>> R = 4e3; L = .4; C = 1e-7; syms s
>> eval(solve('s^2 + 1/(L*C)', 's'))
>> eval(solve('s^2 + s*(R/L) + 1/(L*C)', 's'))

```

Zeroes: $\pm 5000j$ rad/sPole: -5000 rad/s

$$Z_{eq} = 4 \times 10^3 \frac{(s + 5000j)(s - 5000j)}{(s + 5000)^2}$$

10/13

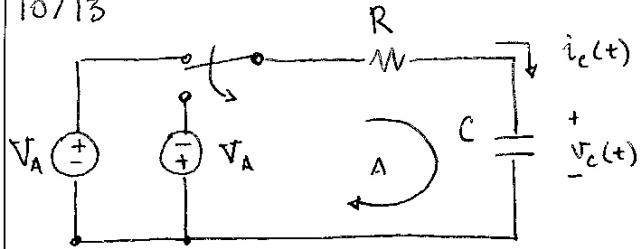1st Transform circuit to s -domain

$$i_c(t) = C \frac{dv_c}{dt}$$

$$\Rightarrow i_c(s) = sC V_c(s) - C V_c(0)$$

$$\text{closing switch} \Rightarrow V_A u(t) \rightarrow V_A / s$$

2nd Apply KCL or KVL (KVL is slightly easier)

$$\text{note: } i_c(s) = sC V_c(s) - C V_c(0)$$

$$i_c(s) + C V_c(0) = sC V_c(s)$$

$$V_c(s) = (sC)^{-1} i_c(s) + s^{-1} V_c(0)$$

$$\underline{\text{KVL @ A:}} s^1 V_A + i_c(s) R + (sC)^{-1} i_c(s) + s^{-1} V_c(0) = 0$$


$$CV_A + i_c(s) sRC + i_c(s) + CV_A = 0$$

$$i_c(s) = -2CV_A \times \frac{1}{sRC + 1}$$

$$i_c(s) = -\frac{2V_A}{R} \times \frac{1}{s + (RC)^{-1}}$$

$$i_c(t) = -\frac{2V_A}{R} \times e^{-t/RC} u_t$$

10/21

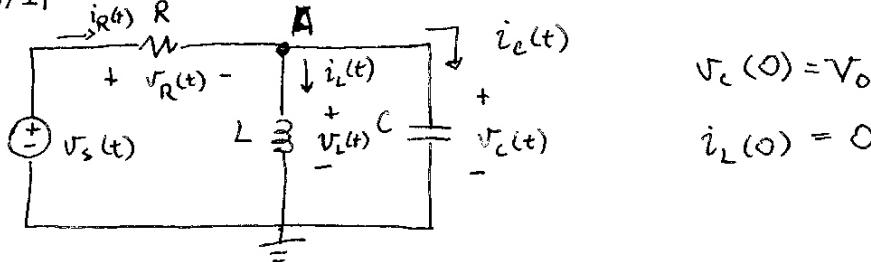

$$v_c(0) = V_0$$

$$i_L(0) = 0$$

In the s-domain:

$$i_c(s) = sC v_c(s) - C v_c(0) \Leftrightarrow v_c(s) = (sC)^{-1} i_c(s) + s^{-1} v_c(0)$$

$$v_L(s) = sL i_L(s) - L i_L(0) \Leftrightarrow i_L(s) = (sL)^{-1} v_L(s) + s^{-1} i_L(0)$$

Zero-state : $v_c(0) = 0, i_L(0) = 0$

$$\text{KCL @ A: } i_R - i_L - i_c = 0$$

$$v_A = v_L = v_c$$

$$\frac{1}{R} (v_s - v_A) - (sL)^{-1} v_L(s) - sC v_c(s) = 0$$

$$\frac{1}{R} (v_s - v_A) - (sL)^{-1} v_A(s) - sC v_A(s) = 0$$

$$v_A(s) \left(-\frac{1}{R} - \frac{1}{sL} - sC \right) = -\frac{v_s(s)}{R}$$

$$v_A(s) (sL + R + s^2 RLC) = sL v_s(s)$$

$$v_A(s) = \boxed{\frac{sL}{s^2 RLC + sL + R} v_s(s) = v_c(s)} \quad (\text{for zero state})$$

Zero-input : $v_s(t) = 0, v_c(0) = V_0, i_L(0) = 0$


$$\text{KCL @ A: } i_R - i_L - i_c = 0$$

$$\frac{1}{R} (-v_c(s)) - (sL)^{-1} v_c(s) - s^{-1} \cancel{i_L(0)} - sC v_c(s) + C v_c(0) = 0$$

$$v_c(s) \left(-\frac{1}{R} - \frac{1}{sL} - sC \right) = -CV_0$$

$$\boxed{v_c(s) = \frac{sRLCV_0}{s^2 RLC + sL + R}} \quad (\text{for zero input})$$

10/35

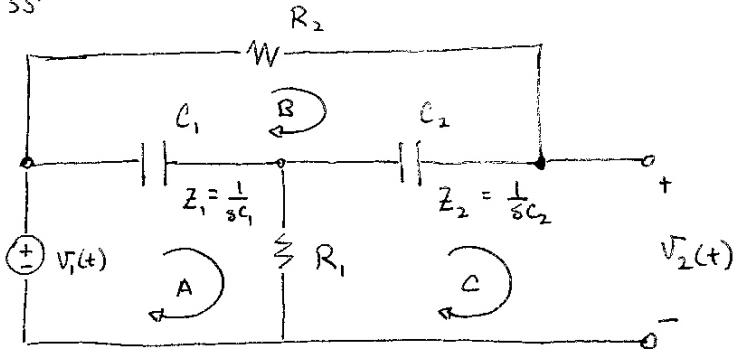

No initial energy $\Rightarrow v_{c_1}(0) = v_{c_2}(0) = 0$

(a) In the s-domain

$$Z_{c_1} = \frac{1}{sC_1} \Leftrightarrow i_{c_1}(s) = sC_1 v_{c_1}(s)$$

$$Z_{c_2} = \frac{1}{sC_2} \Leftrightarrow i_{c_2}(s) = sC_2 v_{c_2}(s)$$

Answer:

$$\frac{V_2(s)}{V_1(s)} =$$

$$s^2 R_1 R_2 C_1 C_2 + s(R_1 C_1 + R_2 C_2) + 1$$

$$s^2 R_1 R_2 C_1 C_2 + s(R_1 C_1 + R_2 C_2 + R_1 C_2) + 1$$

Mesh equations:

$$\left. \begin{array}{l} A: \frac{1}{sC_1} (i_A - i_B) + R_1 (i_A - i_C) = V_1(s) \\ B: \frac{1}{sC_1} (i_B - i_A) + R_2 (i_B) + \frac{1}{sC_2} (i_B - i_C) = 0 \\ C: R_1 (i_C - i_A) + \frac{1}{sC_2} (i_C - i_B) = -V_2(s) \end{array} \right\} \quad (1)$$

noting that $i_C(s) = 0$

$$(1) \Rightarrow \left. \begin{array}{l} \left(R_1 + \frac{1}{sC_1} \right) i_A + \left(-\frac{1}{sC_1} \right) i_B = V_1(s) \\ \left(-\frac{1}{sC_1} \right) i_A + \left(R_2 + \frac{1}{sC_1} + \frac{1}{sC_2} \right) i_B = 0 \\ \left(-R_1 \right) i_A + \left(-\frac{1}{sC_2} \right) i_B = -V_2(s) \end{array} \right\} \quad \begin{array}{l} (2) \\ (3) \\ (4) \end{array}$$

$$(b) 3 \Rightarrow i_A = i_B \left(sC_1 R_2 + 1 + \frac{C_1}{C_2} \right)$$

$$2 \Rightarrow \left[\left(R_1 + \frac{1}{sC_1} \right) \left(sC_1 R_2 + 1 + \frac{C_1}{C_2} \right) - \frac{1}{sC_1} \right] i_B = V_1(s)$$


$$1 \Rightarrow \left[-R_1 \left(sC_1 R_2 + 1 + \frac{C_1}{C_2} \right) - \frac{1}{sC_2} \right] i_B = -V_2(s)$$

$$V_2(s) \left[sR_1 R_2 C_1 + R_1 + \frac{R_1 C_1}{C_2} + \frac{1}{sC_2} \right]^{-1} = i_B(s)$$

$$\left[sR_1 R_2 C_1 + R_1 + \frac{C_1 R_1}{C_2} + R_2 + \cancel{\frac{1}{sC_1}} + \frac{1}{sC_2} - \cancel{\frac{1}{sC_1}} \right] \left(sR_1 R_2 C_1 + R_1 + \frac{R_1 C_1}{C_2} + \frac{1}{sC_2} \right)^{-1} = \frac{V_1}{V_2}$$

answer @ top

10/44

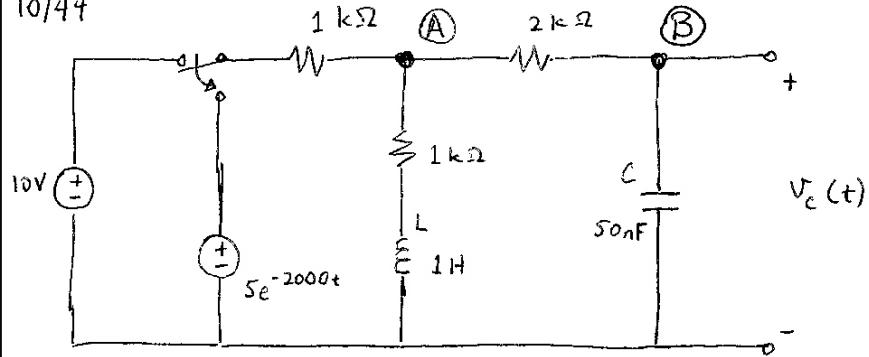

Initial conditions:

$$i_L(0) = \frac{10V}{2k\Omega} = 5 \times 10^{-3} A$$

$$v_c(0) = 10V \times \frac{1k\Omega}{1+1k\Omega} = 5V$$

Answer:

$$v_c(t) = 50e^{-2000t} + 5.3e^{6425t} - 50e^{-1025t}$$

After the switch is closed:

$$\text{KCL @ A: } \left(\frac{5}{s+2000} - v_A \right) \times \frac{1}{1k\Omega} +$$

$$\frac{1}{1k\Omega} \left(v_A - \frac{5}{s+2000} \right) + i_L + \frac{v_A - v_B}{2k\Omega} = 0$$

$$sL i_L - L i_L(0) = v_L$$

$$i_L = (sL)^{-1} v_L + s^{-1} (5 \times 10^{-3})$$

$$v_L = v_A - i_L (1000 \Omega)$$

$$i_L (1 + 1000/(sL)) = (sL)^{-1} v_A + s^{-1} (5 \times 10^{-3})$$

$$\Rightarrow 10^{-3} \left(v_A - \frac{5}{s+2000} \right) + (v_A + 5 \times 10^{-3})/(s+1000) + \frac{v_A - v_B}{2000} = 0$$

$$\text{KCL @ B: } \frac{v_A - v_B}{2000} - i_C = 0$$

$$i_C = sC v_C - C v_C(0)$$

$$= sC v_C - sC$$

$$= 5 \times 10^{-8} s v_C - 2.5 \times 10^{-7}$$

$$\frac{v_A - v_B}{2000} - 2.5 \times 10^{-7} + 5 \times 10^{-8} s v_B = 0$$

Use MatLab

$$\begin{cases} v_A = (s^2 + 10^3 s + 2.2 \times 10^7) / (-9 \times 10^{10} s^2 - 7 \times 10^7 s - 8 \times 10^{10} + 3s^3) \\ v_B = 5(3 \times 10^4 + 1.1 \times 10^4 s + 3s^2) / (-9 \times 10^3 s^2 - 7 \times 10^7 s - 8 \times 10^{10} + 3s^3) \end{cases}$$