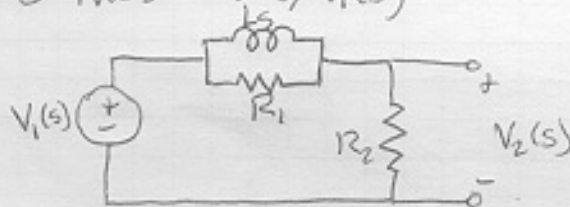


P.11.2 find driving pt. impedance & $T_V(s) = V_2(s)/V_1(s)$

$$Z_{EQ} = R_2 + \frac{R_1 Ls}{R_1 + Ls}$$

$$Z_{EQ} = \frac{(R_1 + R_2)Ls + R_1 R_2}{R_1 + Ls}$$



$$V_2(s) = T_V(s) V_1(s) \rightarrow \text{voltage divider}$$

$$T_V(s) = \frac{R_2}{Z_{EQ}}$$


$$T_V(s) = \frac{R_2(Ls + R_1)}{(R_1 + R_2)Ls + R_1 R_2}$$

P.11.4 find driving pt. impedance & $T_V(s)$

OP-AMP Golden rule $I_N = I_P = 0$


$$\therefore Z_{EQ} = \infty$$
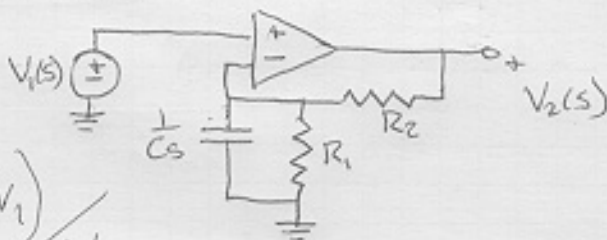
$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{R_2 + \left(\frac{1}{R_1 + Cs}\right) \cdot V_1}{\left(\frac{1}{R_1 + Cs}\right) V_1}$$



$$T_V(s) = \frac{R_1 R_2 Cs + R_1 + R_2}{R_1}$$

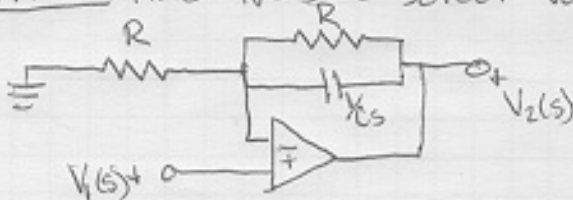P.11.7 find $T_V(s)$ & select values of R & C so there is a pole @ $s = -500 \text{ rad/s}$



inverting amplifier

$$T_V(s) = \frac{R}{RCs + 1} + R$$

$$T_V(s) = \frac{RCs + 2}{RCs + 1}$$

any values of R & C

such that


$$RC = \frac{1}{500}$$

ex.

$$R = 1 \text{ k}\Omega$$

$$C = 2 \mu\text{F}$$

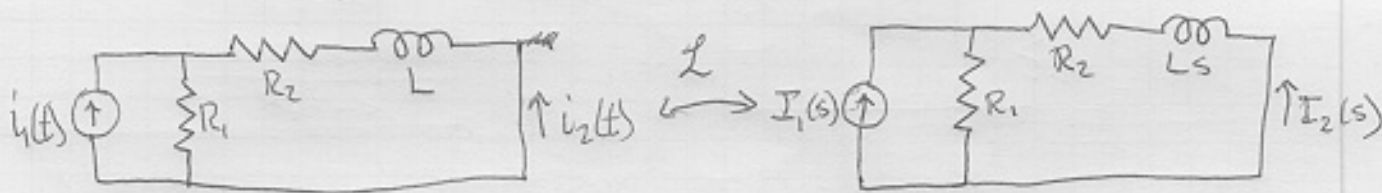P.11.28 If circuit is in steady state with $i_1(t) = 10 \cos 500t$ mA
 & $R_1 = 100 \Omega$, $R_2 = 400 \Omega$, & $L = 100$ mH
 find $i_{2ss}(t)$. Repeat with $i_1(t) = 10 \cos 5000t$ mA



with input $i_1(t) = A \cos(\omega t)$
 steady state output will have the form $i_{ss}(t) = A |T(j\omega)| \cos(\omega t + \theta)$

so what is $T(s) \rightarrow$ use current divider where $\theta = \angle T(j\omega)$

$$T(s) = \frac{\frac{1}{R_2 + Ls}}{\frac{1}{R_1} + \frac{1}{R_2 + Ls}} = \frac{R_1}{Ls + R_1 + R_2} = \frac{R_1/L}{s + \frac{R_1 + R_2}{L}}$$

with given values $T(s) = \frac{1000}{s + 5000}$

$$|T(j500)| = \frac{1000}{\sqrt{500^2 + 5000^2}} = \frac{2}{\sqrt{101}}$$

$$\theta(j500) = 0 - \tan^{-1}\left(\frac{500}{5000}\right)$$

$$i_1(t) = 10 \cos(500t) \text{ mA}$$

$$i_{2ss}(t) = -10 |T(j500)| \cos(500t + \theta) \text{ mA}$$

$$= 10 |T(j500)| \cos(500t + \pi + \theta) \text{ mA}$$

$$i_{2ss}(t) \approx 1.99 \cos(500t + 3.04) \text{ mA}$$

$$i_1(t) = 10 \cos(5000t) \text{ mA}$$

$$|T(j5000)| = \frac{1000}{\sqrt{5000^2 + 5000^2}} = \frac{1}{5\sqrt{2}}$$

$$\theta = 0 - \tan^{-1}\left(\frac{5000}{5000}\right)$$


$$i_{2ss}(t) \approx 10 \frac{1}{5\sqrt{2}} \cos(5000t + \pi + \theta) \text{ mA}$$

$$i_{2ss}(t) \approx 1.41 \cos(5000t + 2.356) \text{ mA}$$


P.11.53 Design a circuit to fit $T_V(s) = \pm \frac{1000s}{(s+500)(s+1000)}$

using only resistors, capacitors & not more than one OP-AMP
 - scale it so that the final design uses only 20kΩ resistors
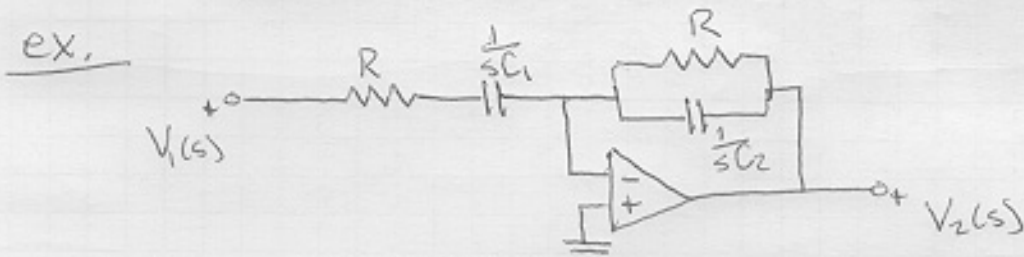
$$T_V(s) = \frac{k_1}{s+500} \frac{k_2 s}{s+1000}$$



inverting amplifier ~~form~~

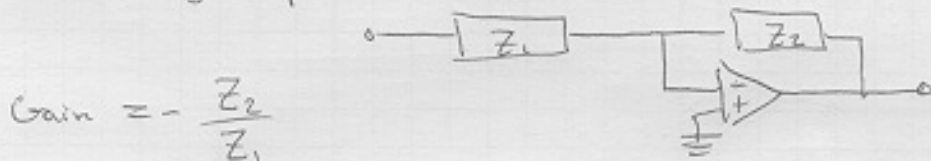

$$\text{Gain} = - \frac{Z_2}{Z_1}$$

in example $Z_2 = \frac{1}{\frac{1}{R} + sC_2} = \frac{R}{RC_2s + 1}$

$$Z_1 = R + \frac{1}{sC_1} = \frac{RC_1s + 1}{C_1s}$$

$$T_V(s) = - \frac{Z_2}{Z_1} = - \frac{R}{RC_2s + 1} \frac{C_1s}{RC_1s + 1}$$

$$= - \frac{1}{RC_2} \frac{1}{s + \frac{1}{RC_2}} \frac{s}{s + \frac{1}{RC_1}}$$

if $R = 20k\Omega$



$C_1 = 100nF$

$C_2 = 50nF$

$$T_V(s) = - \frac{1000s}{(s+500)(s+1000)}$$

P.11.58 Show that both circuits satisfy the transfer function
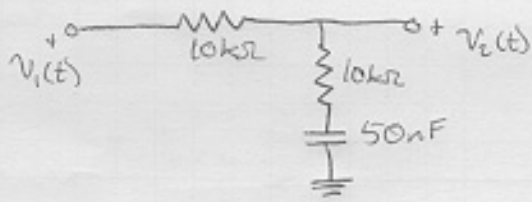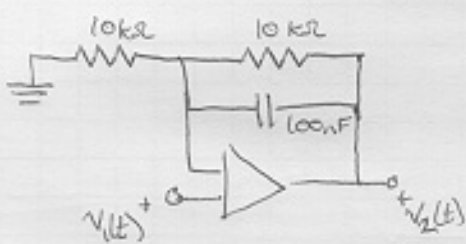
$$T_V(s) = K \left(\frac{s+2000}{s+1000} \right)$$



non-inverting amplifier

$$\begin{aligned} \text{Gain} = T_V(s) &= \frac{R/Cs}{R + 1/Cs} + R \\ &= \frac{R}{RCs + 1} \\ T_V(s) &= \frac{s + 2/RC}{s + 1/RC} \\ T_V(s) &= \frac{s + 2000}{s + 1000} \end{aligned}$$

voltage divider

$$\begin{aligned} V_2(s) &= \frac{R + 1/Cs}{R + R + 1/Cs} V_1(s) \\ T_V(s) &= \frac{R + 1/Cs}{2R + 1/Cs} \\ &= \frac{RCs + 1}{2RCs + 1} \\ &= \frac{1}{2} \frac{s + 1/RC}{s + 1/2RC} \\ T_V(s) &= \frac{1}{2} \frac{s + 2000}{s + 1000} \end{aligned}$$

~~Which circuit would you choose to drive a 1kΩ load?~~

b) Which circuit would you choose to drive a 1kΩ load?

OP-AMP circuit


c) Which would you pick if driven by a 50Ω source?

OP-AMP circuit

d) Do you agree with the statement that the transfer function would be $|T_V(s)|^2$ if the two circuits were connected in cascade, regardless of order? Explain.

Yes. Neither order would suffer from loading,

P.12.4) find $T_V(s)$

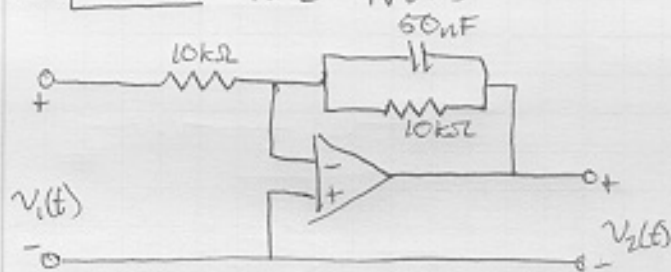

inverting amplifier

$$T_V(s) = - \frac{\left(\frac{R}{RCs+1}\right)}{R}$$

$$= - \frac{1}{RCs+1}$$

$$T_V(s) = - \frac{1}{RC} \frac{1}{s + 1/RC}$$

$$T_V(s) = - \frac{2000}{s + 2000}$$

a) $\boxed{\text{dc gain} = |T(0)| = 1}$



$\boxed{\text{infinite frequency gain} = |T(\infty)| = 0}$

$\boxed{\text{cutoff frequency} = \text{absolute value of pole} = 2000 \text{ rad/s}}$

$\boxed{\text{what type of filter is this?}}$

$\boxed{\text{Low-Pass}}$

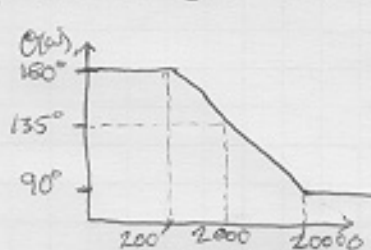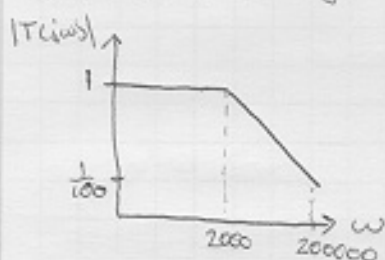b) Draw a straight line approx. for gain & phase of $T_V(j\omega)$



$$\theta(\omega) = \pi - \tan^{-1}\left(\frac{\omega}{2000}\right)$$

c) What element values would you change to double the passband gain without changing the cutoff frequency?

have the left most resistor
i.e. make it $5k\Omega$


P.12.10 a) Identify the gain response, cutoff frequency & passband gain for $T(s) = \frac{10/s}{100/s + 1/20}$

b) Sketch straight line gain response & estimate the gain for $0.5\omega_c$, ω_c , $2\omega_c$

a) $|T(0)| \rightarrow 1/10$
 $|T(\infty)| \rightarrow 0$ Low - Pass


$\omega_c = 2000 \frac{\text{rad}}{\text{s}}$

passband gain $|T(0)| = \frac{1}{10}$

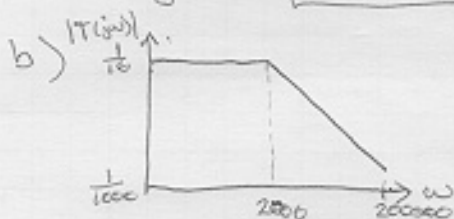

$|T(0.5\omega_c)| \approx \frac{1}{10}$
 $|T(\omega_c)| \approx \frac{1}{10\sqrt{2}}$
 $|T(2\omega_c)| \approx \frac{1}{100}$

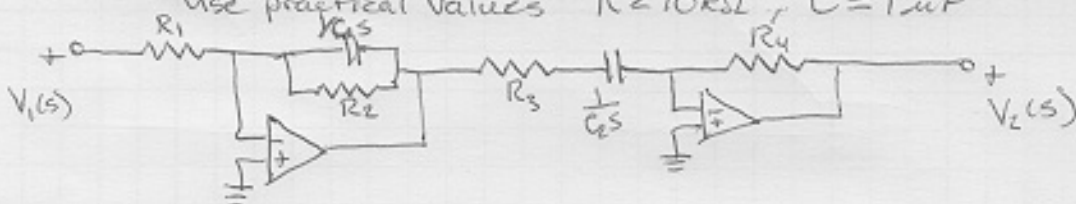P.12.15 for the circuit, identify the elements that control the two cutoff frequencies & select element values so that the passband gain is 10 & the cutoff frequencies are $100 \frac{\text{rad}}{\text{s}}$ & $2500 \frac{\text{rad}}{\text{s}}$.
 Use practical values $R \geq 10\text{k}\Omega$, $C \leq 1\mu\text{F}$



cascade connection of high-pass & low-pass

$T(s) = T_1(s) \cdot T_2(s)$

$T_1(s) = -\frac{R_2}{R_1} \frac{1}{s + \frac{1}{R_2 C_1}}$ $T_2(s) = -\frac{R_4 C_2}{R_3 C_2} \frac{s}{s + \frac{1}{R_3 C_2}}$

$T_V(s) = \frac{R_2 R_4}{R_1 R_3} \frac{1}{s + \frac{1}{R_2 C_1}} \frac{s}{s + \frac{1}{R_3 C_2}}$

$R_2, R_3, C_1, \& C_2$ determine the cutoff frequencies

ex. select

$R_2 = 10\text{k}\Omega, C_1 = 40\text{nF}$ $\omega_{c1} = 2500 \frac{\text{rad}}{\text{s}}$
 $R_3 = 10\text{k}\Omega, C_2 = 1\mu\text{F}$ $\omega_{c2} = 100 \frac{\text{rad}}{\text{s}}$

take $\omega_{c1} \ll \omega \ll \omega_{c2}$

$T(j\omega) = \frac{R_4}{R_1} \frac{1}{j\omega} \frac{j\omega}{\omega_{c2}} = \frac{R_4}{R_1} \frac{1}{2500} \stackrel{\text{set}}{=} 10$


$R_4 = 2500 R_1$

choose

$R_4 = 25\text{M}\Omega$

$R_1 = 10\text{k}\Omega$

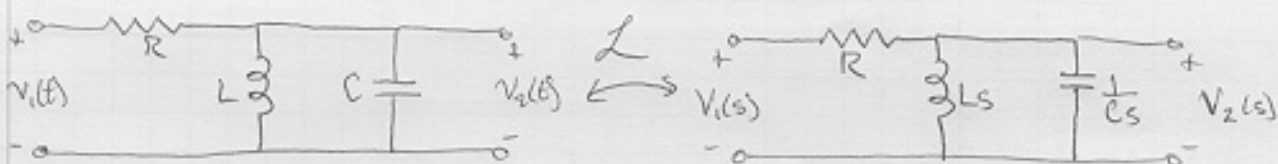P.12.28 for the bandpass circuit find $T_V(s)$, B , Q , ω_{c1} & ω_{c2} when $R=50\Omega$, $L=50\mu\text{H}$ & $C=20\text{nF}$



voltage divider

$$V_2(s) = \frac{\left(\frac{1}{Ls + Cs}\right)}{R + \left(\frac{1}{Ls + Cs}\right)} V_1(s) \Rightarrow T_V(s) = \frac{\left(\frac{1}{Ls + Cs}\right)}{R + \left(\frac{1}{Ls + Cs}\right)}$$

$$= \frac{Ls}{RLCs^2 + Ls + R}$$

$$T_V(s) = \frac{1}{RC} \frac{s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$T_V(s) = \frac{1}{R} \frac{1}{Cs + \frac{1}{Ls} + \frac{1}{R}}$$

the cutoff frequencies occur when

$$\left(Cs + \frac{1}{Ls}\right) \Big|_{s=j\omega} = \pm \frac{j}{R}$$

$$\Rightarrow -\omega^2 \pm \frac{1}{RC}\omega + \frac{1}{LC} = 0$$

by quadratic formula

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \approx 6.18 \times 10^5 \frac{\text{rad}}{\text{s}}$$

$$\omega_{c2} = +\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \approx 1.62 \times 10^6 \frac{\text{rad}}{\text{s}}$$

$$B = \omega_{c2} - \omega_{c1} = \frac{1}{RC} = 10^6 \frac{\text{rad}}{\text{s}}$$

$$Q = \frac{\omega_0}{B} = R\sqrt{\frac{C}{L}} = 1$$