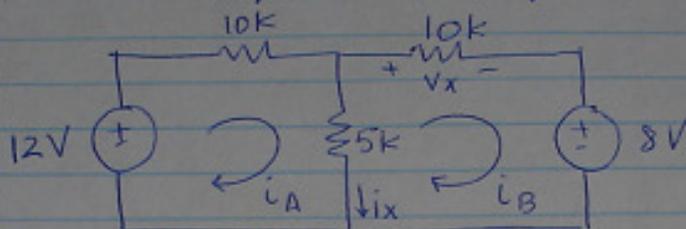


- 3.9a) Formulate mesh-current equations for the circuit  
 b) Use these equations to find  $V_x$  and  $i_x$ .



$$V_x = 10k i_B$$

$$i_x = i_A - i_B$$

KVL in loop A:

$$10k i_A + 5k(i_A - i_B) - 12 = 0$$

$$10k i_A + 5k i_A - 5k i_B = 12$$

$$15k i_A - 5k i_B = 12$$

KVL in loop B:

$$10k i_B + 8 + 5k(i_B - i_A) = 0$$

$$10k i_B + 5k i_B - 5k i_A = -8$$

$$15k i_B - 5k i_A = -8$$

$$\begin{bmatrix} 10k+5k & -5k \\ -5k & 10k+5k \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 12 \\ -8 \end{bmatrix}$$

$$i_A = \frac{5k i_B + 12}{15k}$$

$$15k i_B - 5k \left( \frac{5k i_B + 12}{15k} \right) = -8$$

$$15k i_B - \frac{5k}{3} i_B - 4 = -8$$

$$45k i_B - 5k i_B = 3(-4)$$

$$40k i_B = -12$$

$$i_B = \frac{-12}{40k} = \frac{-3}{10k} = -0.3 \text{ mA}$$

$$i_A = \frac{5(-0.3) + 12}{15k}$$

$$= \frac{10.5}{15k} = 0.7 \text{ mA}$$


$$V_x = 10k(-0.3 \text{ mA})$$

$$V_x = 3 \text{ V}$$

$$i_x = 1 \text{ mA}$$

26 4:

3.16)

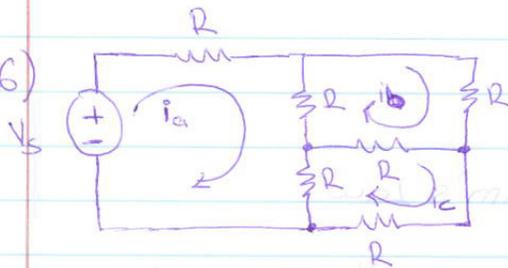

a) Mesh A:  $-V_s + Ri_a + R(i_a - i_b) + R(i_a - i_c) = 0$

$$\Rightarrow 3Ri_a - Ri_b - Ri_c = V_s$$


Mesh B:  $R(i_b - i_a) + Ri_b + R(i_b - i_c) = 0$

$$\Rightarrow -Ri_a + 3Ri_b - Ri_c = 0$$

Mesh C:  $R(i_c - i_a) + R(i_c - i_b) + Ri_c = 0$

$$\Rightarrow 3Ri_c - Ri_a - Ri_b = 0$$
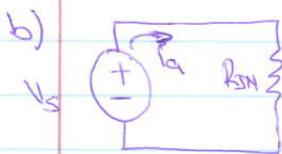
$$\Rightarrow \begin{bmatrix} 3R & -R & -R \\ -R & 3R & -R \\ -R & -R & 3R \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$




(Note: It can be understood as  
It is not problem, you can follow the same way)

The only thing that we need to do is find  $i_a$  and apply Ohm's Law ( $V_s = i_a \cdot R_N$ )

$$\begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \frac{1}{R} \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \frac{1}{R} \begin{bmatrix} 0.5 & 0.25 & 0.25 \\ 0.25 & 0.5 & 0.25 \\ 0.25 & 0.25 & 0.5 \end{bmatrix} \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$

from this equation  $i_a = \frac{V_s}{R} \cdot 0.5$   $i_c = \frac{V_s}{R} \cdot 0.25$   
 $i_b = \frac{V_s}{R} \cdot 0.25$

3.16) b) cont.)

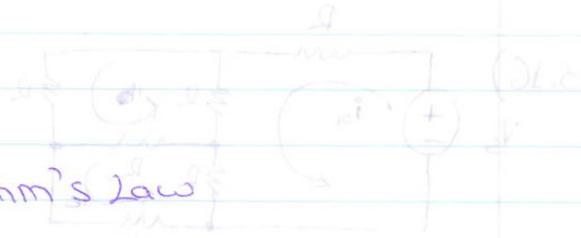


Now apply Ohm's law

$$v_s = R_{in} \cdot i_a \Rightarrow R_{in} = \frac{v_s}{i_a} \Rightarrow R_{in} = \frac{v_s}{\frac{v_s \cdot 0.5}{R}} = 2R$$

$$0 = (i_a - i_s)R + i_s R + (i_a - i_s)R$$

$$0 = i_a R - i_s R + i_s R + i_a R - i_s R$$

3.17

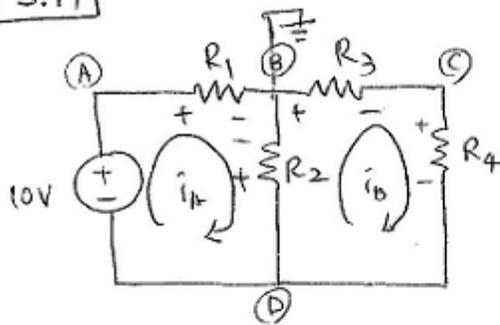

Find:  $V_A$ ,  $V_D$ ,  $i_A$  and  $i_B$

$$R_1 = R_2 = R_3 = R_4 = 1\text{ k}\Omega$$

$V_C = -2\text{V}$  when node B is connected to ground.

Mesh-current eqns:

$$\text{Mesh (A): } -10 + R_1 i_A + R_2 (i_A - i_B) = 0$$

$$\text{Mesh (B): } R_2 (i_B - i_A) + R_3 i_B + R_4 i_B = 0$$


$$\begin{bmatrix} 2000 & -1000 \\ -1000 & 3000 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$\Rightarrow \underline{i_A = 6\text{mA}}, \quad \underline{i_B = 2\text{mA}}$$

$$V_A = R_1 i_A = (1000)(6 \times 10^{-3}\text{A}) = \underline{\underline{6\text{V}}}$$

$$V_D = R_2 (i_B - i_A) = 1000(2 \times 10^{-3} - 6 \times 10^{-3}) = \underline{\underline{-4\text{V}}}$$

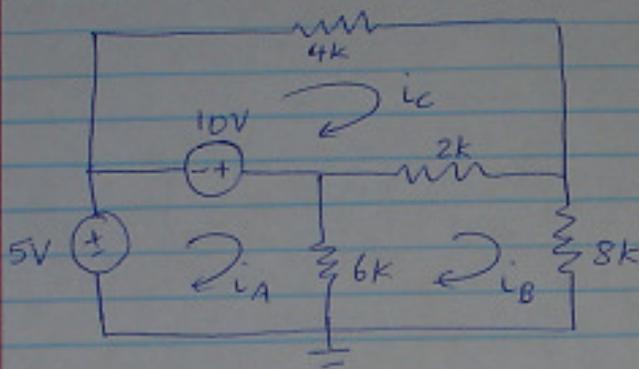3.20 Find the mesh currents  $i_A$ ,  $i_B$  and  $i_C$



KVL in Loop A

$$-5 - 10 + 6k(i_A - i_B) = 0$$

$$6ki_A - 6ki_B = 15 \quad \Rightarrow \quad i_A = \frac{15 + 6ki_B}{6k}$$

Loop B:  $2k(i_B - i_C) + 8ki_B + 6k(i_B - i_A) = 0$

$$16ki_B - 6ki_A - 2ki_C = 0$$

Loop C:  $4ki_C + 2k(i_C - i_B) + 10 = 0$

$$6ki_C - 2ki_B = -10 \quad \Rightarrow \quad i_C = \frac{-10 + 2ki_B}{6k}$$

$$\begin{bmatrix} 6k & -6k & 0 \\ -6k & 16k & -2k \\ 0 & -2k & 6k \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 15 \\ 0 \\ -10 \end{bmatrix}$$

$$16ki_B - 6k\left(\frac{15 + 6ki_B}{6k}\right) - 2k\left(\frac{-10 + 2ki_B}{6k}\right) = 0$$

$$10ki_B - \frac{2ki_B}{3} - 15 + \frac{10}{3} = 0$$

$$30ki_B - 2ki_B - 45 + 10 = 0$$


$$28ki_B = 35 \quad \Rightarrow$$

$$i_B = 1.25\text{mA}$$

$$i_A = 3.75\text{mA}$$

$$i_C = -1.25\text{mA}$$

3.27)

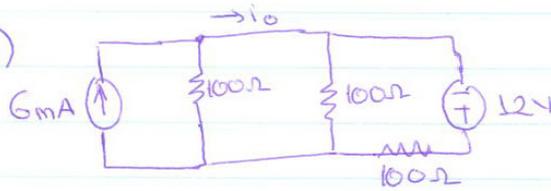


Superposition

Remember:  
Voltage Source  $\xrightarrow{\text{Replace with}}$  Short circuit


Current Source  $\xrightarrow{\text{Replace with}}$  Open circuit

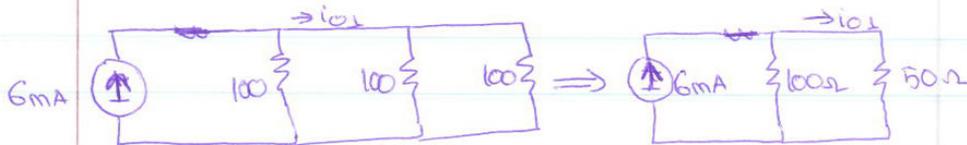Step 1: Replace voltage source with short circuit and find  $i_{o1}$



Two path current division  $i_{o1} = \frac{100\Omega}{(100+50)\Omega} \cdot 6\text{mA} = 0.4\text{mA}$

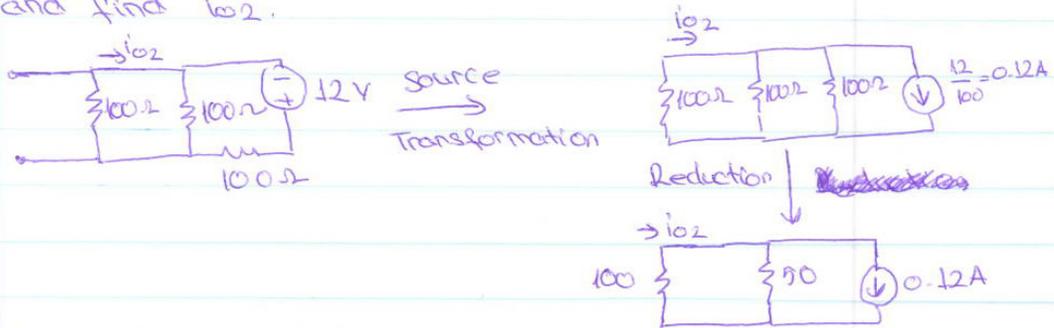Step 2: Replace current source with open circuit and find  $i_{o2}$ .




Two path current division  $i_{o2} = \frac{100\Omega}{(100+50)\Omega} \cdot 0.12\text{A} = 0.04\text{A} = 40\text{mA}$

Step 3:  $i_o = i_{o1} + i_{o2} = 0.4\text{mA} + 40\text{mA} = \underline{\underline{44\text{mA}}}$

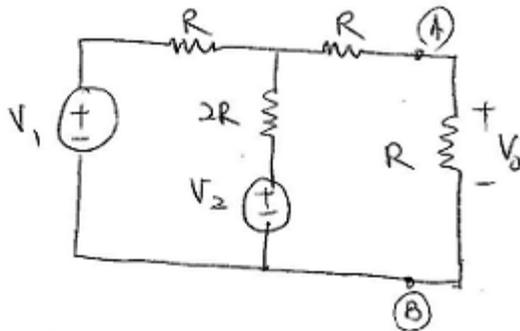
3.30

Use the superposition principle to find  $V_o$  in terms of  $V_1$ ,  $V_2$  and  $R$ .



Step 1

"turn off"  $V_2$



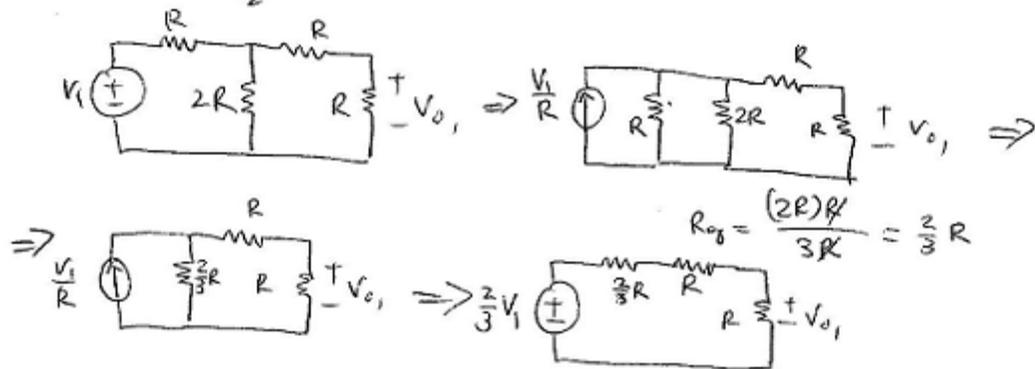


$$\begin{aligned} \therefore V_{o1} &= \frac{R}{\left(\frac{2}{3}R + R + R\right)} \left(\frac{2}{3}V_1\right) \\ &= \frac{3}{8} \left(\frac{2}{3}V_1\right) \\ &= \frac{V_1}{4} \end{aligned}$$

3

Step 2

"turn off"  $V_1$

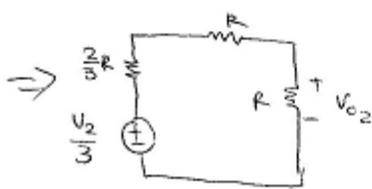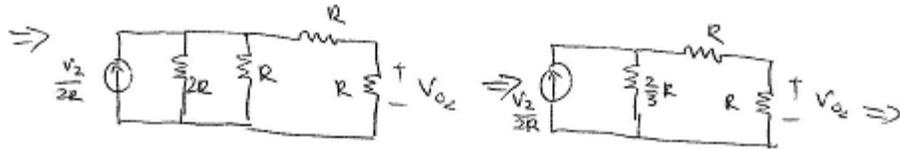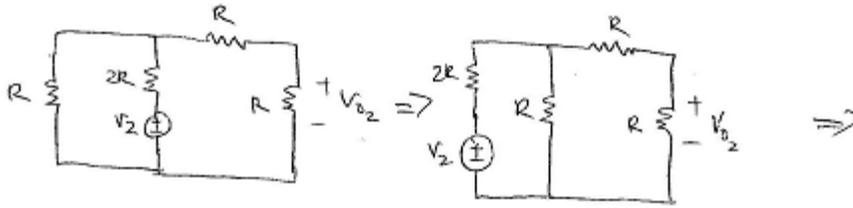

$$R_{eq} = \frac{(2R)R}{3R} = \frac{2}{3}R$$

$$\begin{aligned} \therefore V_{02} &= \frac{R}{\left(\frac{1}{3}R + R + R\right)} \left(\frac{V_2}{2}\right) \\ &= \left(\frac{3R}{8}\right) \left(\frac{V_2}{2}\right) \\ &= \frac{V_2}{8} \end{aligned}$$

$$\therefore V_0 = V_{01} + V_{02}$$

$$= \frac{V_1}{4} + \frac{V_2}{8}$$

$$= \frac{1}{8}(2V_1 + V_2)$$

3.33  $V_s = 10V$ ,  $i_s = 10mA$   
 $V_o = 2V$ ,  $i_s = \text{off}$   
 $V_o = 1V$ ,  $V_s = i_s = \text{off on}$

$$V_o = k_1 X_1 + k_2 X_2$$
$$V_o = k_1 V_s + k_2 i_s$$

$V_o = k_1 V_s$  when  $i_s = \text{off}$   
 $2V = k_1 10V$

$$k_1 = 0.2$$


$$V_o = k_1 V_s + k_2 i_s$$
$$1 = (0.2)(10) + k_2 (10mA)$$
$$1 = 2 + k_2 (10mA)$$

$$k_2 = \frac{-1}{10mA} = -0.1k$$

changing  $V_s = 5V$ ,  $i_s = -10mA$

$$V_o = k_1 V_s + k_2 i_s$$
$$V_o = (0.2)(5) + (-0.1k)(-10mA)$$
$$= 1 + 1$$

$$V_o = 2V$$

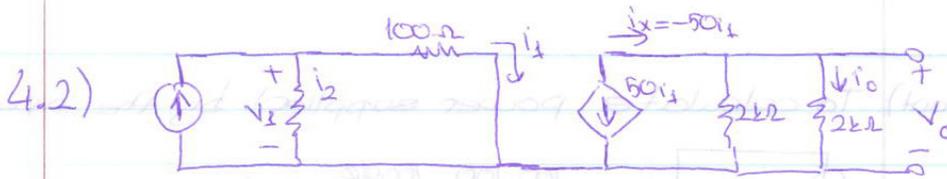

Two path current division for source part

$$i_1 = \left( \frac{100}{100+100} \right) i_s = \frac{i_s}{2} \quad i_2 = i_s - i_1 = \frac{i_s}{2}$$

Two path current division for right hand side

$$i_0 = \left( \frac{2}{2+2} \right) i_x = \frac{1}{2} (-50 i_1) = -\frac{25}{2} i_s$$

current gain  $\frac{i_0}{i_s} = \frac{-25/2 i_s}{i_s} = -\frac{25}{2}$


Calculate  $V_x$  and  $V_0$  from Ohm's Law

$$V_x = 100 i_2 = 100 \frac{i_s}{2} = 50 i_s$$

$$V_0 = 2000 \left( \frac{-25}{2} \right) i_s = -25000 i_s$$

voltage gain  $\frac{V_0}{V_x} = \frac{-25000 i_s}{50 i_s} = -500$

4.2) cont) To calculate power supplied by the input source

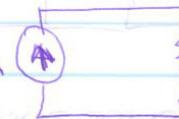$i_s = 2\text{mA}$    $R_{eq} = \frac{100 \cdot 100}{100 + 100} + \frac{100 \cdot 100}{100 + 100} = 50 \Omega$

$$P_s = (i_s)^2 \cdot 50 = 0.2 \text{ mW}$$


Calculate power delivered to  $2\text{k}\Omega$  load

Resistor  $(100 \Omega) \parallel 100 \Omega = 50 \Omega$  in series with  $2\text{k}\Omega$

$$P_o = (i_o)^2 \cdot 2\text{k}\Omega = \left( \frac{-25.2\text{mA}}{2} \right)^2 \cdot 2\text{k}\Omega$$

$$P_o = 1250 \text{ mW} = 1.25 \text{ W}$$

f.8

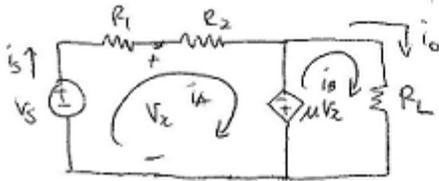

Find an expression for the current gain  $i_B/i_s$  in the circuit

### Mesh Analysis

$$\text{Mesh (A): } -V_s + (R_1 + R_2)i_A - M V_x = 0 \quad \text{--- (1)}$$

$$\text{Mesh (B): } M V_x + i_B R_L = 0 \quad \text{--- (2)}$$

plug  $V_x = V_s - i_A R_1$  into (1) & (2):

$$-V_s + (R_1 + R_2)i_A - M(V_s - i_A R_1) = 0 \quad \text{--- (3)}$$

$$M(V_s - i_A R_1) + i_B R_L = 0 \quad \text{--- (4)}$$

From (3),

$$(R_1 + R_2 + M R_1)i_A = V_s(1 + M)$$

$$i_A = \frac{V_s(1 + M)}{R_1(1 + M) + R_2}$$

From (4),


$$i_B = \frac{-M(V_s - i_A R_1)}{R_L} = -\frac{M}{R_L} \left[ V_s - \frac{V_s(1 + M)}{R_1(1 + M) + R_2} R_1 \right]$$

$$= -\frac{M}{R_L} \left[ \frac{V_s R_1(1 + M) + V_s R_2 - V_s(1 + M) R_1}{R_1(1 + M) + R_2} \right] = -\frac{M}{R_L} \left[ \frac{V_s R_2}{R_1(1 + M) + R_2} \right]$$

$$\therefore \frac{i_B}{i_s} = \frac{i_B}{i_A} = \frac{-\frac{M}{R_L} \left[ \frac{V_s R_2}{R_1(1 + M) + R_2} \right]}{\frac{V_s(1 + M)}{R_1(1 + M) + R_2}}$$

$$= \boxed{-\frac{M}{R_L} \left[ \frac{R_2}{(1 + M)} \right]}$$

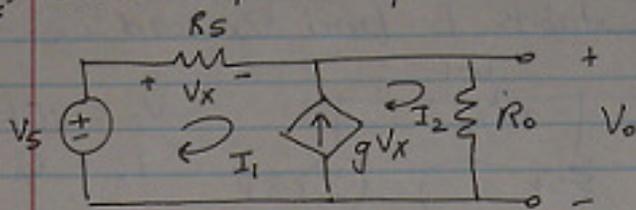4.9) Find an expression for the voltage gain  $\frac{V_o}{V_s}$



KVL in loop 1

$$-V_s + V_x + V_o = 0$$
$$V_x = V_s - V_o$$

$$V_x = I_1 R_s$$

$$V_o = I_2 R_o$$

$$I_2 - I_1 = gV_x$$

$$I_1 R_s = V_s - V_o$$

$$(I_2 - gV_x) R_s = V_s - V_o$$

$$\left(\frac{V_o}{R_o} - gV_x\right) R_s = V_s - V_o$$

$$V_o \frac{R_s}{R_o} - gV_x R_s = V_s - V_o$$

$$V_o \frac{R_s}{R_o} - gR_s(V_s - V_o) = V_s - V_o$$

$$V_o \frac{R_s}{R_o} - gR_s V_s + gR_s V_o = V_s - V_o$$

$$V_o \left(\frac{R_s}{R_o} + gR_s + 1\right) = V_s (1 + gR_s)$$

$$\frac{V_o}{V_s} = \frac{(1 + gR_s) R_o}{R_s + R_o + gR_s R_o}$$