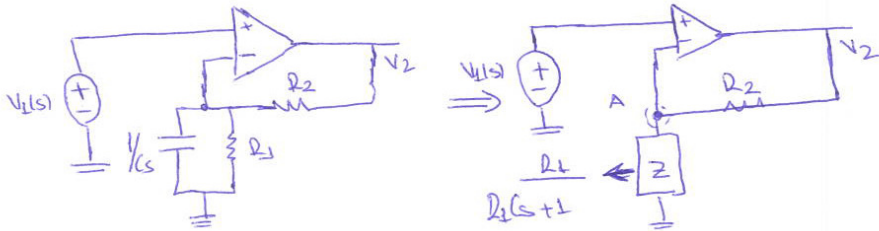


11.4) In Op-Amp $i_p = i_n = 0$, identically there is infinite resistance, then we can conclude $Z_{eq} = \infty$



$$V_A = V_1(s) = \frac{\left(\frac{R_1}{R_1 C s + 1}\right)}{R_2 + \frac{R_1}{R_1 C s + 1}} V_2(s) = \frac{R_1}{R_1 R_2 C s + R_2 + R_1} V_2(s) \quad (\text{current + division})$$

$$\Rightarrow T_V(s) = \frac{V_2}{V_1} = \frac{R_1 R_2 C s + R_2 + R_1}{R_1}$$

P.11.7 find $T_V(s)$ & select values of R & C so there is a pole @ $s = -500 \frac{\text{rad}}{\text{s}}$

inverting amplifier


$$T_V(s) = \frac{R}{R C s + 1} + R$$

$$T_V(s) = \frac{R C s + 2}{R C s + 1}$$

any values of R & C
such that $R C = \frac{1}{500}$

ex.
 $R = 1 \text{ k}\Omega$
 $C = 2 \mu\text{F}$

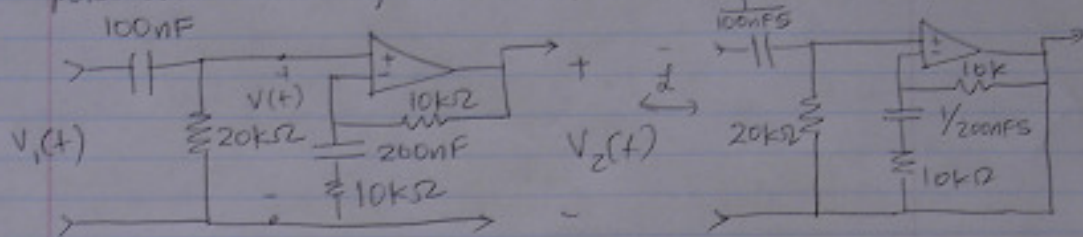11.10) Find the voltage transfer function $T_V(s) = V_2(s)/V_1(s)$ of the cascade connection in the figure below. Locate the poles and zeros of the Transfer function




$$T_1(s) = \frac{V(s)}{V_1(s)} = \frac{20k}{20k + \frac{1}{100nFs}} = \frac{2000 \times 10^6 s}{2000 \times 10^6 s + 1}$$

$$\begin{aligned} T_2(s) &= \frac{V_2(s)}{V(s)} = \frac{Z_1(s) + Z_2(s)}{Z_1(s)} = \frac{\left(10k + \frac{1}{200nFs}\right) + 10k}{10k + \frac{1}{200nFs}} \\ &= \frac{20k(200nFs) + 1}{10k(200nFs) + 1} \\ &= \frac{4000 \times 10^6 s + 1}{2000 \times 10^6 s + 1} \end{aligned}$$

$$\begin{aligned} T_V(s) &= T_1(s) \cdot T_2(s) \\ &= \left(\frac{0.002s}{0.002s + 1}\right) \left(\frac{0.004s + 1}{0.002s + 1}\right) \\ &= \frac{8 \times 10^{-6} s^2 + 0.002s}{(0.002s + 1)(0.002s + 1)} = \frac{s(8 \times 10^{-6} s + 2 \times 10^{-3})}{(0.002s + 1)^2} \end{aligned}$$

poles: $-1/2 \times 10^{-3} = \boxed{-500}$

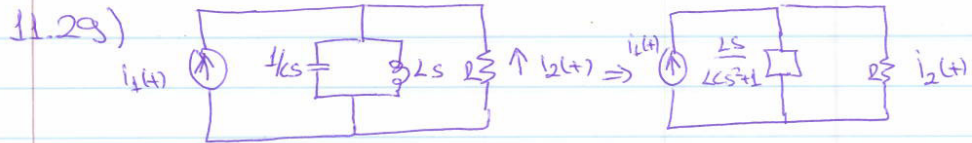zeros: $0, \frac{-2 \times 10^{-3}}{8 \times 10^{-6}} = -0.25 \times 10^3$
 $\boxed{0, -250}$



Use two path current division

$$i_2(s) = \frac{\overset{\text{because of direction}}{-} \frac{Ls}{Lcs^2+1} i_1(s)}{R + \frac{Ls}{Lcs^2+1}} \Rightarrow T(s) = \frac{i_2(s)}{i_1(s)} = \frac{-s/Rc}{s^2 + s/Rc + 1/Lc}$$

$$s = j\omega \Rightarrow |T(j\omega)| = \frac{\omega/Rc}{\sqrt{\left(\frac{1}{Lc} - \omega^2\right)^2 + \left(\frac{\omega}{Rc}\right)^2}}$$

$$\angle T(j\omega) = \angle(-j\omega/Rc) - \angle\left(\frac{1}{Lc} - \omega^2 + j\omega/Rc\right)$$

$$= \underbrace{-\frac{\pi}{2}} - \tan^{-1}\left(\frac{\omega/Rc}{\frac{1}{Lc} - \omega^2}\right)$$

for $i_1(t) = 5 \cos(\underbrace{1000t}_{\omega})$ and $R = 1000 \Omega$
 $L = 2 \mu$ and $C = 5000 e^{-9} F$

$$|T(1000j)| = 1 \quad \angle T(1000j) = -\pi$$

Then $i_2 = 5 \times 1 \cos(1000t - \pi) \text{ mA}$

for $i_1(t) = 10 \cos(2000t)$

$$|T(2000j)| = 0.8 \quad \angle T(2000j) = -1.2\pi$$

Then

$$i_2(t) = (10 \times 0.8 \cos(2000t - 1.2\pi))$$


$$= 8 \cos(2000t - 1.2\pi)$$

P.11.53 Design a circuit to fit $T_V(s) = \pm \frac{1000s}{(s+500)(s+1000)}$

using only resistors, capacitors & not more than one OP-AMP
 - scale it so that the final design uses only 20kΩ resistors

$$T_V(s) = \frac{k_1}{s+500} \frac{k_2 s}{s+1000}$$

ex.

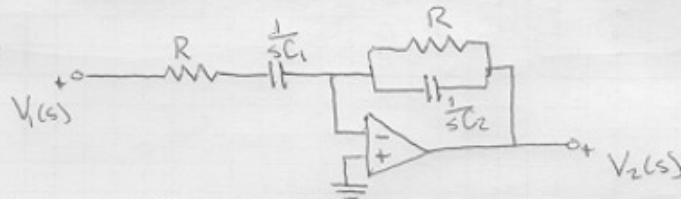

inverting amplifier

$$\text{Gain} = -\frac{Z_2}{Z_1}$$

in example $Z_2 = \frac{1}{\frac{1}{R} + sC_2} = \frac{R}{RC_2s + 1}$

$$Z_1 = R + \frac{1}{sC_1} = \frac{RC_1s + 1}{C_1s}$$

$$T_V(s) = -\frac{Z_2}{Z_1} = -\frac{R}{RC_2s + 1} \frac{C_1s}{RC_1s + 1}$$

$$= -\frac{1}{RC_2} \frac{1}{s + \frac{1}{RC_2}} \frac{s}{s + \frac{1}{RC_1}}$$


if $R = 20\text{k}\Omega$
 $C_1 = 100\text{nF}$
 $C_2 = 50\text{nF}$

$$T_V(s) = -\frac{1000s}{(s+500)(s+1000)}$$

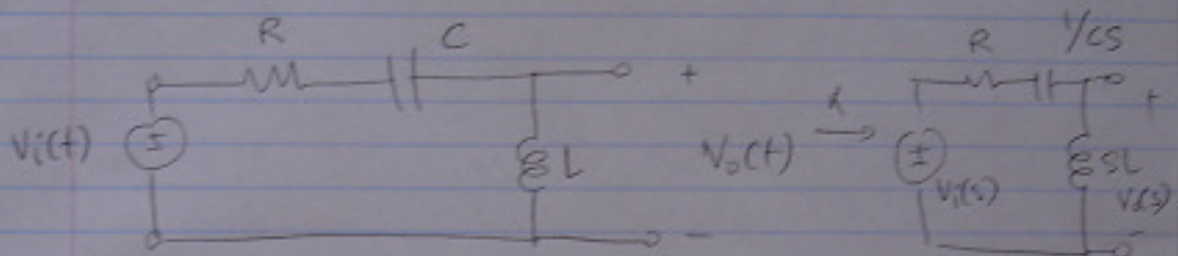11.54) Design a circuit to realize the TF below using only resistors, capacitors, and inductors (no op-Amps allowed). Scale the circuit so that all inductors are 50mH or less.

$$T_V(s) = \frac{s^2}{(s+2000)(s+4000)}$$

$$T_V(s) = \frac{s^2}{s^2 + 6000s + 8 \times 10^6} = \left(\frac{s}{s+2000} \right) \left(\frac{s}{s+4000} \right)$$



$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)} = \frac{sL}{R + \frac{1}{Cs} + sL}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{LCs^2}{RCs + 1 + LCs^2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{s^2}{s^2 + 6000s + 8 \times 10^6}$$

$$\frac{R}{L} = 6000 \quad \frac{1}{LC} = 8 \times 10^6$$


$$L = 50 \times 10^{-3} \text{ H}$$

$$\Rightarrow R = 6000 \times 50 \times 10^{-3} = 300000 \times 10^{-2} = 300 \Omega$$

$$C = \frac{1}{5 \times 10^{-2} \times 8 \times 10^6} = \frac{10^{-4}}{40} = 3 \mu\text{F}$$

9 3

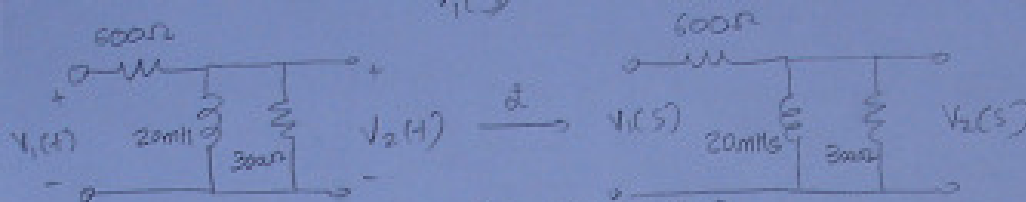12-2 Find the $T_V(s) = \frac{V_2(s)}{V_1(s)}$



$$T_V(s) = \frac{Z_2}{Z_1 + Z_2} = \frac{(300)(200 \text{ mS})}{300 + 200 \text{ mS}} \\ = \frac{60 \text{ S}}{600 \Omega + \frac{60 \text{ S}}{300 + 0.25}} = \frac{60 \text{ S}}{180 \text{ S} + 18000} \\ T_V(s) = \frac{\frac{1}{3} \text{ S}}{s + 100}$$


a.) DC gain $|k|$ ($|T(j\omega)| \rightarrow T_{max}$)

$$|k| = \frac{1}{3}$$

$$|T(j\omega)| = \frac{\frac{1}{3} \omega}{\omega + 100} = \frac{\frac{1}{3}}{1 + \frac{100}{\omega}} = \frac{1}{3} \quad \text{Infinite frequency gain}$$

Cutoff frequency $\omega_c = 100 \text{ rad/s}$

Type of gain response: 1 order High Pass

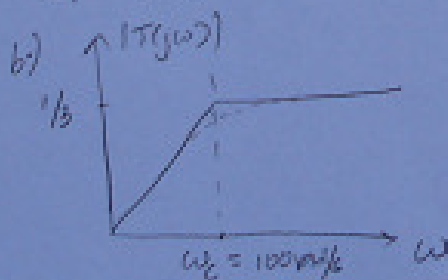

c.) i) $|T(j0.5\omega_c)| = |T(j50)|$

$$|T(j\omega)| = \frac{\frac{1}{3} \omega}{\sqrt{\omega^2 + 100^2}} \\ |T(j50)| = \frac{\frac{1}{3}(50)}{\sqrt{50^2 + 100^2}} = 0.149$$

ii) $\omega = \omega_c = 100 \text{ rad/s}$

$$|T(j100)| = \frac{\frac{1}{3}(100)}{\sqrt{100^2 + 100^2}} = 0.2357$$

iii) $\omega = 2\omega_c = 200 \text{ rad/s}$

$$|T(j200)| = \frac{\frac{1}{3}(200)}{\sqrt{200^2 + 100^2}} = 0.298$$


P.12.10 a) Identify the gain response, cutoff frequency & passband gain for $T(s) = \frac{10/s}{100/s + 1/20}$

b) Sketch straight line gain response & estimate the gain for $0.5\omega_c$, ω_c , $2\omega_c$

a) $|T(0)| \rightarrow 1/10$ $|T(\infty)| \rightarrow 0$ **Low - Pass**



$$\omega_c = 2000 \frac{\text{rad}}{\text{s}}$$

passband gain $|T(0)| = \frac{1}{10}$

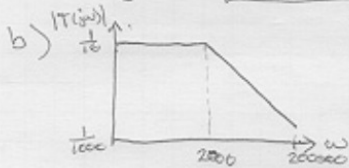

$$\begin{aligned} |T(0.5\omega_c)| &\approx \frac{1}{10} \\ |T(\omega_c)| &\approx \frac{1}{10\sqrt{2}} \\ |T(2\omega_c)| &\approx \frac{1}{60} \end{aligned}$$

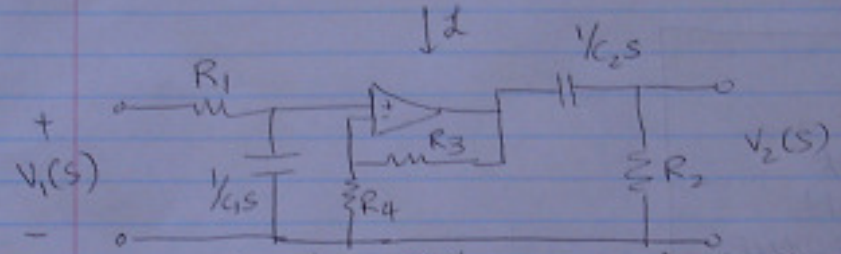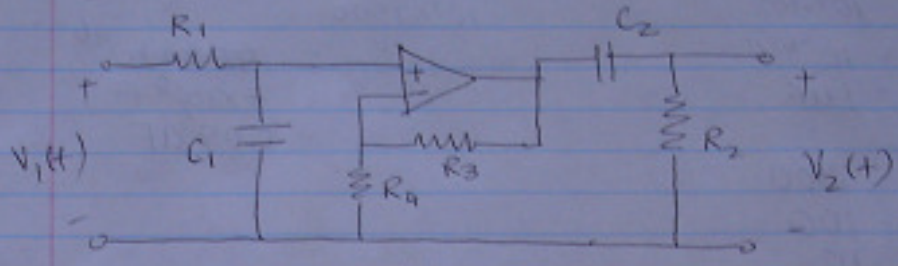12-14 Identify the elements that control the two cutoff frequencies. Select the element values so that the passband gain is 10, and the cutoff frequencies are 100 rad/s and 2500 rad/s. Use practical element values with $R \geq 10k\Omega$ and $C \leq 1\mu F$.



$$T_V(s) = \left(\frac{\frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} \right) \left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{R_2}{R_2 + \frac{1}{C_2 s}} \right)$$

$$= \left(\frac{1}{R_1 C_1 s + 1} \right) \left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{R_2 C_2 s}{R_2 C_2 s + 1} \right)$$

$$T_V(j\omega) = \left(\frac{|k_1|}{\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2}} \right) (k_3) \left(\frac{|k_2| \omega}{\sqrt{\omega^2 + \left(\frac{1}{R_2 C_2}\right)^2}} \right)$$

$$d_1 = \frac{1}{R_1 C_1} \quad k_1 = 1/R_1 C_1 \quad k_2 = 1/R_2 C_2$$

$$d_2 = \frac{1}{R_2 C_2} \quad k_3 = 10$$

$R_4 + R_3 = 10 R_4$ if $R_3 = 100k$
 $9 R_4 = R_3$ $R_4 = \frac{100k}{9} = 11.11k\Omega$

$$100 = \frac{1}{R_2 C_2}$$

$$2500 = \frac{1}{R_1 C_1}$$

if $R_2 = 10k$

$$C_2 = \frac{1}{10^4 \cdot 10^2}$$

$$= 10^{-6} F$$

$$= 1 \mu F$$

if $R_1 = 10k$

$$C_1 = \frac{1}{10^4 \times 2500}$$

$$= \frac{10^{-6}}{25} = ~~400 \times 10^{-6}~~^{-6}$$

$$= 4 \times 10^{-8} F$$

$$= 0.04 \mu F$$

$$K_1 = 2500$$

$$K_2 = 100$$

$$K_3 = 10$$

$$R_1 = 10k$$

$$R_2 = 10k$$

$$R_3 = 100k$$


$$R_4 = 11.11k$$

$$C_1 = 0.04 \mu F$$

$$C_2 = 1 \mu F$$

9 3:26

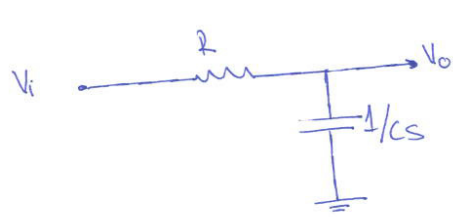12.54) This is basically low-pass filter.



$$V_o = \frac{1/cs}{R + 1/cs} V_i$$

$$V_o = \frac{1}{RCs + 1} V_i \Rightarrow T(s) = \frac{1}{RCs + 1}$$

The magnitude of the transfer function is

$$|T(j\omega)| = \left| \frac{1}{1 + jRC\omega} \right| = \frac{1}{\sqrt{R^2 C^2 \omega^2 + 1}}$$

units are given as dB then

$$|T(j\omega)|_{dB} = 20 \log_{10} (|T(j\omega)|)$$

the frequency of RF noise = $3.2 \text{ MHz} = 3.2 \times 10^6 \times 2\pi \text{ rad/sec}$
 " " " signal data = $1.1 \text{ MHz} = 1.1 \times 10^6 \times 2\pi \text{ rad/sec}$

for RF noise $|T(j\omega)|_{dB} \leq -7 \text{ dB}$

for signal data $|T(j\omega)|_{dB} \geq -2 \text{ dB}$

We need to try the values which are given in Table 12.54. and observe which value is best for that purpose.

for 2AEN46 ($R = 470 \Omega$ and $C = 1000 \text{ pF}$)

$$|T(j(\text{signal data}))|_{dB} \approx -1.06$$

$$|T(j(\text{RF noise}))|_{dB} \approx -7.00$$