

**MAE 140 – Linear Circuits – Winter 2009  
Midterm**

**Instructions**

- 1) This exam is open book. You may use whatever written materials you choose, including your class notes and textbook. You may use a hand calculator with no communication capabilities.
- 2) You have 70 minutes.
- 3) Write your name, student number and instructor.

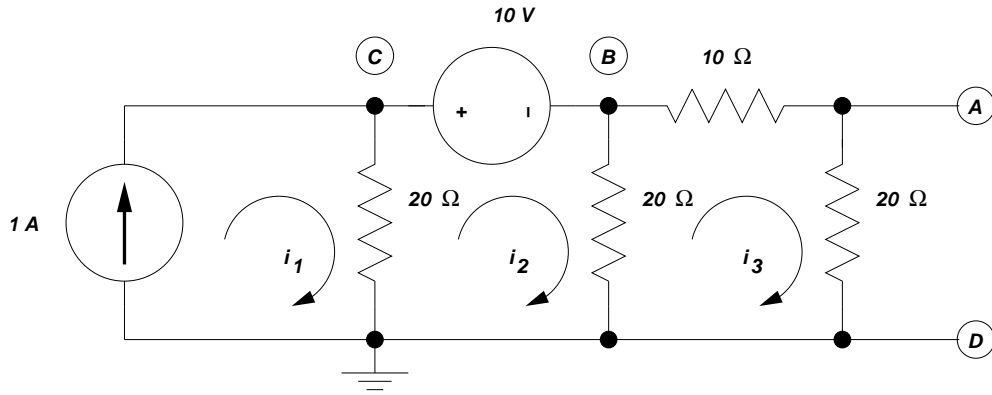


Figure 1: Circuit for questions 1-4.

**Questions**

**1. Equivalent circuits**

- (a) (2 points) Turn off all the sources in the circuit of Figure 1 and find the equivalent resistance as seen from terminals A and D.
- (b) (3 points) Find the Thévenin equivalent as seen from terminals A and D.
- (c) (1 point) Find the power absorbed by a  $10\ \Omega$  resistor if connected to terminals A and D.

**2. Mesh current analysis**

- (a) (6 points) Formulate mesh-current equations for the circuit in Figure 1. Use the mesh currents shown in the figure and clearly indicate how you handle the presence of a current source, the final equations and the unknowns they must be solved for. **Do not modify the circuit or the labels in any way. Do not use source transformation. Do not solve any equations!**

**3. Nodal voltage analysis**

- (a) (6 points) Assuming that the node labeled D is the ground node (reference), formulate node-voltage equations for the circuit in Figure 1. Use the node labels provided in the figure and clearly indicate how you handle the presence of a voltage source, the final equations, and the unknowns they must be solved for. **Do not modify the circuit or the labels in any way. Do not use source transformation. Do not solve any equations!**  
*Hint: Use a super-node.*

**4. Bonus Question**

- (a) (1 point) If you were allowed to modify the circuit in Figure 1, describe what would you do in order to avoid having to use a super-node in Question 3? **Do not write or solve any equations!**